

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations July-2021

Analog Electronic Circuits

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 Draw the block diagram of CE-CC cascaded amplifier and analyze its various parameters. 12M

OR

- 2 Let us consider the two stage amplifier, the first stage in the circuit is a CE amplifier and second stage is CC amplifier, calculate R_i , A_i , A_v , R_o , A_{vs} and A_{is} if circuit parameters are: $R_s=1K$, $R_{c1} = 3.3K$, $R_{E2}= 4.7k\Omega$. Assume that $h_{ic}= 2k$, $h_{fe} = 50$, $h_{re} = 0$ and $h_{oc} = 0$. 12M

UNIT-II

- 3 Derive the expressions of input and output resistances for Voltage Shunt Feedback amplifiers. 12M

OR

- 4 a Give the detailed analysis of Current Series feedback amplifier. 7M
b Calculate the gain, input impedance and output impedance of voltage series feedback Amplifier having gain $A = -300$, $R_{in} = 1.5 k\Omega$ and $R_{out} = 50 k\Omega$, $\beta = 0.05$. 5M

UNIT-III

- 5 a Draw the circuit diagram of RC phase shift Oscillator and Explain its working. 6M
b Explain the concept of frequency stability of Oscillators. 6M

OR

- 6 a Draw the circuit diagram of Colpitts oscillator and explain its working. 7M
b Find the frequency of the oscillations of a transistorized Colpitts oscillator having $C_1 = 150 pF$, $C_2 = 1.5nF$ and $L = 50 \mu H$. 5M

UNIT-IV

- 7 a Draw the circuit diagram of push pull class B amplifier and explain its working principle. 7M
b Write short note on power output and efficiency of class A power amplifiers. 5M

OR

- 8 a Draw the circuit diagram of complementary symmetry class B amplifier and explain its working principle. 7M
b For a transistor, $T_j = 160^\circ C$, $T_A = 40^\circ C$, and $\Theta_{j-A} = 80^\circ C/W$. Calculate the power that the transistor can safely dissipate in free air. 5M

UNIT-V

- 9 a How High pass RC circuit be used as a Differentiator. 6M
b Derive the Response of a low pass RC circuit for Step input. 6M

OR

- 10 a With help of diagram explain the operation of Bi-stable Multivibrator. 6M
b Explain the positive clamper circuit with wave forms. 6M

*** END ***