

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

B.Tech II Year II Semester Supplementary Examinations July-2021

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Mechanical Engineering)

Time: 3 hours


Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

PART-A

UNIT-I

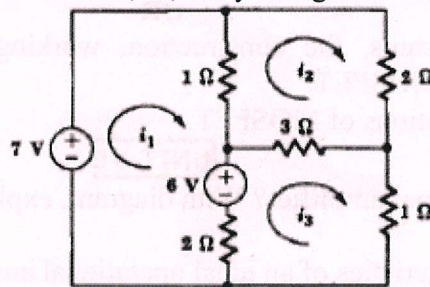- 1 a State and prove Kirchoff law's with an example 5M
 b In the circuit shown below find i_1, i_2, i_3 by using Kirchoff's laws? 5M




OR

- 2 a Define RMS value, average value, form factor and peak factor. 5M
 b Explain about passive elements in detail 5M


UNIT-II

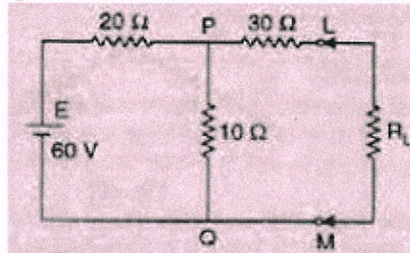- 3 a State Nortons theorem 2M
 b Determine the maximum power delivered to the load in the circuit shown in fig. 8M



OR

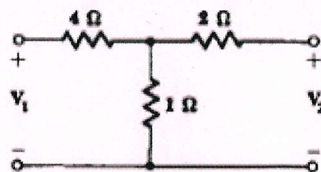- 4 Find the Open circuit parameters for the circuit shown in fig. 10M



UNIT-III

- 5 a Derive Torque equation of dc motor. 5M
 b Calculate the value of Torque established by the armature of a 4-pole motor having 774conductors, 2 paths in parallel, 24mwb flux per pole when the total Armature current is 50A. 5M

OR

- 6 a Explain principle of operation of transformer. 5M
 b Derive EMF equation of a transformer. 5M

PART-B**UNIT-IV**

- 7 Describe the working of a PN junction diode when it is connected in forward bias And reverse bias. Draw VI Characteristics of PN Junction Diode. **10M**

OR

- 8 Discuss Zener Diode breakdown mechanism. Draw the Zener diode in its reverse bias and explain its Volt-Ampere characteristics. **10M**

UNIT-V

- 9 a Draw the circuit diagram for a common base circuit arrangement and plot its input and Output characteristics. Show the different regions of the output characteristics and explain their occurrence. **5M**

- b Discuss with neat diagrams, the Common Emitter Configuration and its characteristics. **5M**

OR

- 10 a Explain with diagrams, the construction, working and characteristics of N-channel Depletion MOSFET. **5M**

- b Mention the applications of MOSFET. **5M**

UNIT-VI

- 11 a What is an operational amplifier? With diagram, explain single input and dual Input Op Amps. **5M**

- b Discuss the Characteristics of an ideal operational amplifier. **5M**

OR

- 12 a Explain Differential Amplifier with neat diagram. **5M**

- b In the inverting amplifier of op amp circuit, the input resistance is $R_i = 12K\Omega$ and The feedback resistance is $R_f = 300k\Omega$. Determine the closed loop gain (i) as a dimension-less unit and (ii) in dB. **5M**

***** END *****