

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Supplementary Examinations August-2021

SWITCHING THEORY AND LOGIC DESIGN

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Perform the following 6M
 i) Subtraction by using 10's complement for the given $3456 - 245$.
 ii) Subtraction by using 2's complement for the given $111001 - 1010$.
 b i) State Duality theorem. List Boolean laws and their Duals. 6M
 ii) Simplify the following Boolean expressions to minimum no. of literals.
 $(BC' + A'D)(AB' + CD')$

OR

- 2 a i) Perform the following using BCD arithmetic $(79)_{10} + (177)_{10}$ 6M
 ii) Convert the following to gray code $(BC54)_{16}$
 b Write expressing in canonical form $F = (A+B)(B+C)$ 6M

UNIT-II

- 3 a Minimize the following Boolean function using K-Map 6M
 $F(A,B,C,D) = \sum(1,3,7,11,15) + d(0,2,5)$
 b Simplify the following Boolean function for minimal POS form using K-map 6M
 $F(X,Y,Z) = X'YZ + XY'Z' + XYZ + XYZ$

OR

- 4 a Minimize the given Boolean function $F(A,B,C,D) = \sum m(0,1,2,3,6,7,13,15)$ using 7M
 tabulation method and implement using basic gates.
 b Implement the following Boolean equation using only NAND gates $Y = AB + CDE + F$. 5M

UNIT-III

- 5 a Design & implement a 4-bit Binary-To-Gray code converter. 6M
 b Design & implement Full Adder using Decoder. 6M

OR

- 6 a What is encoder? Design octal to binary encoder. 5M
 b Explain Carry Look Ahead Adder circuit with the help of logic diagram. 7M

UNIT-IV

- 7 a Design D Flip Flop by using SR Flip Flop and draw the timing diagram. 6M
 b With a neat sketch explain MOD 6 Johnson counter using D FF. 6M

OR

- 8 a Draw the circuit of JK flip flop using NAND gates and explain its operation. 6M
 b Design a binary counter having repeated binary sequence using JK flip flops: 6M
 $0,1,2,4,5,6$.

UNIT-V

- 9 a Implement the following Boolean function using PLA 6M
 $F_1(w,x,y,z) = \sum m(0,1,3,5,9,13)$ $F_2(w,x,y,z) = \sum m(0,2,4,5,7,9,11,15)$
 b Discuss Mealy & Moore Machine models of sequential machines. 6M

OR

- 10 a Give the logic implementation of a 32×4 bit ROM using a decoder of a suitable figure. 6M
 b Differentiate among ROM, PROM, DROM, EPROM, EEPROM, and RAM. 6M

*** END ***