

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Supplementary Examinations August-2021

ELECTRONIC MEASUREMENTS AND INSTRUMENTATION

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Explain with the help of circuit diagram the construction & working of a series type ohm meter. **8M**
 b Define sensitivity. Calculate the sensitivity of a 200 μ A meter movement which is to be used as a dc voltmeter. **4M**

OR

- 2 a Explain with the help of circuit diagram the construction & working of a series type ohm meter. **6M**
 b With neat sketch explain thermocouple type RF ammeter. **6M**

UNIT-II

- 3 a Explain with the block diagram how the digital frequency and time period can be measured using Counter/meter instrument. **8M**
 b Draw the neat diagrams of vertical deflection systems and explain briefly about their working. **4M**

OR

- 4 a Explain the major parts of CRT with a block diagram. **7M**
 b Discuss in detail, the construction and working of a digital sampling oscilloscope. **5M**

UNIT-III

- 5 a With help of a neat sketch, explain the working of a frequency selective wave analyser. **6M**
 b Explain how wave analyser can be tuned to a particular frequency within the audible frequency range. **6M**

OR

- 6 a Describe the diagram with operation of a harmonic distortion analyser using Wein bridge and frequency selective type. **5M**
 b Draw the circuit diagram and explain the working of a heterodyne type wave analyser. **7M**

UNIT-IV

- 7 a Describe the operation of the Wheatstone bridge and derive the expression for DC resistance. **6M**
 b A Maxwell bridge is used to measure an inductive impedance the bridge constants at balance are $C_1=0.01 \mu\text{F}$, $R_1=470\text{K}\Omega$, $R_2=5.1 \text{K}\Omega$ and $R_3=100 \text{K}\Omega$. Find the series equivalent of the unknown impedance. **6M**

OR

- 8 a Draw the Anderson's bridge circuit and derive necessary equations & explain it. **6M**
 b List the applications of Schering bridge circuit. **6M**

UNIT-V

- 9 a With a neat sketch explain the operation of LVDT. 8M
- b Define a transducer. List the applications. 4M

OR

- 10 a Draw the diagram of Resistance Thermometer & explain briefly. 6M
- b Discuss about signal conditioning circuits. 6M

*** END ***