

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations March-2021

ELECTRONIC CIRCUIT ANALYSIS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Compare the CE, CB and CC transistor amplifier parameters. 6M
b With neat diagram, derive the CE amplifier parameters using approximate analysis. 6M

OR

- 2 a Obtain the expression for current gain, voltage gain, input impedance and output impedance for Common Emitter Amplifier with Emitter Resistor. 6M
b Draw the circuit diagram of a single stage RC coupled Amplifier and discuss the steps used for designing it. 6M

UNIT-II

- 3 a Draw the Hybrid- π model and explain the significance of each and every component in it. 6M
b Mention the typical values of Hybrid- π parameters. 6M

OR

- 4 a Describe the relationship between low frequency h-parameters and high frequency Parameters. 8M
b Write about Collector junction capacitance and Emitter junction capacitance of hybrid- π model. 4M

UNIT-III

- 5 Describe different methods used for coupling multistage amplifiers with their frequency response. 12M

OR

- 6 a Explain the effect of cascading of amplifiers on bandwidth. 6M
b An amplifier consists of 3 identical stages in cascade; the bandwidth of overall amplifier extends from 20 Hz to 20 kHz. Calculate the bandwidth of individual stage. 6M

UNIT-IV

- 7 Explain the characteristics of negative feedback amplifiers 12M

OR

- 8 a Discuss the working principle of Wein-bridge oscillator and derive the expression for Frequency of oscillations. 6M
b Explain the concept of stability of Oscillators. 6M

UNIT-V

- 9 a Discuss with diagram, Transformer coupled Class A Power Amplifier and derive its Maximum efficiency. 6M
b Describe Higher order harmonic distortion by five point method. 6M

OR

- 10 a Explain the effect of cascading single tuned amplifiers on bandwidth. 6M
b Explain the advantages, disadvantages and applications of Tuned Amplifiers. 6M

*** END ***