

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations March-2021

SWITCHING THEORY AND LOGIC DESIGN

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 Convert the following to Decimal and then to Octal 12M
- i) $(1234)_{16}$
 - ii) $(12EF)_{16}$
 - iii) $(10110011)_2$
 - iv) $(10001111)_2$
 - v) $(352)_{10}$
 - vi) $(999)_{10}$

OR

- 2 Simplify the following Boolean expression:
- a $F = (A+B)(A'+C)(B+C)$ 6M
 - b $F = A+B+C'+D(E+F)$ 6M

UNIT-II

- 3 a Minimize the following Boolean function using K-Map 6M
 $F(A, B, C, D) = \sum m(0, 2, 4, 6, 8, 10, 12, 14)$.
- b Realize it using NAND Gates. 6M

OR

- 4 Simplify the following Boolean function using Tabulation method 12M
 $Y(A, B, C, D) = \sum (1, 3, 5, 8, 9, 11, 15)$

UNIT-III

- 5 What is encoder? Design octal to binary encoder. 12M

OR

- 6 a Implement the following Boolean function using 8:1 multiplexer. 5M
 $F(A, B, C, D) = A'BD' + ACD + B'CD + A'C'D$.
- b What is multiplexer? Construct 4*1 multiplexer with logic gates and truth table. 7M

UNIT-IV

- 7 a Design D Flip Flop by using SR Flip Flop and draw the timing diagram. 6M
- b Write the differences between combinational and sequential circuits. 6M

OR

- 8 Design a binary counter having repeated binary sequence using JK flip flops: 0,1,2,4,5,6. 12M

UNIT-V

- 9 Explain the minimization procedure for determining the set of equivalent state of a specified machine M. 12M

OR

- 10 Given the 8-bit data word 01011011, generate the 12-bit composite word for the hamming code that corrects and detects single errors. 12M

*** END ***