

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)**

**B.Tech I Year I Semester Regular & Supplementary Examinations May-2022**

**BASIC ELECTRICAL & ELECTRONICS ENGINEERING**

(Mechanical Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)


**PART-A**

**UNIT-I**

- 1 a Write the derivation for equivalent resistance in series circuit. L3 5M  
 b A 5 ohm, 10 ohm, 20 ohm, resistors are connected in series across 120V DC supply calculates Total Resistance, Total current, Voltage drop across each resistor. L4 5M

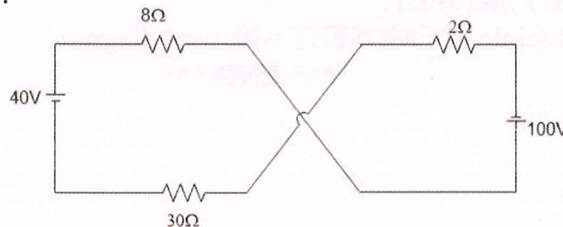**OR**


- 2 Find the voltage across 30 ohm resistor and current across 30 ohm resistor given circuit as shown below. L2 5M



- b Write the derivation of RMS Value of Alternating voltage L3 5M

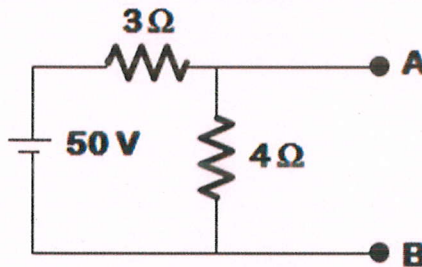**UNIT-II**

- 3 a State Thevenin's theorem L1 2M  
 b Find the Thevenin's equivalent circuit across AB for the circuit shown. L3 8M



**OR**

- 4 Write the constructional features of a DC machine with neat diagram. L3 10M

**UNIT-III**

- 5 a Discuss about the principle of operation of DC motors L5 5M  
 b Calculate the value of torque established by the armature of a 4-pole DC motor having 774 conductors, 2 paths in parallel, 24mwb flux per pole when the total armature current is 50A. L5 5M

**OR**

- 6 a Derive EMF equation of a transformer. L3 6M  
 b A 100 kVA, 11000/400 V, 50 Hz transformer has 40 secondary turns. Calculate the number of primary turns and primary and secondary currents. L4 4M

**PART-B****UNIT-IV**

- 7 a Distinguish between conductors, semiconductors and insulators. L4 5M  
 b Discuss why an intrinsic semiconductor is relatively a poor conductor L3 5M

**OR**

- 8 a Explain the working principle of Bridge Wave Rectifier. Draw its input and output waveforms with neat circuit diagram. L2 5M  
 b Explain the working principle of rectifiers with capacitor filter. L2 5M

**UNIT-V**

- 9 a Discuss the operation of PNP transistor with neat diagram. L1 5M  
 b If the base current in a transistor is  $20\mu\text{A}$  when the emitter current is  $6.4\text{mA}$ , what are the values of  $\alpha$  and  $\beta$ ? Also calculate the collector current. L4 5M

**OR**

- 10 Explain the Fixed Bias of a BJT with a neat diagram. L2 10M

**UNIT-VI**

- 11 a With a neat diagram explain the Drain characteristics of N-channel JFET. L2 5M  
 b Compare between CS, CG, CD configuration of JFET. L4 5M

**OR**

- 12 a Compare between BJT and JFET. L4 5M  
 b Explain working principle of EMOSFET with neat diagram. L2 5M

\*\*\* END \*\*\*