

**Reg. No:**

--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year II Semester Supplementary Examinations October-2020**

**ANALOG ELECTRONIC CIRCUITS**

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

**UNIT-I**

- 1 Describe different methods used for coupling multistage amplifiers with their frequency response. **12M**

**OR**

- 2 With neat diagram, analyze the two stage RC coupled amplifier. **12M**

**UNIT-II**

- 3 **a** Explain Feedback topologies. **8M**  
**b** Give the detailed analysis of Current Series feedback amplifier. **4M**

**OR**

- 4 **a** Draw the block diagram of an amplifier with feedback and explain its concept. **7M**  
**b** Derive the stabilization gain of negative feedback amplifier. **5M**

**UNIT-III**

- 5 **a** Draw the circuit diagram of Colpitts oscillator and explain its working. **5M**  
**b** In Colpitts oscillator,  $C_1 = 0.2 \mu\text{F}$  and  $C_2 = 0.02 \mu\text{F}$ . if the frequency of the oscillator is 10 KHz, find the value of the inductor. Also find the required gain for oscillation. **7M**

**OR**

- 6 **a** State and explain Barkhausen criterion of Oscillations. **6M**  
**b** In a Hartley oscillator, the value of the capacitor in the tuned circuit is 500 pF and the two sections of coil have inductances 38  $\mu\text{H}$  and 12  $\mu\text{H}$ . Find the frequency of oscillations and the feedback factor  $\beta$ . **6M**

**UNIT-IV**

- 7 **a** Explain the classification of amplifiers based on the based on biasing condition. **6M**  
**b** Write short note on class A amplifiers. **6M**

**OR**

- 8 **a** Explain about Power dissipation thermal stability for a transistor. **6M**  
**b** In a class B amplifier,  $V_{CE(\text{min})} = 2\text{V}$  and supply voltage  $V_{CC} = 15\text{v}$ . Find the collector circuit efficiency. **6M**

**UNIT-V**

- 9 **a** Derive the response of a high pass RC circuit for step Input. **6M**  
**b** How High pass RC circuit be used as a Differentiator. **6M**

**OR**

- 10 **a** Derive the Response of a low pass RC circuit for Step input. **6M**  
**b** Determine the upper 3-dB frequency for low pass RC circuit, if a pulse of 0.4  $\mu\text{sec}$  is required to pass without distortion. Find the value of resistance if the capacitor is 0.001 $\mu\text{F}$ . **6M**

\*\*\* END \*\*\*