

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Supplementary Examinations November-2020

LINEAR IC APPLICATIONS

(Common to EEE & ECE)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 Calculate the amplification factor for AC signal input in dual input balanced output differential amplifier. **12M**

OR

- 2 a Explain how the constant current bias circuit is replaced by the current mirror circuit. **6M**
b Explain and derive the current expression of current mirror circuit diagram **6M**

UNIT-II

- 3 Explain in detail about external frequency compensation techniques with neat sketches. **12M**

OR

- 4 a Explain the importance of the stability criterion of the op-amp. **6M**
b Define the total input offset voltage and thermal drift. **6M**

UNIT-III

- 5 Draw the circuit diagram of the instrumentation amplifier and derive the gain. **12M**

OR

- 6 Explain the operation of first order low pass butter worth filter & derive the expression for filter gain & draw a neat sketch of frequency response. **12M**

UNIT-IV

- 7 a Explain the comparator and zero crossing detector. **6M**
b Explain the operation of Schmitt trigger. Discuss its characteristics & limitations. **6M**

OR

- 8 a Using op-amp, explain how to generate a triangular wave from the square wave. **6M**
b Explain the operation of Wein bridge oscillator and derive its frequency expression with neat circuit diagram. **6M**

UNIT-V

- 9 Draw the circuit diagram of single Slope ADC and explain its working with neat sketches. **12M**

OR

- 10 a Draw and explain the weighted resistor DAC. **6M**
b Explain ladder type DAC with a neat circuit diagram. **6M**

*** END ***