

Reg. No:

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**B.Tech III Year II Semester Regular & Supplementary Examinations October-2020**
DIGITAL IC APPLICATIONS

(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Draw the circuit diagram of basic TTL NAND gate and explain the three parts with the help of functional operation. **7M**
- b Explain TTL and CMOS interfacing. **5M**

OR

- 2 a Design CMOS transistor circuit for 2-input AND gate. With the help of function table, explain the circuit **6M**
- b Design a CMOS circuit that has the functional behavior $f(Z)=A.(B+C)$. **6M**

UNIT-II

- 3 Design the logic circuit and write VHDL program for the following functions
- a $F(X) = \Sigma A, B, C, D (0, 2, 5, 7, 8, 10, 13, 15) + d (1, 6, 11)$. **6M**
- b $F(Y) = \Pi A, B, C, D (1, 4, 5, 7, 9, 11, 12, 13, 15)$. **6M**

OR

- 4 a What is the importance of time dimension in VHDL and explain **6M**
- b Explain the behavioral design elements of VHDL. **6M**

UNIT-III

- 5 a Write a VHDL code for 4-bit ALU IC 74x181. **6M**
- b Draw the structure of a 4-bit comparator and briefly explain about it. Write a structural VHDL code for it. **6M**

OR

- 6 a Design a Full adder with Half adders logic circuit. **6M**
- b Write VHDL code for the above design in structural model. **6M**

UNIT-IV

- 7 a Draw the standard IC diagram of 74x194 and explain its operation. Write VHDL code for 74X194. **8M**
- b What do you mean by self-correcting counter. **4M**

OR

- 8 a Design a 4-bit Johnson Counter and explain its operation. **6M**
- b Write a VHDL code for the above design. **6M**

UNIT-V

- 9 a Distinguish between the synchronous and asynchronous counters. **6M**
- b What are the impediments to synchronous design? **6M**

OR

- 10 a Design an 8 bit serial in and parallel out shift register. **6M**
- b Design a decade counter and explain its operation with necessary waveforms. **6M**

*** END ***