

Reg. No:

--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations October-2020

ELECTRICAL CIRCUITS

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

- 1 a State Kirchoff's Laws and explain in detail. **4M**
 b Find the current through each branch by network reduction technique from the network shown in Fig. (1) **8M**

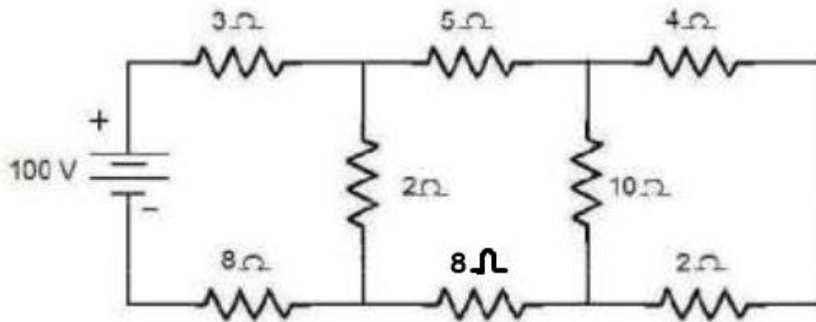


Fig.(1)

OR

- 2 a What are the types of sources? Explain them with suitable diagrams and Characteristics? **6M**
 b Derive an expression for total resistance when three resistances R1, R2 & R3 are connected in Parallel. **6M**

UNIT-II

- 3 Define Average value and RMS value? Find the average value and RMS value of a full wave rectified sine wave. **12M**

OR

- 4 A 1KΩ resistor is connected in series with an inductance of 50mH across a 230V, 50HZ AC Supply. Find (i) Inductive reactance (ii) Impedance (iii) Current (iv) Phase angle (v) Voltage drop across resistance (vi) Voltage drop across Inductance. **12M**

UNIT-III

- 5 A series RLC circuit has R=10Ω, L=0.5H and C=40μF. The applied voltage is 100V. Find (a) Resonant frequency & Quality factor of a coil (b) Bandwidth (c) Upper and lower Half power frequencies (d) Current at resonance & current at half power points (e) Voltage across inductance & voltage across capacitance at resonance. **12M**

OR

- 6 a Define the following terms: (i) impedance (ii) admittance **4M**
 b Draw the Locus diagram of a Series RL Circuit? **8M**

UNIT-IV

- 7 a Derive the expression for equivalent inductance when the coupled inductors are connected in Series aiding and series opposition? **8M**
 b Two coupled coils have a self inductances 37.5 mH and 193 mH, with the mutual inductance of 63.75 mH. Find the co efficient of coupling. **4M**

OR

- 8 Explain in detail about Statically Induced EMF and Dynamically Induced EMF? **12M**

UNIT-V

- 9 a Write the Statement of Superposition Theorem? **2M**
 b Find the current passing through Each Resistor for the circuit shown below in Fig.(a) by using Superposition Theorem? **10M**


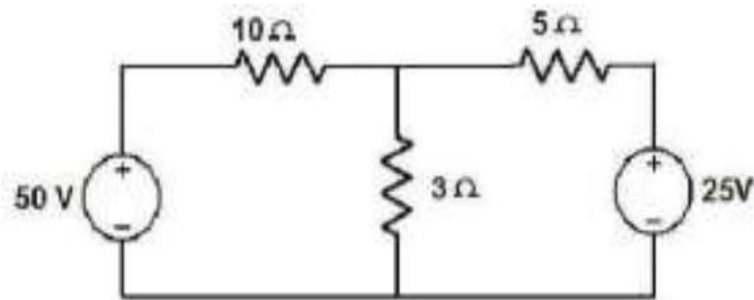


Fig.(a)

OR

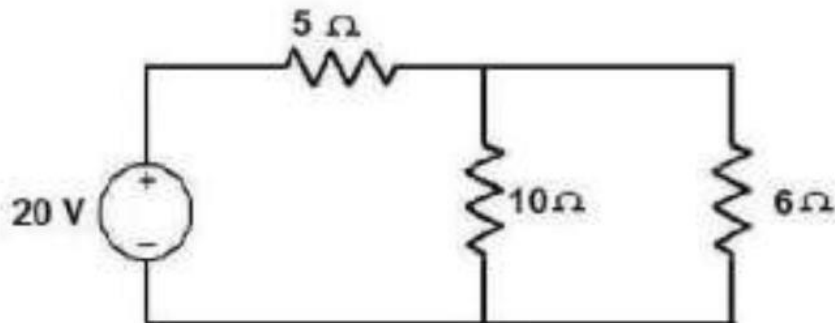- 10 a State and prove Norton's Theorem? **6M**
 b Using Norton's Theorem, Find current through 6Ω resistance shown in below Fig. **6M**



*** END ***