

Reg. No:

--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations November-2020

NETWORK ANALYSIS & SYNTHESIS

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

- 1 An unbalanced 4 wire star connected load has a balanced voltage of 400V. The load are $Z_1 = (4+j8) \Omega$, $Z_2 = (5+j4)\Omega$, $Z_3 = (15+j20)\Omega$. Calculate line currents, current in neutral wire, total power. **12M**

OR

- 2 A balanced delta connected load of $(4+j3) \Omega$ per phase is connected to a balanced 3ϕ , 440V supply. Find i) active power ii) reactive power iii) Apparent power. **12M**

UNIT-II


- 3 A series RL circuit with $R=30\Omega$ and $L=15H$ has a constant voltage $V=60V$ applied at $t=0$. Determine the current I, the voltage across the resistor and across the inductor. **12M**

OR

- 4 Derive the transient response of a RC circuit with AC excitation. **12M**


UNIT-III

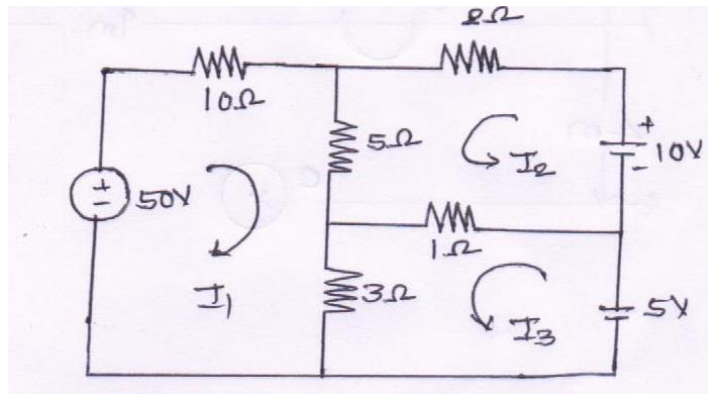- 5 Determine mesh currents for the following network using network topology. **12M**



OR

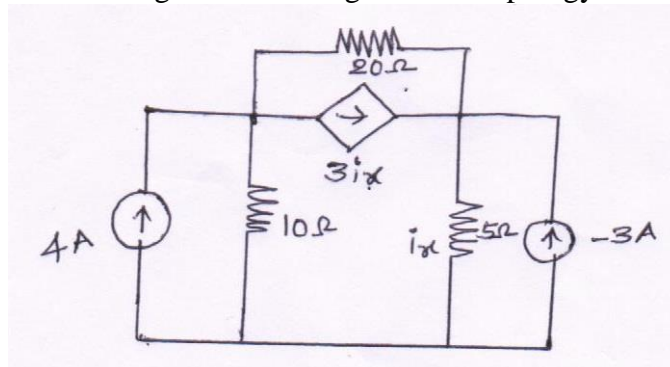- 6 Determine i_x for the following network using network topology. **12M**



UNIT-IV

- 7 Prove the g parameters can be obtained from the z parameters as 12M

$$g_{11} = \frac{1}{z_{11}} \quad g_{12} = \frac{-z_{12}}{z_{11}} \quad g_{21} = \frac{z_{21}}{z_{11}} \quad g_{22} = \frac{\Delta_z}{z_{11}}$$

OR

- 8 Derive the expressions for Y-parameters in terms of ABCD parameters. 12M

UNIT-V

- 9 Explain about constant K low pass filter. 12M

OR

- 10 Design a low pass filter having cut of frequency of 5KHz with load resistance of 800 ohms. 12M

*** END ***