

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B Tech I Year II Semester Supplementary Examinations October-2020**

**NETWORK ANALYSIS**

(Electronics & Communication Engineering)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

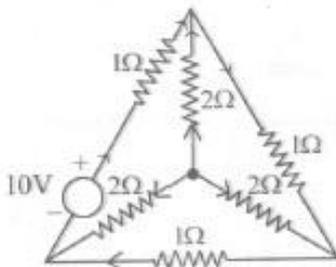
**UNIT-I**

- 1 a Define and state the properties of incidence matrix. 4M  
 b For the network shown below draw the graph and find incidence and tie – set matrices. 8M



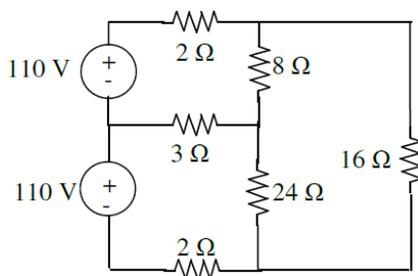**OR**

- 2 a State and explain Kirchoff's laws? 4M  
 b Using nodal analysis find all branch currents for the following circuit. 8M



**UNIT-II**


- 3 a Define power factor, apparent power, active power and reactive power. 4M  
 b A resistor of  $50\Omega$ , inductance of  $100\text{mH}$  and a capacitance of  $100\mu\text{F}$  are connected in series across  $200\text{V}$ ,  $50\text{Hz}$  supply. Determine the following  
 (i) Impedance (ii) current flowing through the circuit (iii) power factor (iv) voltage across R,L & C (v) power in watts. 8M

**OR**

- 4 a Mention the properties of Exponential Response of RLC circuits. 4M  
 b The impedances of parallel circuit are  $Z_1 = (6+j8)$  ohms and  $Z_2 = (8-j6)$  ohms. If the applied voltage is  $120\text{V}$ , find (i) current and power factor of each branch (ii) overall current (iii) power consumed by each impedance. Draw the phasor diagram. 8M

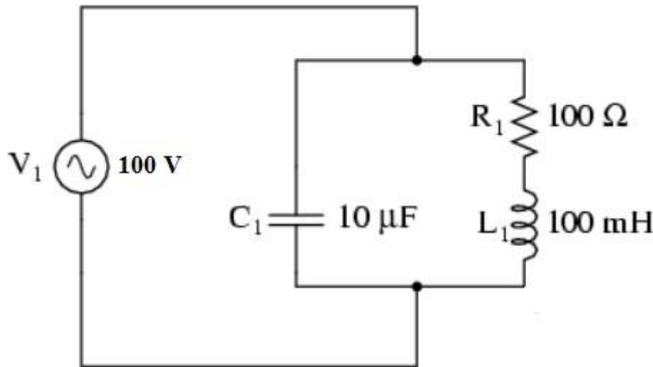**UNIT-III**

- 5 a Write the comparison between series resonance and parallel resonance? **4M**  
 b In a parallel Resonant circuit shown in figure. (1), find the Resonant frequency, **8M**  
 Dynamic Impedance, Bandwidth, Q-factor and Current at resonance?




**OR**

- 6 a Define coupling co-efficient and derive the relation between self-inductance, mutual inductance and coupling co-efficient. **5M**  
 b **7M**  
 A series RLC circuit has  $R=10\Omega$ ,  $L=0.5H$  and  $C=40\mu F$ . The applied voltage is  $100V$ . Find (i) Resonant frequency & Quality factor of a coil (ii) Bandwidth (iii) Upper and lower Half power frequencies (iv) Current at resonance & current at half power points (v) Voltage across inductance & voltage across capacitance at resonance.

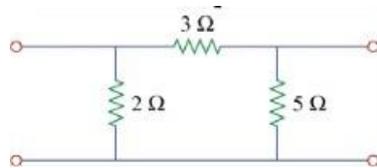**UNIT-IV**

- 7 a Mention the condition for symmetry and reciprocity for h-parameters **4M**  
 b Find the Z- parameters for the following circuit. **8M**



**OR**

- 8 a What are the advantages of state variable analysis? **5M**  
 b The transfer function of a system is  $G(s)=2/(s+1)(s+2)$ . Obtain a state variable **7M**  
 representation for the system.

**UNIT-V**

- 9 a What is a constant K low pass filter, derive its characteristics impedance. **4M**  
 b Design a band elimination filter and explain its design procedure in detail. **8M**

**OR**

- 10 a Explain Neper and Decibel. **4M**  
 b Design a constant K high pass filter and explain its design procedure in detail. **8M**

\*\*\* END \*\*\*