

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)  
B.Tech II Year II Semester Supplementary Examinations October-2020  
BASIC ELECTRICAL & ELECTRONICS ENGINEERING  
(Mechanical Engineering)**

Time: 3 hours


Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

**PART-A**

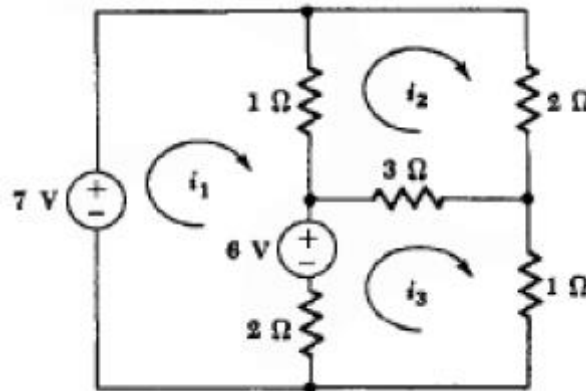
**UNIT-I**

- 1 a State and prove Kirchhoff law's with an example. 5M  
 b In the circuit shown below find  $i_1, i_2, i_3$  by using Kirchhoff's laws? 5M




OR

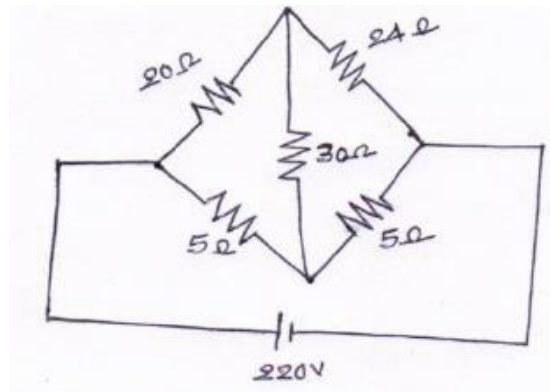- 2 Find the current delivered by the source for the circuit shown in figure. 10M



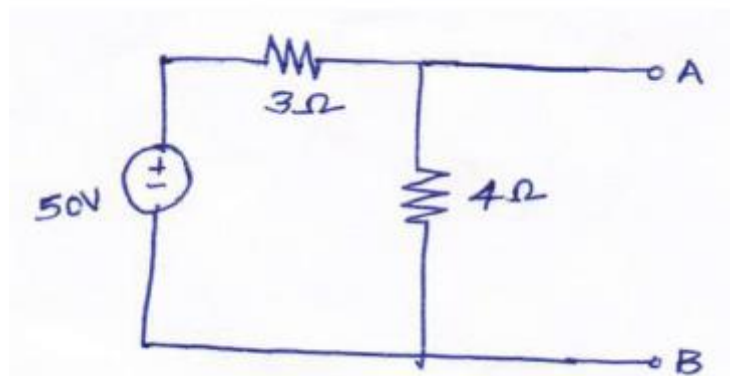
**UNIT-II**

- 3 a State Norton's theorem 4M  
 b Find Norton's equivalent circuit across AB for the circuit shown in below. 6M



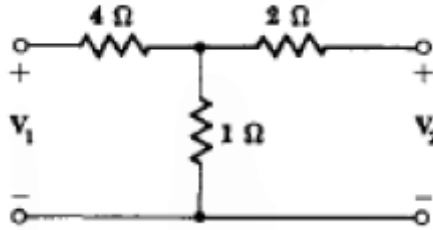**OR**

- 4 Find the Short circuit parameters for the circuit shown in figure. 10M



**UNIT-III**

- 5 a Derive Torque equation of dc motor 5M  
 b The counter EMF of shunt motor is 227 Volts. The field resistance is  $160\Omega$ , field current is 1.5A and the line current is 36.5A. Find the armature resistance also find armature current when the motor is stationary. 5M

**OR**

- 6 a Explain OC and SC test of a single-phase transformer. 5M  
 b A Single phase 2200/250V, 50Hz transformer has a net core area of  $36\text{cm}^2$  and a maximum flux density of  $6\text{wb/m}^2$ . Calculate the number of turns of primary and secondary. 5M

**PART-B**

**UNIT-IV**

- 7 Describe the working of a PN junction diode when it is connected in forward bias and reverse bias. Draw VI Characteristics of PN Junction Diode. 10M

**OR**

- 8 a Draw the circuit diagram of a Bridge Rectifier and explain its operation with input and output waveforms. 5M  
 b Discuss the operation of half wave rectifier with capacitor filter. 5M

**UNIT-V**

- 9 a Discuss with neat diagrams, the Common Emitter Configuration and its characteristics. 5M  
 b Compare the characteristics of BJT CB, CE and CC transistor configurations. 5M

**OR**

- 10 a Explain with diagrams, the construction, working and characteristics of N-channel Depletion MOSFET. 5M  
 b For a voltage divider biasing using BJT,  $R_C = 1\text{k}\Omega$ ,  $R_E = 2\text{k}\Omega$ ,  $R_1 = 10\text{k}\Omega$ ,  $R_2 = 5\text{k}\Omega$ , and  $V_{CE} = 10\text{V}$ . Find the coordinates of the extremities of the load line and the Q-point. Assume Silicon Transistor. 5M

**UNIT-VI**

- 11 a What is an oscillator and how the oscillators are classified? Write Barkhausen criteria for Oscillator. 5M  
 b Mention the types of RC oscillators. Explain RC phase shift oscillator with diagram. 5M

**OR**

- 12 a Discuss the Characteristics of an ideal operational amplifier. 5M  
 b Describe Integrator amplifier of op amp with diagram. 5M

\*\*\* END \*\*\*