

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Supplementary Examinations November-2020

POWER ELECTRONICS

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

1 a Describe input and transfer characteristics of an IGBT. **8M**

b Define Latching current and Holding current. **4M**

OR

2 a Explain the switching characteristics of BJT. **6M**

b Write short note on Turn on methods of SCR. **6M**

UNIT-II

3 Explain the operation of single phase fully controlled rectifier with RL load and also derive the average and RMS load voltage. **12M**

OR

4 a A single phase full converter feeds power to RLE load with $R=60\Omega$, $L=6\text{mH}$ and $E=60\text{V}$. The ac source voltage is 230V, 50Hz. For continuous conduction, find the average value of load current for a firing delay of 50° . In case one of the four SCRs gets open circuit due to a fault, find the new value of average load current taking the output current as continuous. **6M**

b List the different application of phase controlled converters. **6M**

UNIT-III

5 Explain the effect of source inductance in the operation of three phases fully controlled converter. **12M**

OR

6 a Give the difference between discontinuous mode and continuous mode of operation. **6M**

b Give the difference between midpoint and bridge type converters. **6M**

UNIT-IV

7 Explain the principle of operation of single phase to single phase step-up cycloconverter. **12M**

OR

8 A single phase half wave ac voltage controller feeds a load of $R=20\Omega$ with an input voltage of 230v, 50Hz. Firing angle of thyristor is 45° . Determine **12M**

i) rms value of output voltage

ii) power delivered to load and input pf

iii) Average input current.

UNIT-V

9 Draw and explain about step-down chopper and derive expression for output voltage. **12M**

OR

10 Describe different types of pulse width modulation techniques (PWM) inverter. **12M**

*** END ***