

**Reg. No:**

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B Tech I Year II Semester Regular Examinations October-2020**

**Electrical Circuits - I**

(Electrical & Electronics Engineering)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

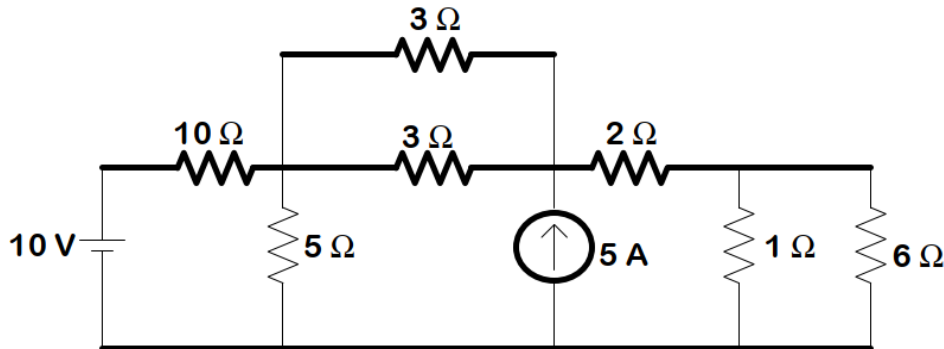
**UNIT-I**

- 1 a** Derive the equivalent resistances when two resistances are connected in series. **3M**  
**b** Determine the voltages at each node for the circuit shown in Figure. **9M**



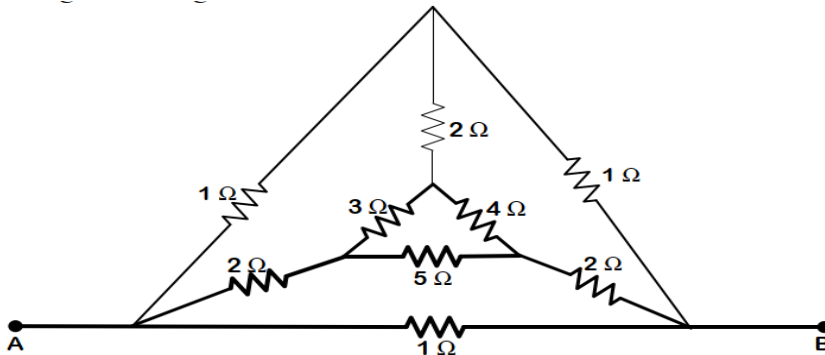**OR**

- 2 a** Find the equivalent resistance across the terminals A and B of the network shown in Figure. using Star-delta transformation **9M**



- b** Write a formula for Star to Delta transformation with necessary diagram **3M**

**UNIT-II**

- 3 a** Define Relative permeability and coupling coefficient **3M**  
**b** Explain Self Inductance, Mutual Inductance and Co-efficient of coupling in detail. **9M**  
 Give the relation between  $L_1$ ,  $L_2$ ,  $k$  and  $M$ .

**OR**


- 4 a** When two identical coupled coils are connected in series, the inductance of the combination is found to be 80 mH. When the connections to one of the coils are reversed, a similar measurement indicates 20 mH. Find the coupling coefficient between the coils.. **9M**  
**b** State the transformer working principle. **3M**

**UNIT-III**

- 5 a A Capacitor of  $1\mu\text{F}$  is connected across an AC Voltage of  $V=170 \sin (400t)$ . 8M  
 Determine,  
 (i) Capacitive Reactance  
 (ii) Sinusoidal expression for current  
 (iii) Maximum current.  
 b Define Root Mean Square value. 4M

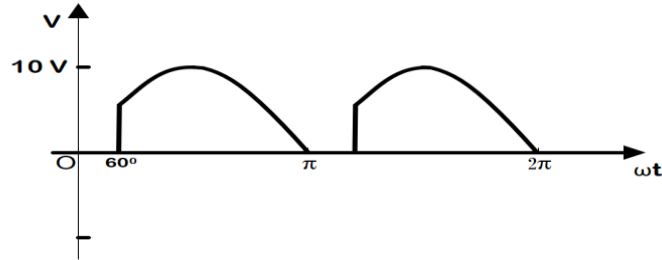
**OR**

- 6 a Draw phasor diagram for simple RC series circuit. 4M  
 b The full wave rectified sine wave shown in Figure has a delay angle of  $60^\circ$ . 8M  
 Calculate the average value and RMS value.



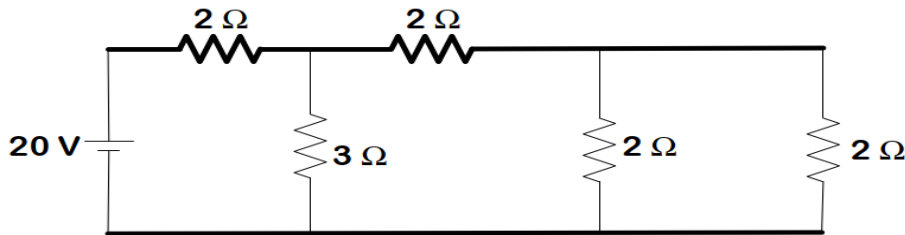**UNIT-IV**


- 7 a Verify Reciprocity Theorem for the network shown in Figure. 9M



- b State Milliman's Theorem. 3M

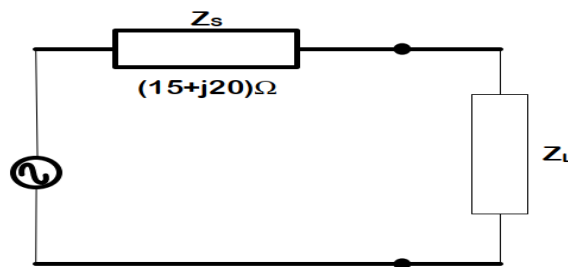**OR**

- 8 a State Tellegen's theorem. 3M  
 b For the circuit shown in Figure, find the value of load impedance for which the source delivers maximum power. Also calculate the value of maximum power. 9M



**UNIT-V**

- 9 a Obtain the expression for resonant frequency for parallel RL-RC circuit. 6M  
 b In a parallel resonance circuit (Tank circuit)  $R=2\Omega$ ,  $L=1\text{mH}$  and  $C=10\mu$ . Find the Resonant frequency, Dynamic impedance and Bandwidth. 6M

**OR**

- 10 a Derive and draw the Locus diagram of a Series RC Circuit. 9M  
 b Define Bandwidth and quality factor. 3M

\*\*\* END \*\*\*