

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Regular Examinations November-2021

ELECTRONIC DEVICES AND CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Define cutin voltage of a PN Junction diode and give its values for Si and Ge diodes. L1 4M
b When a reverse bias is applied to a germanium PN junction diode, the reverse saturation current at room temperature is $0.3\mu\text{A}$. Determine the current flowing in the diode when 0.15V forward bias is applied at room temperature. L5 4M
c Mention the importance of Diode Clipper and list its applications. L2 4M

OR

- 2 a Analyze the current components in a PN diode and determine the expression for diode current equation. L4 6M
b Draw and explain the V-I characteristics of Zener diode. Show that the Zener diode can act as a voltage regulator with a neat diagram. L1 6M

UNIT-II

- 3 a Draw the circuit diagram of a Half wave rectifier and explain its operation with the help of waveforms. L1 6M
b Determine the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output and AC Power input of a Full Wave Rectifier. L5 6M

OR

- 4 a A $5\text{K}\Omega$ load is fed from a bridge rectifier connected across a transformer secondary whose primary is connected to 460V, 50 Hz supply. The ratio of number of primary turns to secondary turns is 2:1. Estimate dc load current, ripple voltage and PIV rating of diode. L5 4M
b Demonstrate the working principle of LC filter with neat diagram and derive the expression for its ripple factor. L2 8M

UNIT-III

- 5 a Explain the current components of PNP transistor, the Emitter Efficiency, Base Transportation Factor and Large signal current gain. L2 6M
b Evaluate the relation between α , β and γ of a Transistor. L5 6M

OR

- 6 a With the help of neat diagram, explain the operation and characteristics of n-channel Enhancement type MOSFET. L2 6M
b Compare the performance of BJT with FET. L2 6M

UNIT-IV

- 7 a Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point. **L2 6M**
- b Design the circuit ,for given Q-point values are to be $I_{CQ}=1\text{mA}$ and $V_{CEQ}=6\text{V}$.Assume that $V_{CC}=10\text{V}$, $\beta=100$ and $V_{BE}(\text{on})=0.7\text{V}$ **L4 6M**

OR

- 8 a List the different types of Biasing a Transistor and explain the Fixed Bias of a Transistor. **L4 6M**
- b Design a collector to base bias circuit for the specified conditions: $V_{cc} = 15\text{V}$, $V_{CE} = 5\text{V}$, $I_C = 5\text{mA}$ and $\beta = 100$. **L6 6M**

UNIT-V

- 9 a Why hybrid model is used for the analysis of BJT amplifier at low frequencies? Draw the hybrid model for CE transistor and derive the hybrid parameters. **L3 6M**
- b For a CB transistor amplifier driven by a voltage source of internal resistance $R_s = 1200\Omega$, the load Impedance of $R_L = 1000\Omega$. The h parameters are $h_{ib} = 22\Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$, $h_{ob} = 0.5\mu\text{A/V}$. Find current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. **L5 6M**

OR

- 10 a Using low frequency h-parameter model, Evaluate the expressions for voltage gain, current gain, input impedance and output admittance for a BJT Amplifier in CE configuration. **L5 6M**
- b A CE amplifier is driven by a voltage source of internal resistance $R_s = 1000\Omega$ and the load impedance of $R_C = 2\text{k}\Omega$. The h-parameters are $h_{ie} = 1.3\text{k}$, $h_{fe} = 55$, $h_{oe} = 22\mu\text{A/V}$ and $h_{re} = 2 \times 10^{-4}$. Neglecting biasing resistors, Estimate the value of current gain, voltage gain, input impedance, output impedance for the value of Emitter Resistor $R_E = 200\Omega$ inserted in the emitter circuit. **L5 6M**

*** END ***