

Reg. No:

| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|
| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Regular & Supplementary Examinations October-2022

DIGITAL LOGIC DESIGN

(Common to CSM, CAD & CIC)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Convert the following numbers L1 6M
 i) $(31.6876)_{10}$ to Hexadecimal number
 ii) $(10101101.1001)_2$ to base-8 and base-4
 iii) $(3564)_{10}$ to base2
 b Subtract $(111001)_2$ from $(101011)_2$ using 1's complement. L2 6M

OR

- 2 a Convert the following numbers L5 6M
 i) $(CD)_{16} = ()_2$
 ii) $(1546)_8 = ()_{16}$
 iii) $(101101.10)_2 = ()_8$
 b Perform the following Using BCD arithmetic $(7129)_{10} + (7711)_{10}$ L5 6M

UNIT-II

- 3 a Design the circuit by Using NOR gates $F = (X+Y) \cdot (X'+Y'+Z')$ L5 6M
 b Simplify the Boolean expression using K-MAP $F(A,B,C,D) = \sum m(1,2,3,8,9,10,11,14) + d(7,15)$ L5 6M

OR

- 4 a Explain NAND- NOR implementations. L2 6M
 b Simplify the Boolean expression using K-map L2 6M
 $F(A,B,C,D,E) = \sum m(0,1,4,5,16,17,21,25,29)$

UNIT-III

- 5 a Explain Carry Look ahead Generator. L2 6M
 b Implement the following Boolean function using 8:1 multiplexer L5 6M
 $F(A, B, C, D) = A'BD' + ACD + A'C'D + B'CD$

OR

- 6 a Design the combinational circuit binary to gray code. L2 6M
 b Explain about Binary Half Adder. L2 6M

UNIT-IV

- 7 a Explain the Logic diagram of JK flip-flop. L2 6M
 b Design and draw the 3 bit up-down synchronous counter. L5 6M

OR

- 8 a Explain about Shift Registers. L2 6M
 b Draw and explain the operation of D Flip-Flop. L5 6M

UNIT-V

- 9 a Explain about Error correction & Detection Codes. L2 6M
 b Explain about the construction of 4 X 4 RAM. L2 6M

OR

- 10 a Explain about Hamming Code with example. L2 6M
 b Explain different types of ROM. L2 6M

*** END ***