

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR

(AUTONOMOUS)

B.Tech II Year II Semester Regular Examinations October-2022

DIGITAL ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Subtraction by using 1's complement for the given 10101 - 11011.
L3 6M
- b Subtraction by using 2's complement for the given 111001-1010.
L3 6M

OR

- 2 What is Grey code? What are the rules to construct gray code? Develop the 4 bit gray code for The decimal 0 to 15.
L1 12M

UNIT-II

- 3 Minimize the following Boolean function using K-Map
L2 12M
- $$F(A, B, C, D) = \sum m(0, 2, 4, 6, 8, 10, 12, 14).$$

OR

- 4 Simplify the following Boolean expressions using K-map.
L3 12M
- $$F(A, B, C, D, E) = \sum m(0, 5, 6, 8, 9, 10, 11, 16, 20, 24, 25, 26, 27, 29, 31)$$

UNIT-III

- 5 What is Demultiplexer? Design 1:4 Demultiplexer using 1:4 Demultiplexers.
L1 12M

OR

- 6 Design & implement Half Adder and Full Adder with truth table.
L3 12M

UNIT-IV

- 7 a Write the differences between combinational and sequential circuits.
L2 6M
- b Explain working of Master Slave Flip flop with neat diagram.
L1 6M

OR

- 8 Draw the circuit of JK flip flop using NAND gates and explain its operation.
L3 12M

UNIT-V

- 9 Explain about Mealy and Moore Models of sequential machines.
L3 12M

OR

- 10 What is design procedure for FSM? Give the advantages of FSM.
L3 12M

*** END ***