



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code : Network Analysis(16EE205)

Course & Branch: B.Tech - ECE


Year & Sem: I-B.Tech & II-Sem

Regulation: R16

UNIT –I


INTRODUCTION

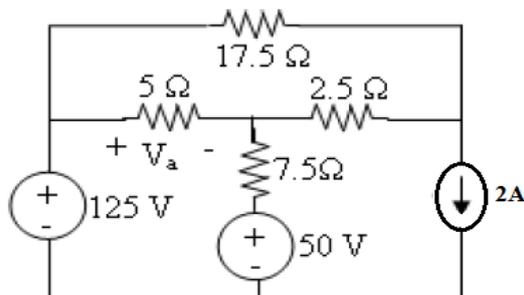1. a) What do you mean by an electric network and an electric circuit? [L1] [4M]
b) Find the value of V_a for the following circuit using KVL. [L3] [6M]




2. a) Explain the concept of source transformation? [L3] [4M]

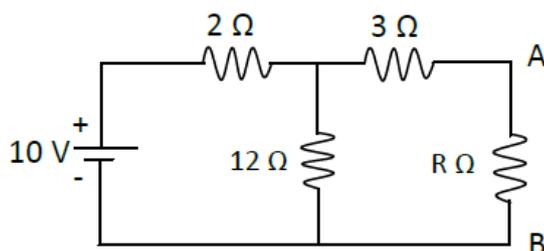
b) Find the maximum power delivered to the load by using maximum power transfer theorem for the following circuit. [L3] [6M]



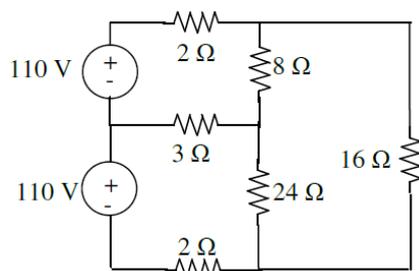
3. (a) State and explain Kirchoff's laws? [L3] [4M]
(b) Using nodal analysis find all branch currents for the following circuit [L3] [6M]



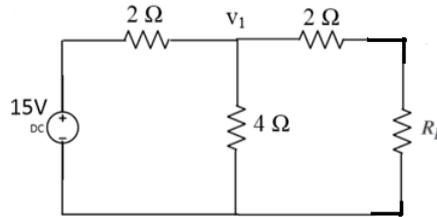
4. a) What is the condition for maximum power transfer to the load? [L3] [4M]
 b) Find Thevenin's equivalent for the following circuit. [L3] [6M]



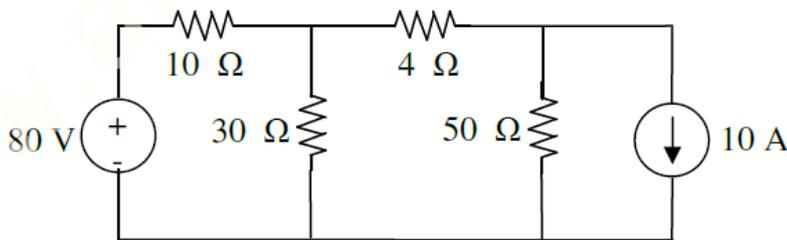
5. a) State and explain Superposition theorem? [L3] [4M]
 b) Verify Superposition theorem for 4Ω resistor for the following circuit. [L3] [6M]



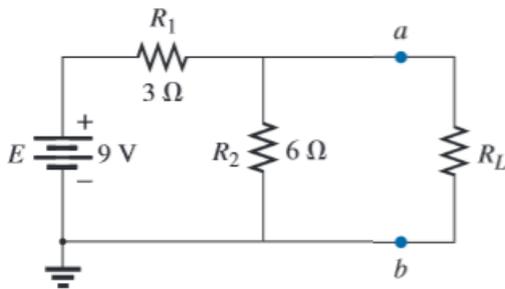
6. a) State and explain milliman's theorem. [L3] [4M]
 b) Find Norton's equivalent for the following circuit. [L3] [6M]



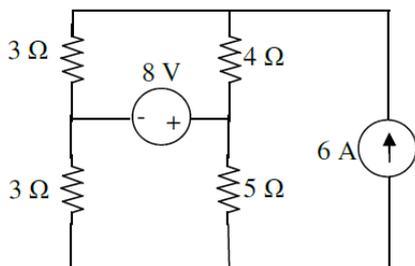7. (a) State Kirchoff's voltage law? [L3] [4M]
 (b) Find branch currents for the following circuit. [L3] [6M]



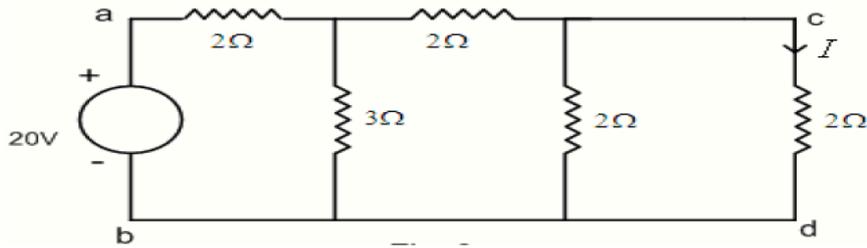8. a) State and explain Norton's theorem? [L3] [4M]
 b) Verify the reciprocity theorem for the network shown in fig. [L3] [6M]




9. (a) Define the following terms

- (i) Branch (ii) Sub graph (iii) Node (iii) Tree

[L3] [4M]

(b) For the graph shown below find incidence and cut set matrices.

[L3] [6M]

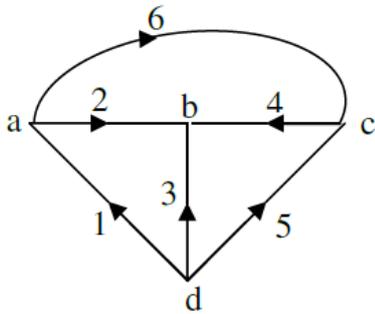


10. (a) Define and state the properties of incidence matrix.

[L2] [4M]

(b) For the network shown below draw the graph and find incidence and tie – set matrices.

[L3] [6M]

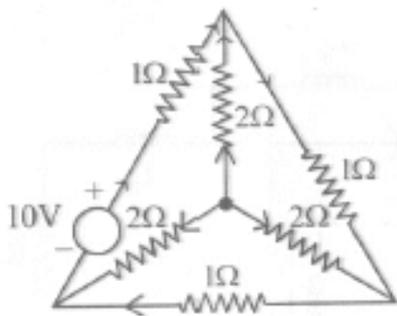



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code : Electrical Circuits(16EE201)

Course & Branch: B.Tech - EEE

Year & Sem: I-B.Tech & II-Sem

Regulation: R16

UNIT-II

AC CIRCUITS

1. a) What is time constant? What are the time constants of series RL and RC circuits? [L3] [4M]
 b) Deduce the transient response source free series RC circuit. [L3] [6M]
2. (a) Explain about properties of Exponential Response of RLC circuits. [L3] [4M]
 (b) Deduce the transient response source free series RL circuit [L3] [6M]
- 3.(a) Explain about Source free RL and RC Circuits. [L3] [4M]
 (b) Explain the complete response of source free series RLC Circuits. [L3] [6M]
4. (a) Explain about Natural & Forced Response of RLC Circuits. [L3] [4M]
 (b) Explain the complete response of source free parallel RLC Circuits. [L3] [6M]
- 4.a) Define Admittance [L3] [2M]
 b) The impedances of parallel circuit are $Z_1 = (6+j8)$ ohms and $Z_2 = (8-j6)$ ohms. If the applied voltage is 120V, find (i) current and power factor of each branch (ii) overall current (iii) power consumed by each impedance. Draw the phasor diagram. [L3] [8M]
- 5.(a) Explain the phasor relation for R,L,C elements. [L3] [4M]
 (b) A resistor of 50Ω , inductance of 100mH and a capacitance of $100\mu\text{F}$ are connected in series across 200V, 50Hz supply. Determine the following [L3] [6M]
 (i) Impedance (ii) current flowing through the circuit (iii) power factor
 (iv) voltage across R,L &C (v) power in watts
6. (a) Explain the phasor relation for series RL and RC circuit. [L3] [4M]
 (b) A 120V AC circuit contain 10Ω resistance and 30Ω inductive reactance in series. What is average power of this circuit. [L3] [6M]
7. (a) Explain the phasor relation for parallel RLC circuit. [L2] [4M]
 (b) A parallel RLC circuit is supplied with a voltage source of 230 V, 50Hz. Determine circuit current and power factor if $R=40\Omega$, $L=0.2\text{H}$ and $C=50\mu\text{F}$. [L3] [6M]
8. (a) Define power factor, apparent power, active power and reactive power. [L3] [4M]
 (b) The impedances of parallel circuit are $Z_1 = (4+j6)$ ohms and $Z_2 = (12-j8)$ ohms. If the applied voltage is 220V, find (i) current and power factor of each branch (ii) overall current (iii) power consumed by each impedance. Draw the phasor diagram. [L3] [6M]
9. (a) Explain the phasor relation for parallel RL and RC elements. [L3] [4M]

- (b) A 120V AC circuit contain 10 Ω resistance and 30 Ω inductive reactance in series. What is average power of this circuit. [L3] [6M]
10. (a) Explain the characteristics of sinusoids. [L3] [4M]
- (b) A resistor of 150 Ω , inductance of 200mH and a capacitance of 10 μ F are connected in series across 500V, 150Hz supply. Determine the following [L3] [6M]
- (i) Impedance (ii) current flowing through the circuit (iii) power factor
(iv) voltage across R,L &C (v) power in watts



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code : Electrical Circuits(16EE201)

Course & Branch: B.Tech - EEE

Year & Sem: I-B.Tech & II-Sem

Regulation: R16

UNIT-III

RESONANCE & MAGNETICALLY COUPLED CIRCUITS

- A series RLC circuit has $R=10\Omega$, $L=0.5H$ and $C=40\mu F$. The applied voltage is 100V. Find (a) Resonant frequency & Quality factor of a coil (b) Bandwidth (c) Upper and lower Half power frequencies (d) Current at resonance & current at half power points (e) Voltage across inductance & voltage across capacitance at resonance. [L3] [10M]
- (a) In a parallel resonance circuit (Tank circuit) $R=2\Omega$, $L=1mH$ and $C=10\mu F$, Find the Resonant frequency, Dynamic impedance and Bandwidth. [L3] [6M]
(b) Obtain the expression for resonant frequency for parallel RL-RC circuit. [L3] [4M]
- Obtain the expression for resonant frequency, bandwidth and Q-factor for parallel R-L-C circuit. [L3] [10M]
- Obtain the expression for resonant frequency, bandwidth and Q-factor for Series R-L-C circuit. [L3] [10M]
- Show that the resonant frequency circuit $f_r^2 = f_1 f_2$ where f_1 and f_2 are the half power frequencies and f_r is the resonant frequency. [L3] [10M]
- Write the comparison between series resonance and parallel resonance? [L2] [10M]
- Define and explain self and mutual inductance. [L3] [10M]
- a) Explain about dot convention in mutually coupled circuits. [L1] [4M]
b) Discuss briefly about energy considerations in mutually coupled circuits. [L3] [6M]
- Explain about linear transformer and ideal transformer. [L2] [10M]
- In a parallel Resonant circuit shown in figure. (1), find the Resonant frequency, Dynamic Impedance, Bandwidth, Q-factor and Current at resonance? [L3] [10M]

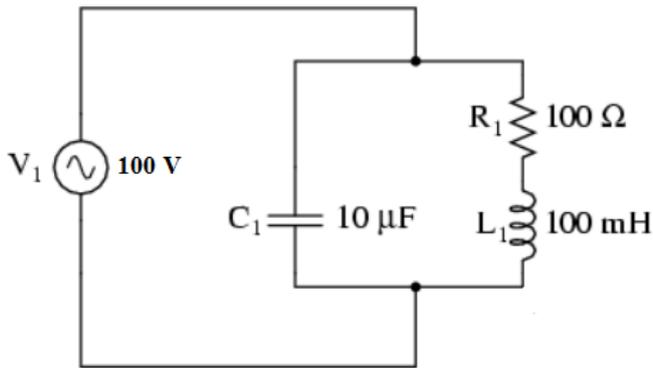


Fig.(1)



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code : Electrical Circuits(16EE201)

Course & Branch: B.Tech - EEE


Year & Sem: I-B.Tech & II-Sem

Regulation: R16


UNIT-IV

TWO PORT NETWORKS & STATE VARIABLE ANALYSIS

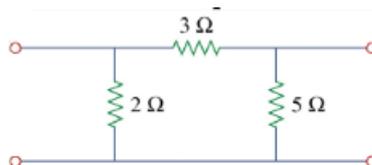
1. a) Find the Z- parameters for the following circuit. [L3] [6M]



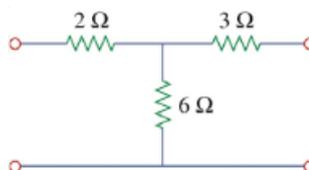- b) Express ABCD parameters in terms of h parameters. [L3] [4M]
2. a) Find the Y- parameters for the following circuit. [L3] [6M]




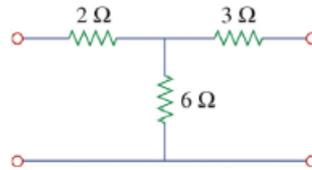- b) Express h parameters in terms of ABCD parameters. [L3] [4M]
3. a) Find the ABCD parameters for the following circuit. [L3] [6M]




b) Express Y parameters in terms of h parameters. [L3] [4M]

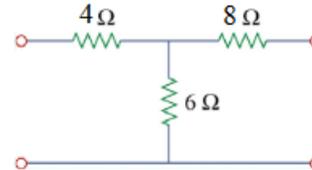4. a) Find the h- parameters for the following circuit. [L3] [6M]




b) Find the relationship between Z and h parameters. [L3] [4M]

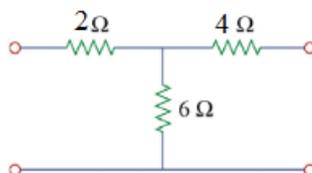5. Find the Z and Y parameters for the following circuit. [L3] [10M]




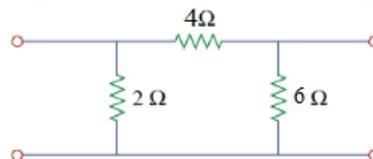6. a) Find the Y- parameters for the following circuit. [L3] [6M]



b) Express Z parameters in terms of ABCD parameters. [L3] [4M]

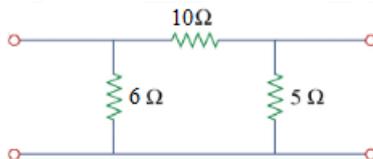7. Find the ABCD and h - parameters for the following circuit. [L3] [10M]



8. Explain about the state variables and state variables of circuits. [L3] [10M]

9. a) What are the advantages of state variable analysis. [L3] [4M]

b) The transfer function of a system is $G(s)=2/(s+1)(s+2)$. Obtain a state variable representation for the system. [L3] [6M]

10. Explain about proper and improper behavior of the circuits. [L3] [10M]



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code : Electrical Circuits(16EE201)

Course & Branch: B.Tech - EEE

Year & Sem: I-B.Tech & II-Sem

Regulation: R16

**UNIT-V
FILTERS**

1. a) Explain Neper and Decibel. [L2] [4M]
b) What is a constant K low pass filter, derive its characteristics impedance. [L2] [6M]
2. a) What is a filter? Explain about various types of filters. [L2] [4M]
b) Explain the classification of pass band and stop band in detail. [L2] [6M]
3. Derive the expression for characteristic impedance in a pass band filter. [L2] [10M]
4. Explain the design procedure for a constant K low pass filter and its characteristics. [L2] [10M]
5. Design a constant K high pass filter and explain its design procedure in detail. [L2] [10M]
6. What is high pass filter. Explain the general configuration and parameters of a constant-K high pass filter. [L2] [10M]
7. What is an m-derived filter? Explain the general configuration and parameters of m-derived low pass filter. [L2] [10M]
8. Derive necessary expressions for m-derived high pass filter. [L2] [10M]
9. Give the analysis for the design of constant-K band pass filter. [L2] [10M]
10. Design a band elimination filter and explain its design procedure in detail. [L2] [10M]

Prepared by:

**C.R.HEMAVATHI
ASSISTANT PROFESSOR
DEPT. OF EEE
SIETK**