



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code: Basic Electronics Engineering
(20EC0445)

Year & Sem: I-B.Tech & I-Sem

Course & Branch: B.Tech – CSE,
CSIT, CSM & CIC

Regulation: R20

UNIT –I

Basics of Semiconductor

1	a	Distinguish among conductors, semiconductors and insulators.	[L4][CO1] [8M]
	b	What is meant by Doping in a semiconductor? And list the different types of acceptor and donor impurities.	[L1][CO1] [4M]
2	a	Explain the differences between intrinsic and extrinsic semiconductors.	[L2][CO1] [8M]
	b	Define the terms Drift and Diffusion current.	[L1][CO1] [4M]
3	a	With the help of Energy band diagram define the following terms: i) valence band, ii) conduction band, and iii) band gap	[L1][CO1] [8M]
	b	Compare and contrast the semiconductors Silicon and Germanium.	[L4][CO1] [4M]
4		With the help of Energy band diagrams explain Conductors, Semiconductors & Insulators.	[L2][CO1] [12M]
5	a	Explain the differences between P-type and N-type semiconductors.	[L2][CO1] [6M]
	b	State and explain the term Conductivity in conductors and in semiconductors.	[L2][CO1] [6M]
6		Describe the operation of Intrinsic semiconductor at T=0 Kelvin and T=300 Kelvin.	[L2][CO1] [12M]
7	a	What is meant by Acceptor energy level?	[L2][CO1] [3M]
	b	State and Explain the law of electrical neutrality in semiconductor.	[L2][CO1] [9M]
8		Describe the operation of P-type semiconductor at T=0 Kelvin and T=300 Kelvin.	[L2][CO1] [12M]
9	a	What is meant by Donor energy level?	[L2][CO1] [3M]
	b	Explain in detail about mass action law.	[L2][CO1] [9M]
10		Describe the operation of N-type semiconductor at T=0 Kelvin and T=300 Kelvin.	[L2][CO1] [12M]

UNIT –II
PN JUNCTION DIODE

1	a	Explain how a barrier potential is developed at the PN junction.	[L2][CO1] [10M]
	b	Mention the applications of PN diode.	[L1][CO1] [2M]
2		With the help of V-I Characteristics explain the action of PN junction diode under forward and reverse bias condition.	[L2][CO1] [12M]
3	a	Distinguish between Avalanche and Zener breakdown.	[L2][CO1] [6M]
	b	Plot the graph for different breakdown mechanisms in semiconductors.	[L2][CO1] [6M]
4		Explain the terms i) Transition capacitance C_T of a PN diode. ii) Diffusion capacitance C_D of a PN diode	[L3][CO1] [12M]
5	a	Explain Quantitative Theory of PN Diode Currents.	[L2][CO1] [8M]
	b	A p-n junction germanium diode has a reverse saturation current of $0.10 \mu\text{A}$ at the room temperature of 27°C . It is observed to be $30\mu\text{A}$, when the room temperature is increased. Calculate the new room temperature. Also determine the current passing through the diode at this new temperature.	[L3][CO1] [4M]
6	a	Draw the V-I characteristics of Zener diode and explain its operation.	[L4][CO1] [10M]
	b	Mention the applications of Zener diode.	[L3][CO1] [2M]
7		Explain the terms w.r.t PN diode. i) Static Resistance ii) Dynamic Resistance and iii) Reverse Resistance.	[L2][CO1] [12M]
8	a	Explain the effect of temperature on the Diode characteristics.	[L2][CO1] [8M]
	b	When a reverse bias is applied to a germanium PN junction diode, the reverse saturation current at room temperature is $0.3\mu\text{A}$. Determine the current flowing in the diode when 0.15V forward bias is applied at room temperature.	[L3][CO1] [4M]
9	a	Compare and contrast PN diode with Zener diode.	[L2][CO1] [6M]
	b	The reverse saturation current of a silicon PN junction diode is $10\mu\text{A}$. Solve the diode current for the forward bias voltage of 0.6V at 25°C .	[L2][CO4] [6M]
10		Explain how the zener diode can be used as a voltage regulator.	[L3][CO1] [12M]

UNIT –III
RECTIFIERS

1	a	What is rectifier? Classify the different types of Rectifiers.	[L2][CO1][3M]
	b	Define and formulate the following terms i) Ripple Factor ii) efficiency and iii) PIV	[L1][CO1][9M]
2	a	Draw the circuit diagram of HWR and explain its operation with the help of waveforms.	[L3][CO1][6M]
	b	Derive the expressions for Ripple factor, PIV and efficiency for HWR.	[L2][CO1][6M]
3	a	Draw the circuit diagram of FWR and explain its operation with the help of waveforms.	[L2][CO1][6M]
	b	Derive the expressions for Ripple factor, PIV and efficiency for FWR.	[L2][CO1][6M]
4		A HWR uses a diode with 50Ω internal resistance, if RMS input is 110V and $R_L=1000\Omega$ then calculate: i) Peak output current ii) DC output current iii) RMS output current iv) Efficiency.	[L3][CO2][12M]
5	a	What is Filter? Classify different types of Filters.	[L2][CO1][3M]
	b	Demonstrate the working principle of LC filter with neat diagram and derive the expression for its ripple factor.	[L2][CO1][9M]
6	a	Compare the performance of various types of filters.	[L2][CO1][6M]
	b	Draw the circuit diagram for CLC or π filter and state its ripple factor.	[L1][CO1][6M]
7	a	Obtain the ripple factor of a FWR with shunt capacitor filter.	[L4][CO1][6M]
	b	Derive an expression for the ripple factor in a FWR using inductor filter.	[L4][CO1][6M]
8	a	Describe the operation of shunt capacitor filter with the help of circuit diagram and waveforms.	[L2][CO1][6M]
	b	Find the value of inductance to be used in the inductor filter connected to a full wave rectifier operating at 60 Hz to provide a dc output with 4% ripple for a 100Ω load.	[L1][CO2][6M]
9	a	Describe the operation of inductor filter with the help of circuit diagram and waveforms.	[L2][CO1][6M]
	b	Inspect the value of capacitance to be used in a capacitor filter connected to a full wave rectifier operating at a standard aircraft power frequency of 400 Hz, if the ripple factor is 10% for a load of 500Ω .	[L4][CO2][6M]
10	a	A half wave rectifier ,having a resistive load of 1000Ω ,rectifies an alternating voltage of 325V peak value and the diode has a forward resistance of 100Ω .Calculate (i)peak, average and rms value of current (ii) d.c. power output (iii) ac input power ,and (iv) efficiency of the rectifier.	[L4][CO2][6M]
	b	Compare full wave rectifier with half-wave rectifier.	[L5][CO1][6M]

UNIT –IV
BIPOLAR JUNCTION TRANSISTOR (BJT)

1	a	What is a BJT and its symbols? Explain the construction of NPN and PNP transistors.	[L1][CO1][6M]
	b	Explain the operation of NPN transistor under active region.	[L2][CO1][6M]
2	a	Compare the performance of a transistor in different configurations.	[L2][CO2][6M]
	b	Derive the relationship between α and β .	[L4][CO2] 6M]
3	a	Briefly explain the different configurations in BJT.	[L2][CO1] 6M]
	b	With a neat diagram, explain how a transistor acts as an amplifier.	[L2][CO3] 6M]
4	a	Explain the Input and Output characteristics of a BJT in CB Configuration.	[L2][CO3] 8M]
	b	If a transistor has α of 0.97, find the value of β . If $\beta=200$, find the value of α .	[L1][CO2] 4M]
5	a	Explain the Input and Output characteristics of a BJT in CE Configuration.	[L2][CO1] 8M]
	b	For a transistor, the leakage current is $0.1\mu\text{A}$ in CB configuration, while it is $19\mu\text{A}$ in CE configuration. Find α & β of the same transistor?	[L1][CO4] 4M]
6	a	Explain the Input and Output characteristics of a BJT in CC Configuration.	[L2][CO1] 8M]
	b	If the base current in a transistor is $20\mu\text{A}$ when the emitter current is 6.4mA , What are the values of α and β ? Also calculate the collector current.	[L1][CO2] 4M]
7	a	What is current amplification factor in CB, CE and CC configurations?	[L1][CO1] 6M]
	b	Derive the relation among α , β and γ .	[L6][CO1][6M]
8	a	Define Transistor Biasing. Explain the need for Biasing and their types.	[L1][CO2] 6M]
	b	Draw and explain the circuit for voltage divider bias for establishing a stable operating point.	[L4][CO2] 6M]
9	a	Define Stability Factor S, Stability Factor S' and Stability Factor S''	[L2][CO1][6M]
	b	Derive the relation among I_C , I_B and I_{CBO} .	[L4][CO2][6M]
10	a	Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point.	[L2][CO2] 6M]
	b	Draw a circuit which uses a diode to compensate for changes in I_{CO} . Explain how stabilization is achieved in the circuit.	[L2][CO2][6M]

UNIT –V
FIELD EFFECT TRANSISTOR (FET)

1	a	What is a JFET and its types & symbols?	[L1][CO1] [4M]
	b	Explain the construction and working principle of N-channel JFET.	[L2][CO1] [8M]
2	a	Sketch and explain the n-channel JFET output characteristics under applied bias.	[L2][CO1] [8M]
	b	Classify the types of MOSFETS with their symbols.	[L2][CO1] [4M]
3	a	List the differences between n-channel JFET and p-channel JFET.	[L4][CO1][6M]
	b	Briefly explain the term pinch-off voltage using drain characteristics of JFET.	[L2][CO2] [6M]
4	a	Compare the performance of BJT with FET.	[L2][CO1] [8M]
	b	List the applications of MOSFETs.	[L4][CO1] [4M]
5	a	Sketch the transfer characteristics of n-channel JFET and explain.	[L2][CO1] [8M]
	b	Compare the performance of MOSFET with FET.	[L2][CO1][4M]
6		Define the following FET parameters: i) Drain Resistance ii) Trans-conductance iii) Amplification factor	[L1][CO1] [12M]
7		With the help of neat diagram, explain the operation and characteristics of N-channel Depletion type MOSFET.	[L2][CO2] [12M]
8		With the help of neat diagram, explain the operation and characteristics of n-channel Enhancement type MOSFET.	[L2][CO2] [12M]
9	a	List differences between depletion and enhancement MOSFET.	[L4][CO1] [6M]
	b	Explain the voltage divider bias circuit of FET.	[L2][CO3] [6M]
10	a	List the types of biasing in FET.	[L4][CO3] [4M]
	b	Explain the different methods for fixing the Q-point in a FET.	[L2][CO4] [8M]