



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY  
(AUTONOMOUS)**

(Approved by AICTE, New Delhi & Affiliated to JNTUA, Ananthapuramu)  
(Accredited by NAAC with "A" Grade & ISO 9001 : 2008 Certified Institution)

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code : PRINCIPLES OF ELECTRICAL CIRCUITS (20EE0253)**



**Course & Branch : B. Tech -ECE**





**Year & Semester : I - B. Tech. & I - Semester**






**Regulation : R20**

**UNIT-I**

**FUNDAMENTALS OF ELECTRIC CIRCUITS**

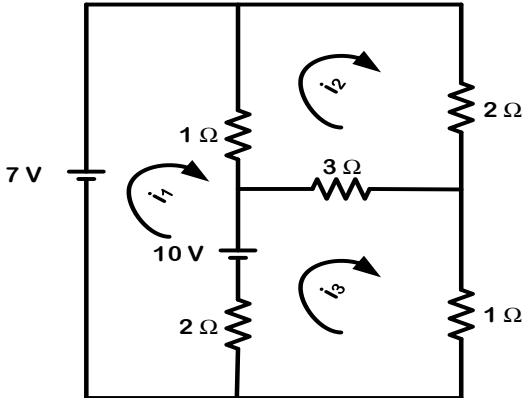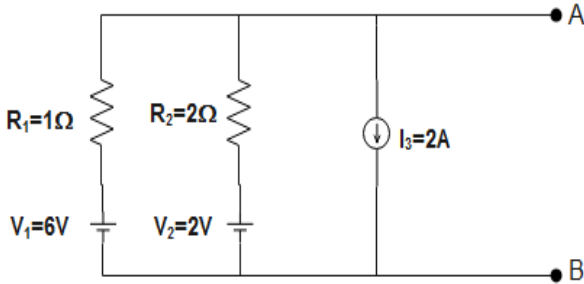1.	a)	Explain in detail about passive elements.	[L1] [CO1][6M]
	b)	State and explain Ohm's law.	[L1] [CO1] [6M]
2.	a)	Three resistances of values 20, 30 and 50 are connected in series across 20 V DC supply. Calculate, i) Equivalent resistance of the circuit. ii) Total current from the supply. iii) Voltage drop across each resistor. iv) Power dissipated in each resistor.	[L3] [CO1] [6M]
	b)	Determine the Equivalent capacitance when the capacitor are connected series and parallel	[L3] [CO1] [6M]
3.	a)	State and prove Kirchhoff's laws with suitable examples.	[L2] [CO1] [6M]
	b)	Find $i_1, i_2, i_3$ for the given circuit by using Kirchhoff's laws? 	[L3] [CO1] [6M]
4.	a)	Determine the equivalent current source between the terminals A-B. 	[L3] [CO1] [6M]

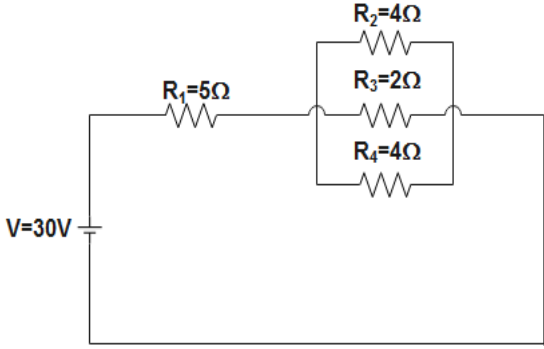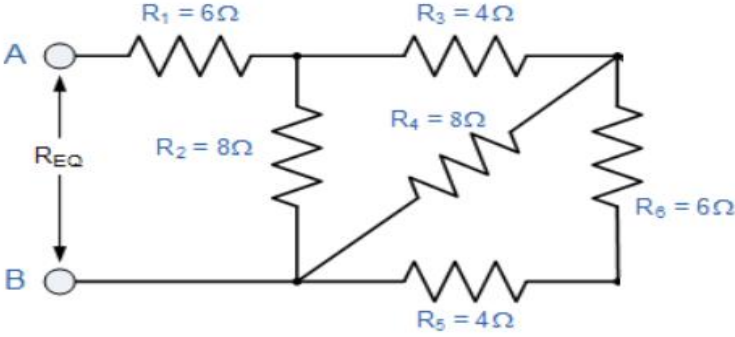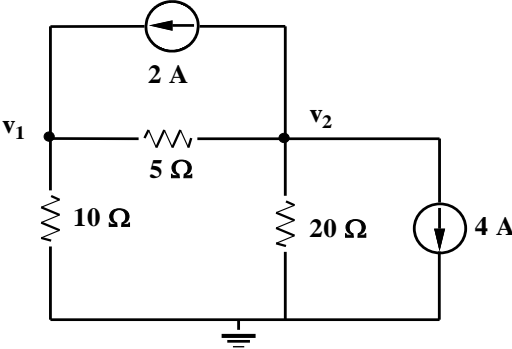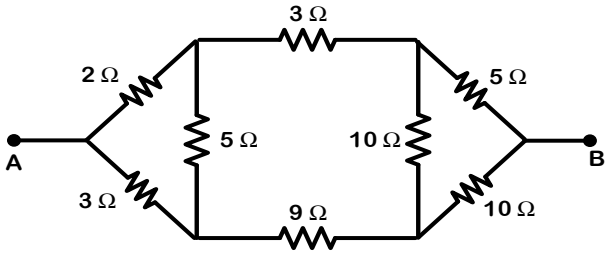
	<p>b) Determine Current through each resistor in the circuit? Using Current division method?</p> 	<p>[L3] [CO1] [6M]</p>
<p>5.</p>	<p>a) Find the equivalent resistance for the circuit shown below.</p> 	<p>[L3] [CO1] [6M]</p>
	<p>b) Determine the current in 5Ω resistor for the following network by using nodal analysis.</p> 	<p>[L3] [CO2] [6M]</p>
<p>6.</p>	<p>Find the voltage to be applied across AB in order to drive a current of 5A into the circuit.</p> 	<p>[L3] [CO1] [12M]</p>
<p>7.</p>	<p>Explain in detail about star to delta and delta to star transformation of given resistive network.</p>	<p>[L2] [CO1] [12M]</p>

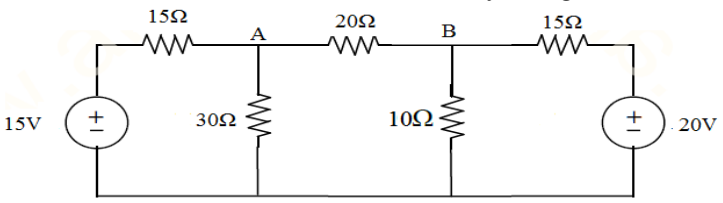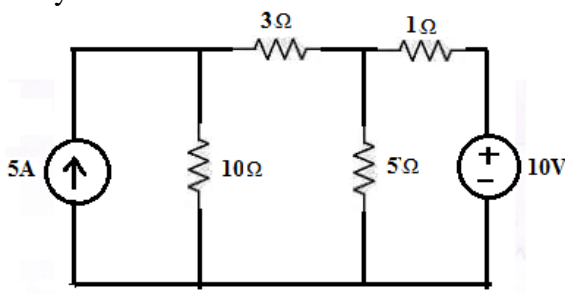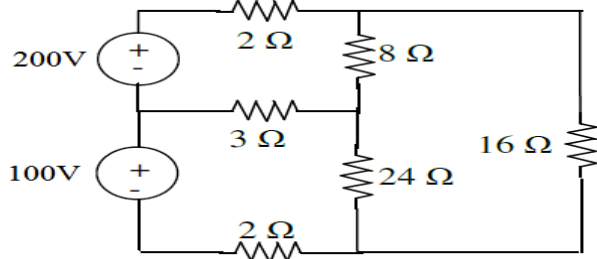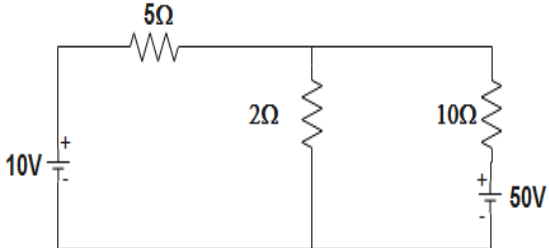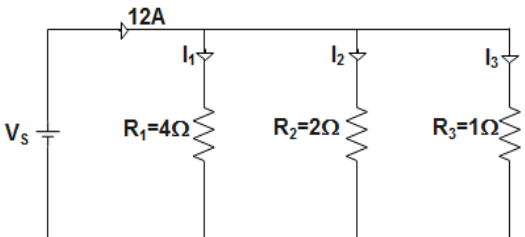8.	a)	<p>Determine the current in branch A-B by using KVL</p> 	[L2] [CO1] [6M]
	b)	<p>Determine the current in 10Ω resistor for the following network by using nodal analysis.</p> 	[L3] [CO2][6M]
9.	a)	<p>Determine the mesh currents for the circuit shown below.</p> 	[L3] [CO2] [6M]
	b)	<p>Explain about source transformation briefly.</p>	[L1][CO1][6M]
10.	a)	<p>Write the Mesh Current equations in the Circuit shown in figure below, and determine the currents</p> 	[L3] [CO2][6M]
	b)	<p>Determine Current through each resistor in the circuit? Using Current division method?</p> 	[L3] [CO1] [6M]

**UNIT - II**  
**NETWORK THEOREMS**


1.	a)	State Super position theorem	[L1] [CO3][2M]
	b)	By using superposition theorem find the current flowing through the 3 ohm resistor	[L3] [CO3] [10M]
2.	a)	State Thevenin's theorem	[L1] [CO3] [2M]
	b)	Find load current by using Thevenin's theorem for the following circuit where $R_L = 3\Omega$	[L3] [CO3] [10M]
3.	a)	State Norton's theorem.	[L1] [CO3] [2M]
	b)	Find Norton's equivalent circuit across AB for the circuit shown.	[L3] [CO3] [10M]
4.	a)	Explain the maximum power transfer theorem.	[L3][CO3][6M]
	b)	Determine the maximum power delivered to the load resistance $R_L$	[L2][CO3][6M]

5	a)	State Reciprocity theorem.	[L1] [CO3] [2M]
	b)	Verify reciprocity theorem for the network shown in below figure.	[L3][CO3][10M]
6.	a)	State Norton's theorem.	[L1] [CO3] [2M]
	b)	Find the Norton's equivalent for the circuit shown below.	[L3][CO3][10M]
7.	a)	Explain Millman's theorem in detail	[L1][CO3][6M]
	b)	Find the current $I_L$ , use millman's theorem as shown in figure below.	[L3][CO3][6M]
8.	a)	State Tellegen's theorem.	[L2][CO3][2M]
	b)	Verify Tellegen's theorem for the circuit shown in below figure.	[L3][CO3][10M]

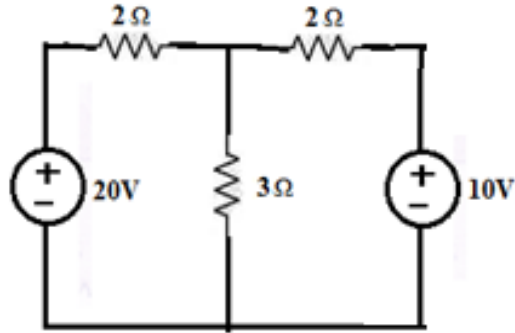


9. a) State Compensation theorem. [L2][CO3][2M]

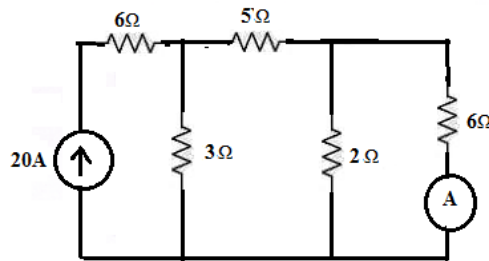
b) Determine the ammeter reading where it is connected to  $6\Omega$  resistor as shown in below figure. The internal resistance of the ammeter is  $2\Omega$ ., by using compensation theorem. [L3][CO3][12M]





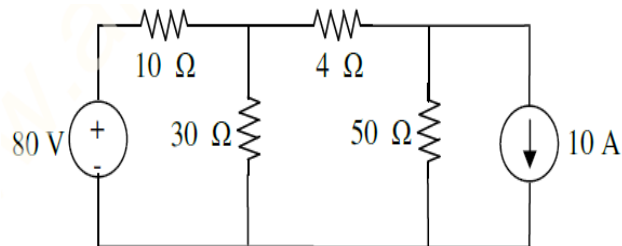10 Verify Superposition Theorem for  $4\Omega$  resistor for the following circuit. [L3][CO3][12M]




**UNIT – III****DC TRANSIENT ANALYSIS**


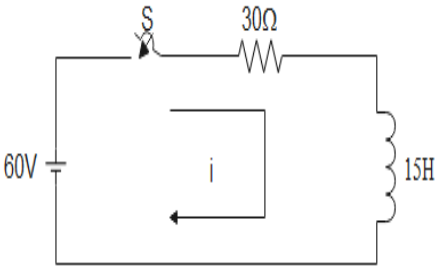
1	a)	Define transient response.	[L1][CO4][4M]
	b)	Derive the Transient Response of series RL-circuit with D.C excitation.	[L3][CO4][8M]
2	a)	Explain the application of transient analysis.	[L1][CO4][6M]
	b)	Derive the Transient Response of series RC-circuit with D.C excitation.	[L3][CO4][6M]
3		The Circuit Consists Of Resistance=20 Ohm, Inductance = 0.05H, Capacitance = 20uF in Series With a 100V Constant at t=0. Find The Current Transient.	[L3][CO4][12M]
4		Derive the Transient Response of series RLC-circuit with D.C excitation.	[L2][CO4][12M]
5	a)	Derive the Laplace Transform of Series RL Circuit.	[L2][CO4][6M]
	b)	What is the transient response of series RL and RC circuits with D.C excitation?	[L3][CO4][6M]
6	a)	Derive the Laplace Transform of Series RC Circuit	[L2][CO4][6M]
	b)	A series RL circuit with $R=30\Omega$ and $L= 15H$ has a constant voltage $V=60v$ applied at $t=0$ . Determine the current “I”, voltage across resistor and voltage across inductor.	[L3][CO4][6M]
			
7		A series RC circuit consists of a resistor of $10\Omega$ and capacitor of $0.1 F$ with a constant voltage of $20v$ , is applied to the circuit at $t=0$ . Obtain the current equation. Determine the voltage across the resistor and the capacitor.	[L3][CO4][6M]
8		A Series RC circuit consists of $R=5000\Omega$ , $C=20MF$ has a constant voltage $V=100v$ applied at $t=0$ and capacitor has no initial charge. Find the equation of $i$ , $V_R$ and $V_C$ .	[L3][CO4][12M]
9	a)	A Series RL circuit with $R=50\Omega$ and $L=10H$ has constant voltage $V=100volts$ applied at $t=0$ by the closing the switch find the complete current.	[L3][CO4][6M]

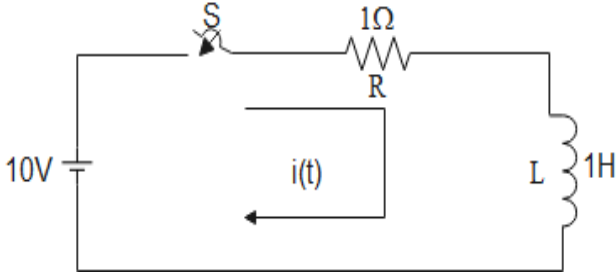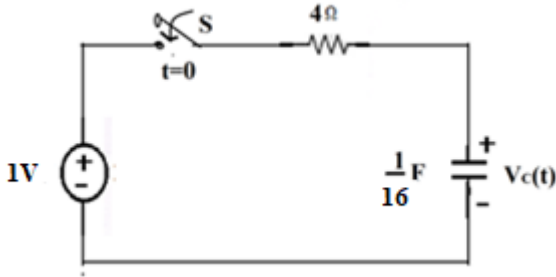	<p>b) A series RL circuit Switch 'S' is Closed at time <math>t = 0</math>. There is no current through 'L' Prior to Switching obtain the particular solution for <math>i(t)</math>.</p> 	[L3][CO4][6M]
10	<p>Determine The Current I for <math>T &gt; 0</math> If <math>V_c(0) = 9V</math> For The Circuit Shown In Fig.</p> 	[L3][CO4][12M]







**UNIT –IV**  
**SINGLE PHASE AC CIRCUITS**

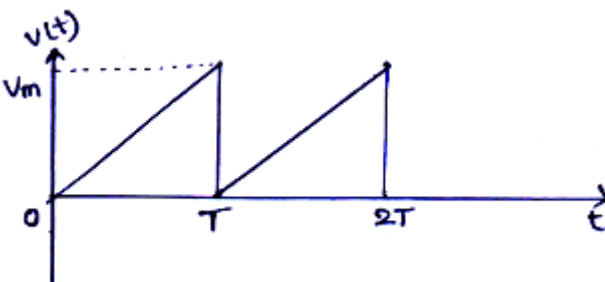1	a)	Derive an expression for RMS values of sine wave form.	[L2][CO5][6M]
	b)	An alternating current is expressed as $I = 14.14 \sin 314t$ . Determine. (i) Maximum current (ii) RMS current (iii) Frequency (iv) Instantaneous current when $t = 0.02$ msec.	[L2][CO5][6M]
2		Derive an expression for the current and impedance for a series RL circuit excited by a Sinusoidally alternating voltage. Draw the phasor diagrams.	[L2][CO5][12M]
3	a)	Define power factor, apparent power, active power and reactive power	[L1][CO5][8M]
	b)	Define Admittance and impedance	[L1][CO5][4M]
4	a)	Find the rms value for the following waveform 	[L3][CO5][6M]
	b)	Explain the phasor relation for R, L & C elements.	[L1][CO5][6M]
5	a)	A resistor of $50\Omega$ and inductance of $100$ mH are connected in series across $200$ V, $50$ Hz supply. Determine the following (i) Impedance (ii) current flowing through the circuit (iii) power factor	[L2][CO5][6M]
	b)	Explain resonance for series RLC circuit and derive the equation for resonant frequency.	[L2 [CO5][6M]
6		Derive an expression for the current and impedance for a series RC circuit excited by a Sinusoidally alternating voltage. Draw the phasor diagrams.	[L2][CO5][12M]

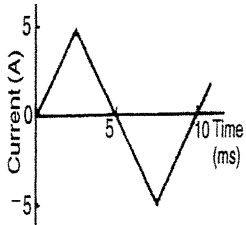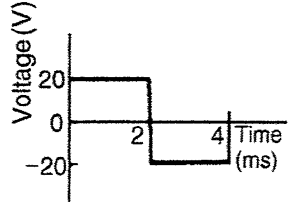7	<p>For the waveform shown below, determine for each (i) the frequency (ii) the average value over half a cycle (iii) the r.m.s. value (iv) the form factor</p> <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;">  <p>(a)</p> </div> <div style="text-align: center;">  <p>(b)</p> </div> </div>	[L3][CO5][12M]
8	<p>Find the peak value, the r.m.s. value, the frequency, the periodic time and the phase angle (in degrees and minutes) of the following alternating quantities:</p> <p>(a) <math>v = 90 \sin 400\pi t</math> volts (b) <math>i = 50 \sin(100\pi t + 0.30)</math> amperes</p> <p>(c) <math>e = 200 \sin(628.4t - 0.41)</math> volts</p>	[L2][CO5][12M]
9	<p>Derive an expression for the voltage and impedance for a series RLC circuit excited by a Sinusoidally alternating voltage.</p>	[L2][CO5][12M]
10	<p>A coil of resistance <math>10\Omega</math> and inductance of <math>0.1\text{H}</math> is connected in series with a <math>150\mu\text{F}</math> capacitor across a <math>200\text{V}</math>, <math>50\text{Hz}</math>. Calculate</p> <p>(i) inductive reactance (ii) capacitive reactance (iii) impedance</p> <p>(iv) current (v) power factor (vi) power in the circuit.</p>	[L3][CO5][12M]

**UNIT -V**  
**TWO PORT NETWORK & FILTERS**

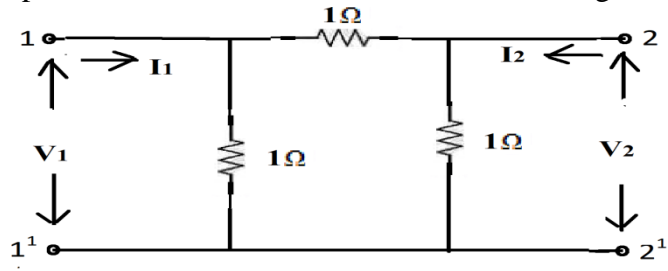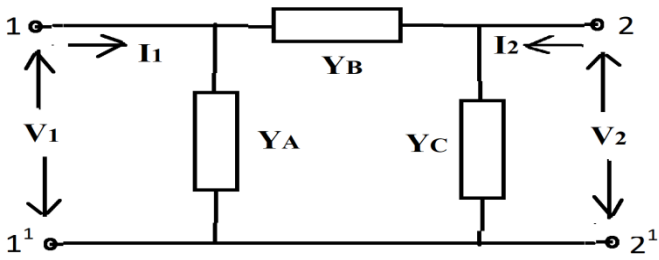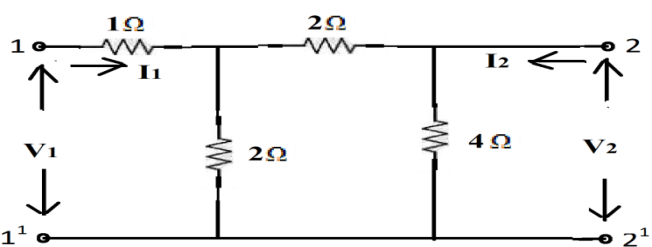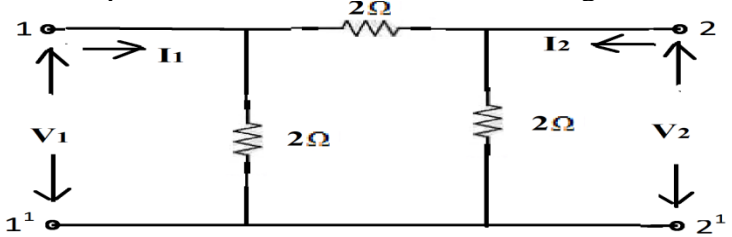1	a)	Explain about Impedance parameters.	[L1][CO6][6M]
	b)	<p>Find the Z-parameters of the network shown in below figure.</p> 	[L3][CO6][6M]
2	a)	Explain about short-circuit parameters.	[L1][CO6][6M]
	b)	<p>Find the Short-circuit parameters for the circuit shown in figure.</p> 	[L2][CO6][6M]
3	a)	Explain about h-parameters in terms of y-parameters	[L1][CO6][6M]
	b)	<p>Find the h-parameters of the network shown in figure.</p> 	[L3][CO6][6M]
4	a)	Explain about ABCD-parameters	[L1][CO6][6M]
	b)	<p>Find the transmission parameters for the circuit shown in figure.</p> 	[L3][CO6][6M]
5	a)	Find the transmission parameters for the circuit shown in figure.	[L3][CO6][6M]

	b)	Determine the y-parameters of the following network.	[L3][CO6][6M]
6	a)	Explain about classification of filters.	[L1][CO6][6M]
	b)	Design a High –pass filter having a cut-off frequency of 1kHz with a load resistance of 600Ω.	[L2][CO6][6M]
7		Explain about Constant-K band -pass filter in detail	[L2][CO6][12M]
8	a)	Explain about Constant-K low-pass filter in detail.	[L1][CO6][6M]
	b)	Design a Band-elimination filter having design impedance of 600Ω and cut-off frequencies $f_1 = 2\text{kHz}$ and $f_2 = 6\text{kHz}$ .	[L2][CO6][6M]
9		Explain about Constant-K High-pass filter in detail.	[L1][CO6][12M]
10		<p>The low-pass filter shown in the diagram, <math>V_{IN} = 10\text{ V}</math>. Calculate: (a) the reactance of the capacitor at 10 Hz, 1 kHz, and 100 kHz (b) the output voltage at each of these frequencies (c) the break frequency of this circuit (d) <math>V_{OUT}</math> at the break frequency.</p>	[L3][CO6][12M]

Prepared By: V.M.THENKANI,S MUNISEKHAR,V SIVA SUBRAMANYAM