

**QUESTION BANK (DESCRIPTIVE)**

SUBJECT WITH CODE:	ELECTRONIC DEVICES AND CIRCUITS (20EC0402)	COURSE & BRANCH:	B.TECH-EEE
YEAR & SEM:	I YR & II SEM	REGULATION:	R20

**UNIT – I
PN JUNCTION DIODE**

1	a)	Describe the construction of PN Junction Diode.	[L1][CO1]	[3M]
	b)	Define the following terms: a) Doping b) Depletion region c) Barrier Potential	[L1][CO1]	[3M]
	c)	Sketch the V-I Characteristics of a PN Junction Diode and illustrate its action under forward bias and reverse bias.	[L3][CO3]	[6M]
2	a)	Define Break down voltage and cut in voltage and give the typical values of cut-in voltage for Si and Ge diodes.	[L1][CO3]	[2M]
	b)	Analyze the current components of a PN Junction Diode and derive the diode current equation.	[L4][CO2]	[6M]
	c)	When a reverse bias is applied to a germanium PN Junction Diode, the reverse saturation current at room temperature is $0.3\mu\text{A}$. Determine the current flowing in the diode when 0.15V forward bias is applied at room temperature.	[L3][CO3]	[4M]
3	a)	Discuss the effect of temperature on V-I characteristics of a PN Junction Diode.	[L2][CO3]	[5M]
	b)	The reverse saturation current of a silicon PN Junction Diode is $10\mu\text{A}$. Calculate the diode current for the forward bias voltage of 0.6V at 25°C .	[L3][CO3]	[4M]
	c)	Draw the ideal diode characteristics of PN Junction Diode and give its circuit symbol.	[L1][CO3]	[3M]
4	a)	A PN junction germanium diode has a reverse saturation current of $0.10\mu\text{A}$ at the room temperature of 27°C . It is observed to be $30\mu\text{A}$, when the room temperature is increased. Calculate the new room temperature. Also determine the current passing through the diode at this new temperature.	[L3][CO2]	[7M]
	b)	Discuss about the forward and reverse resistances of a PN junction diode.	[L2][CO3]	[5M]
5	a)	Derive the expression for forward dynamic resistance of a PN junction diode.	[L3][CO2]	[7M]
	b)	Calculate the forward resistance of a PN Junction Diode when the forward current is 5mA at $T = 300\text{K}$. Assume Silicon diode.	[L3][CO2]	[5M]
6	a)	Define Transition and Diffusion capacitances of a PN Junction Diode.	[L1][CO3]	[4M]
	b)	Derive the expression for transition capacitance of a PN Junction Diode.	[L3][CO2]	[8M]
7	a)	Derive the expression for Diffusion capacitance of a PN Junction Diode.	[L3][CO3]	[8M]
	b)	List the applications of PN Junction and Zener Diodes.	[L1][CO1]	[4M]
8	a)	Explain Breakdown mechanisms in PN Junction Diode.	[L2][CO3]	[6M]
	b)	Draw the circuit symbol of Zener diode and label its terminals.	[L1][CO1]	[1M]
	c)	Explain and plot the V-I characteristics of Zener Diode.	[L2][CO3]	[5M]
9	a)	Show that the Zener Diode can act as a voltage regulator with a neat circuit diagram.	[L2][CO4]	[6M]
	b)	Define clippers and Clampers. Also list their types.	[L1][CO1]	[2M]
	c)	Explain about a Combination Clipper and sketch its input –output waveforms.	[L2][CO4]	[4M]
10	a)	Construct the Positive and Negative Diode Clippers and explain with neat waveforms.	[L3][CO4]	[6M]
	b)	What is a Clamper circuit? Describe about positive and negative clampers with neat circuit diagram.	[L1][CO4]	[6M]

UNIT –II

RECTIFIERS, FILTERS AND SPECIAL PURPOSE DEVICES

1.	a)	Define a Rectifier and list its types.	[L1][CO1]	[2M]
	b)	Draw the circuit diagram of a Half Wave Rectifier and explain its operation with the help of waveforms.	[L1][CO4]	[3M]
	c)	Define the following terms: i) Ripple factor ii) Efficiency iii) Peak inverse voltage iv) Transformer utilization factor.	[L1][CO2]	[3M]
	d)	Derive the expressions for Average DC Voltage, RMS Value of voltage, DC Output Power and AC input Power for a Half Wave Rectifier.	[L3][CO5]	[4M]
2.	a)	Draw the circuit diagram of a Full Wave Rectifier and with the help of waveforms describe its operation.	[L1][CO4]	[6M]
	b)	Derive the expressions for Average DC current, RMS Value of Current, DC Power Output and AC Power input for a Full Wave Rectifier. List the advantages.	[L3][CO5]	[4M]
	c)	List the advantages of FWR and HWR.	[L1][CO1]	[2M]
3.	a)	A Half Wave Rectifier is supplied from a 230V, 50 Hz supply with a step-down ratio of 3:1 to a resistive load of 10k Ω . The diode forward resistance is 75 Ω while transformer secondary is 10 Ω . Calculate maximum, average, RMS values of current, DC output voltage, efficiency of rectification and ripple factor.	[L4][CO5]	[6M]
	b)	A Full Wave Rectifier circuit is fed from a transformer having a center-tapped secondary winding. The RMS voltage from either end of secondary to center tap is 30V. If the diode forward resistance is 2 Ω and that of the half secondary is 8 Ω , for a load of 1 K Ω . Calculate DC power delivered to the load, efficiency of rectification and Transformer Utilization Factor (TUF) of secondary.	[L4][CO5]	[6M]
4.	a)	With a neat circuit diagram and waveforms, illustrate the working of a Bridge rectifier.	[L2][CO3]	[4M]
	b)	A 5K Ω load is fed from a bridge rectifier connected across a transformer secondary whose primary is connected to 460V, 50 Hz supply. The ratio of number of primary turns to secondary turns is 2:1. Estimate DC load current, ripple voltage and PIV rating of diode.	[L4][CO5]	[4M]
	c)	Compare different rectifiers.	[L2][CO2]	[4M]
5.	a)	Define a filter and give its types.	[L1][CO1]	[2M]
	b)	Draw the circuit diagram of Full Wave Rectifier with Inductor filter and illustrate its operation. Also derive the expression for ripple factor.	[L1][CO3]	[5M]
	c)	Find the value of inductance to be used in the Inductor filter connected to a Full Wave Rectifier operating at 60 Hz to provide a DC output with 4% ripple for a 100 Ω load.	[L3][CO6]	[3M]
	d)	List the advantages and disadvantages of FWR with inductor Filter.	[L1][CO5]	[2M]
6.	a)	With neat circuit diagram and waveforms, explain the operation of Full Wave Rectifier with Capacitor filter and derive the expression for its ripple factor.	[L2][CO3]	[6M]
	b)	Calculate the value of capacitance to be used in a Capacitor filter connected to a full wave rectifier operating at a standard aircraft power frequency of 400 Hz, if the ripple factor is 10% for a load of 500 Ω .	[L3][CO6]	[3M]
7.	c)	List the advantages and disadvantages of FWR with capacitor filter.	[L1][CO5]	[3M]
	a)	Demonstrate the working principle of LC filter with neat circuit diagram and derive the expression for its ripple factor. List the advantages and disadvantages.	[L2][CO3]	[5M]
	b)	Explain the working principle of CLC or π section filter and derive expression for its ripple factor. List the advantages and disadvantages.	[L2][CO3]	[5M]
8.	c)	Compare different filter circuits.	[L2][CO2]	[2M]
	a)	Draw the circuit symbol of varactor diode and list its applications.	[L1][CO1]	[2M]

	b)	Explain the principle involved in working of Varactor Diode and give its characteristics.	[L2][CO1] [CO3]	[3M]
	c)	Draw the circuit symbol of Tunnel diode and explain the tunneling phenomenon.	[L1][CO1]	[2M]
	d)	Explain the Volt-Ampere (V-I) characteristics of a Tunnel Diode with the help of energy band diagrams and List its applications.	[L2][CO3]	[5M]
9.	a)	Draw the circuit symbol and label the terminals of UJT. Justify name Uni Junction Transistor.	[L1][CO1]	[2M]
	b)	Demonstrate the construction, working and characteristics of UJT with neat diagram. List the applications	[L2][CO1] [CO3]	[5M]
	c)	Explain with diagram the construction, working and applications of Solar Cell.	[L2][CO1] [CO3]	[5M]
10.	a)	Explain dynamic scattering LCD and field effect LCD with neat diagram. List the advantages and applications	[L2][CO1]	[6M]
	b)	Explain the construction, working principle and characteristics of LED with neat diagram. List the advantages and applications.	[L2][CO1] [CO3]	[6M]

UNIT –III
TRANSISTOR CHARACTERISTICS: BJT & FET



1	a)	Define a transistor. Draw the circuit symbols of PNP and NPN transistor and label all terminals.	[L1][CO1]	[2M]
	b)	Explain the construction of NPN transistor with a neat diagram.	[L2][CO1]	[5M]
	c)	If the base current in a transistor is $20\mu\text{A}$ when the emitter current is 6.4mA , what are the values of α and β ? Also calculate the collector current.	[L3][CO2]	[5M]
2	a)	Explain the operation an NPN transistor.	[L2][CO3]	[6M]
	b)	Explain the current components of a PNP transistor.	[L2][CO3]	[6M]
3	a)	Evaluate the relation between α and β of a Transistor.	[L4][CO2]	[5M]
	b)	With a neat diagram, Explain how a transistor acts as an amplifier.	[L2][CO3]	[7M]
4	a)	With neat diagram, explain the Input and Output characteristics of a BJT in CB Configuration. Explain Early effect.	[L2][CO3]	[5M]
	b)	Define the following terms: i) Emitter efficiency ii) Transport factor iii) Large signal current gain.	[L1][CO2]	[3M]
	c)	For a transistor, the leakage current is $0.1\mu\text{A}$ in CB configuration, while it is $19\mu\text{A}$ in CE configuration. Find α & β of the transistor?	[L3][CO2]	[4M]
5	a)	Explain the Input and Output characteristics of a BJT in CE Configuration.	[L2][CO3]	[4M]
	b)	Why CE configuration is most widely used in amplifier circuits?	[L4][CO5]	[2M]
	c)	Illustrate the Input and Output characteristics of BJT in CC Configuration.	[L2][CO3]	[3M]
	d)	Compare Transistor configurations.	[L4][CO2]	[3M]
6	a)	Define FET and explain different types of FET.	[L1][CO1]	[5M]
	b)	Explain the construction and working principle of N-Channel JFET.	[L2][CO3]	[7M]
7	a)	Explain the characteristics of N-Channel JFET and define JFET parameters.	[L2][CO3]	[5M]
	b)	Explain the construction and Characteristics of N-Channel depletion type MOSFET.	[L2][CO1]	[7M]
8	a)	Draw the circuit symbols of different JFETs and MOSFETs and list their applications.	[L1][CO1] [CO3]	[2M]
	b)	With the help of neat diagram, explain the construction and operation of N-channel enhancement type MOSFET.	[L2][CO2]	[4M]
	c)	Compare BJT with JFET.	[L4][CO2]	[4M]
9	a)	List the differences between Depletion and Enhancement MOSFETs.	[L1][CO2]	[6M]
	b)	Explain the operation of N-Channel depletion type MOSFET with diagram.	[L2][CO3]	[6M]
10	a)	Explain the characteristics of N-Channel enhancement type MOSFET.	[L2][CO1]	[6M]
	b)	Compare the performance of JFET with MOSFET.	[L4][CO1]	[6M]

UNIT- IV TRANSISTOR BIASING AND THERMAL STABILIZATION

1	a)	Define transistor biasing and explain the need for biasing.	[L1][CO2]	[3M]
	b)	Derive the expression for Stability Factor, S_f , from Collector current equation.	[L3][CO3]	[4M]
	c)	Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point.	[L2][CO3]	[5M]
2	a)	List the different types of Biasing a Transistor and explain the Fixed Bias of a Transistor.	[L1][CO3]	[7M]
	b)	Determine the expression for stability factor, S for fixed bias circuit and list its disadvantages.	[L3][CO5]	[5M]
3	a)	Explain Collector to Base bias of a Transistor with neat circuit diagram and determine Q-point.	[L2][CO3]	[6M]
	b)	For the circuit shown in the Figure, solve I_B , I_C , V_{CE} , V_B , V_C and V_{BC} . Assume that $V_{BE} = 0$ and $\beta = 50$.	[L3][CO5]	[6M]

4	a)	Define Stability Factor S . Derive the stability factor, S for collector to base bias of BJT.	[L1][CO5]	[6M]
	b)	Design a collector to base bias circuit for the specified conditions: $V_{cc} = 15V$, $V_{CE} = 5V$, $I_C = 5mA$ and $\beta = 100$.	[L3][CO6]	[6M]
5	a)	Draw the circuit diagram of Self Bias of a Transistor and determine its Q-point.	[L1][CO6]	[6M]
	b)	Estimate the stability factors S , S' and S'' of a BJT Voltage Divider bias.	[L2][CO5]	[6M]
6	a)	Define Bias compensation technique and mention its types.	[L1][CO3]	[4M]
	b)	Explain Diode Compensation Technique for the parameters of V_{BE} and I_{CO} .	[L2][CO4]	[6M]
7	a)	Illustrate Thermistor Compensation Technique for stabilization against variations in Q-point.	[L3][CO4]	[6M]
	b)	For the circuit shown in Figure, $\beta = 100$ for the silicon transistor. Calculate V_{CE} and I_C .	[L3][CO6]	[6M]


8	a)	Define and Explain Thermal Runaway and Thermal Resistance.	[L2][CO2]	[6M]
---	----	--	-----------	------

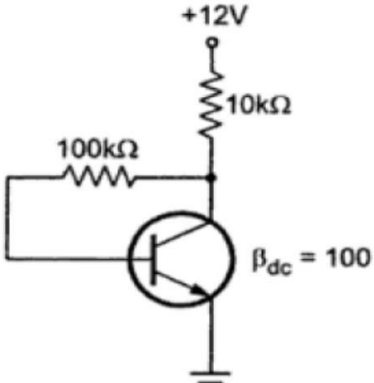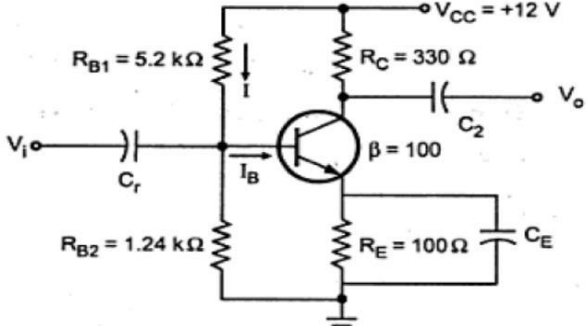	<p>b) Determine the Q-point for the circuit shown in the Figure</p> 	[L3][CO6]	[6M]
9	<p>a) Draw the DC load line for the following transistor configuration. Obtain the quiescent point.</p> 	[L1][CO6]	[6M]
	<p>b) Calculate the values of Resistors in a fixed bias circuit using the following specifications: $I_{CQ}=9.2\text{mA}$, $V_{CEQ}=4.4\text{V}$, $h_{fe}=1115$, $V_{BE}=0.7\text{V}$ & $V_{CC}=9\text{V}$.</p>	[L4][CO6]	[6M]
10	<p>a) Estimate the condition for achieving Thermal Stability.</p>	[L4][CO4]	[6M]
	<p>b) If the various parameters of a CE amplifier which uses the self bias method are $V_{CC}=12\text{V}$, $R_1=10\text{K}\Omega$, $R_2=5\text{K}\Omega$, $R_c=1\text{K}\Omega$, $R_E=2\text{K}\Omega$ & $\beta=100$, find the operating point. Assume Si Transistor.</p>	[L3][CO6]	[6M]

UNIT- V
SMALL SIGNAL LOW FREQUENCY TRANSISTOR
AMPLIFIER

1	a)	What is a small signal low frequency transistor amplifier?	[L1][CO2]	[2M]
	b)	Define h-parameters and draw the generalized h-parameter model of a Transistor. Why hybrid model is used for the analysis of BJT amplifier at low frequencies?	[L1][CO2]	[4M]
	c)	Draw the hybrid model for a transistor in CE configuration and derive its hybrid parameters.	[L1][CO2]	[6M]
2	a)	Using low frequency h-parameter model, Evaluate the expressions for voltage gain, current gain, input impedance and output admittance for a BJT Amplifier in CE configuration.	[L4][CO4]	[7M]
	b)	A CE amplifier is driven by a voltage source of internal resistance $R_s = 800\Omega$ and the load impedance of $R_L = 1000\Omega$. The h-parameters are $h_{ie} = 1k$, $h_{fe} = 50$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Find current gain, voltage gain, input impedance and output impedance using exact analysis.	[L3][CO5]	[5M]
3	a)	With neat diagram, summarize the parameters of CE amplifier using approximate analysis.	[L2][CO5]	[6M]
	b)	Examine the expressions for current gain, voltage gain, input impedance and output impedance of CB amplifier using simplified hybrid model.	[L3][CO5]	[6M]
4	a)	Draw the simplified h-parameter model for a transistor in CE, CB and CC configuration.	[L1][CO2]	[6M]
	b)	A CE amplifier is driven by a voltage source of internal resistance $R_s = 800\Omega$ and the load impedance of $R_L = 1000\Omega$. The h-parameters are $h_{ie} = 1k$, $h_{fe} = 50$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Find current gain, voltage gain, input impedance and output impedance using approximate analysis.	[L3][CO5]	[6M]
5	a)	Derive expressions for A_i , R_i , A_v and R_o for a Common Collector Amplifier using simplified hybrid model.	[L3][CO5]	[6M]
	b)	A voltage source of internal resistance, $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L = 2000\Omega$. The CE h parameters are $h_{fe} = 60$, $h_{ie} = 1200\Omega$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Calculate A_i , R_i , A_v and R_o using approximate analysis.	[L3][CO5]	[6M]
6	a)	For a CB transistor amplifier driven by a voltage source of internal resistance $R_s = 1200\Omega$, the load Impedance of $R_L = 1000\Omega$. The h- parameters are $h_{ib} = 22\Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$, $h_{ob} = 0.5\mu A/V$. Find current gain, voltage gain, input impedance and output impedance using approximate analysis.	[L3][CO6]	[6M]
	b)	Analyze CE amplifier with emitter resistance using simplified h-parameter model.	[L4][CO5]	[6M]
7	a)	Consider a single stage CE amplifier with $R_s = 1k\Omega$, $R_1 = 50k\Omega$, $R_2 = 2k\Omega$, $R_c = 1k\Omega$, $R_L = 1.2k\Omega$, $h_{fe} = 50$, $h_{ie} = 1.1k$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2.5 \times 10^{-4}$, as shown in Fig. Calculate A_i , R_i , A_v , A_{vs} , A_{is} and R_o .	[L3][CO5]	[8M]
	b)	Differentiate between CE, CB and CC amplifiers.	[L4][CO5]	[4M]

8	a)	A CE amplifier is driven by a voltage source of internal resistance, $R_s = 1000\Omega$ and the load impedance of $R_C = 2k\Omega$. The h-parameters are $h_{ie} = 1.3k$, $h_{fe} = 55$, $h_{oe} = 22\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Neglecting biasing resistors, Estimate the value of current gain, voltage gain, input impedance, output impedance for the value of Emitter Resistor $R_E = 200\Omega$ inserted in the emitter circuit.	[L4][CO4]	[8M]
	b)	Draw the small signal model of FET.	[L1][CO2]	[4M]
9	a)	Define JFET parameters and establish relation between them.	[L1][CO2]	[4M]
	b)	Summarize the expressions for input impedance, output impedance and voltage gain of JFET Common Drain amplifier with neat diagram.	[L2][CO5]	[8M]
10	a)	For the circuit shown in figure below, determine input impedance, output impedance and voltage gain.	[L3][CO5]	[6M]
	b)	Draw the circuit diagram of JFET Common Source amplifier with voltage divider bias for bypassed R_s and determine the expression for input impedance, output impedance and voltage gain.	[L1][CO5]	[6M]

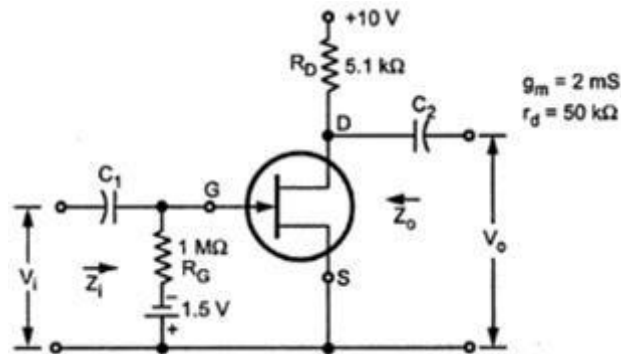

Prepared by

P SARANYA

Assistant Professor

Dept of ECE