



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY::PUTTUR-517583**  
(Autonomous)

Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code:** BASIC ELECTRONICS  
ENGINEERING (20EC0445)

**Course & Branch:** B. Tech & CSE, CSM,  
CAD, CAI, CCC, CSIT, CIC

**Year & Sem:** I-B.Tech & I-Sem

**Regulation:** R20

**UNIT-I**

**Basics of Semiconductor**

1.	a)	Explain the following terms: Conductors Insulators Semiconductors and give an example for each.	[L2][CO1]	[8M]
	b)	Explain the crystal structure of silicon with a neat sketch.	[L2][CO1]	[4M]
2.	a)	Explain the 2-D representation of the Germanium crystal structure with neat a sketch.	[L2][CO1]	[4M]
	b)	Describe the energy band diagrams.	[L2][CO1]	[8M]
3.	a)	Differentiate between the valence band and conduction band in detail.	[L2][CO1]	[4M]
	b)	Distinguish between conductors, semiconductors and insulators.	[L2][CO1]	[8M]
4.	a)	Differentiate between the forbidden energy gap and Fermi level in the valence band and conduction band.	[L2][CO1]	[6M]
	b)	Compare and contrast the electrical properties of Silicon and Germanium.	[L2][CO1]	[6M]
5.	a)	Distinguish between intrinsic and extrinsic semiconductors and explain the process of conduction in each of them.	[L2][CO1]	[8M]
	b)	Give examples of donor and acceptor impurities.	[L2][CO1]	[4M]
6.	a)	Draw the atomic structure of a semiconductor and explain why an Intrinsic semiconductor is relatively a poor conductor of electricity.	[L1][CO1]	[6M]
	b)	What is meant by doping in semiconductors? What is the need for doping?	[L1][CO1]	[6M]
7.	a)	Discuss the conduction properties of semiconductors and explain the process of electron-hole pair generation and recombination.	[L2][CO1]	[8M]
	b)	Intrinsic materials are not widely used, Explain the reasons?	[L2][CO1]	[4M]
8.	a)	List the advantages of n-type over p-type semiconductors.	[L1][CO1]	[4M]
	b)	Compare p-type and n-type semiconductors.	[L2][CO1]	[8M]
9.	a)	Explain drift current with expressions.	[L2][CO1]	[6M]
	b)	Explain diffusion current with expressions.	[L2][CO1]	[6M]
10.	a)	Explain in detail about mass action law.	[L2][CO1]	[4M]
	b)	Describe the charge neutrality in semiconductors in detail.	[L2][CO1]	[8M]


**UNIT –II**  
**PN JUNCTION DIODE**

1.	a)	Define PN Junction and Explain how Depletion layer is formed in open circuited PN junction diode.	[L2][CO1]	[6M]
	b)	Define and discuss the barrier potential of a PN junction diode with a neat sketch.	[L2][CO1]	[6M]
2.	a)	Illustrate the action of PN junction diode under forward bias and reverse bias and sketch its V-I Characteristics.	[L3][CO1]	[6M]
	b)	Draw the ideal diode characteristics of PN junction diode and its electrical equivalent model.	[L1][CO1]	[6M]
3.	a)	A PN junction diode has a reverse saturation current of $30 \mu\text{A}$ at a temperature of $125^{\circ}\text{C}$ . At the same temperature calculate the dynamic resistance for $0.2 \text{ V}$ bias in forward and reverse direction.	[L3][CO4]	[4M]
	b)	Analyze the current components in a PN diode and derive the expression for diode current.	[L4][CO1]	[8M]
4.	a)	When a reverse bias is applied to a germanium PN junction diode, the reverse saturation current at room temperature is $0.3 \mu\text{A}$ . Determine the current flowing in the diode when $0.15 \text{ V}$ forward bias is applied at room temperature.	[L3][CO4]	[4M]
	b)	Demonstrate the temperature dependence of the V-I characteristics of PN junction diode.	[L2][CO1]	[8M]
5.	a)	The reverse saturation current of a silicon PN junction diode is $10 \mu\text{A}$ . Calculate the diode current for the forward bias voltage of $0.6 \text{ V}$ at $25^{\circ}\text{C}$ .	[L3][CO1]	[4M]
	b)	Discuss the Diode Resistances.	[L2][CO1]	[8M]
6.	a)	Calculate the forward resistance of a PN junction diode when the forward current is $5 \text{ mA}$ at $T = 300 \text{ K}$ . Assume Silicon diode.	[L3][CO1]	[6M]
	b)	Define Transition and Diffusion capacitances of a PN junction Diode.	[L1][CO1]	[6M]
7.	a)	Describe Transition and Diffusion capacitances of a PN junction Diode with expressions.	[L5][CO1]	[6M]
	b)	Discuss about Breakdown mechanisms in PN Junction Diode.	[L2][CO1]	[6M]
8.	a)	Distinguish between PN junction diode and Zener diode.	[L1][CO1]	[6M]
	b)	The reverse saturation current of a Germanium PN junction diode is $8 \mu\text{A}$ . Find the diode current for the forward bias voltage of $0.3 \text{ V}$ at $27^{\circ}\text{C}$ .	[L3][CO2]	[6M]
9.	a)	List the applications of PN junction diode and Zener diode.	[L1][CO1]	[6M]
	b)	Define Breakdown voltage and draw the symbol of Zener Diode.	[L1][CO1]	[6M]
10.	a)	Draw and explain the V-I characteristics of Zener diode.	[L1][CO1]	[4M]
	b)	Explain the Zener voltage regulator with a neat diagram.	[L2][CO2]	[4M]
	c)	Design and draw a Zener regulator circuit to meet the following specifications. Load voltage= $8 \text{ V}$ , Input voltage= $30 \text{ V}$ , Load current= $0-50 \text{ mA}$ , $I_{z\text{min}} = 5 \text{ mA}$ , $P_z = 1 \text{ W}$ .	[L3][CO3]	[4M]

**UNIT –III**  
**RECTIFIERS**

1.	a)	i) Define Rectifier and classify them.	[L2][CO1]	[2M]
		ii) Draw the circuit diagram of a half wave rectifier and explain its operation.	[L1][CO1]	[4M]
	b)	Derive the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output, AC Power input and Efficiency of a Half Wave Rectifier.	[L3][CO2]	[6M]
2.	a)	A half wave rectifier, having a resistive load of $1000\Omega$ , rectifies an alternating voltage of 325V peak value and the diode has a forward resistance of $100\Omega$ . Calculate (a) peak, average and rms value of current (b) dc power output (c) ac input power, and (d) efficiency of the rectifier.	[L4][CO2]	[6M]
	b)	A voltage of $200\cos\omega t$ is applied to Half Wave Rectifier with load resistance of 5 kohm, find the maximum dc current, rms current and ripple factor	[L3][CO2]	[6M]
3.	a)	Draw the circuit diagram of a Full wave rectifier and with the help of waveforms describe its operation.	[L1][CO1]	[6M]
	b)	Derive the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output, AC Power input and Efficiency of a Full Wave Rectifier.	[L3][CO2]	[6M]
4.	a)	In a full wave rectifier, the transformer rms secondary voltage from center tap to each end of the secondary is 50V. The load resistance is $900\Omega$ . If the diode resistance and transformer secondary winding resistance together has a resistance of $100\Omega$ , determine the average load current and rms value of load current.	[L3][CO2]	[8M]
	b)	Compare the Full wave and Half wave rectifiers.	[L2][CO1]	[4M]
5.	a)	Determine the ripple factor for both half wave and full wave rectifier.	[L3][CO2]	[6M]
	b)	List the advantages of full wave rectifier over the half wave rectifier.	[L1][CO1]	[6M]
6.	a)	Define Filter and discuss various types of filters.	[L2][CO1]	[4M]
	b)	Draw the circuit diagram of Full wave rectifier with inductor filter and explain its operation. Also derive the expression for ripple factor.	[L3][CO2]	[8M]
7.	a)	Find the value of inductance to be used in the inductor filter connected to a full wave rectifier operating at 60 Hz to provide a dc output with 4% ripple for a $100\Omega$ load.	[L3][CO5]	[4M]
	b)	With neat circuit diagram and waveforms, Explain the operation of Full wave rectifier with capacitor Filter and derive the expression for its ripple factor.	[L3][CO2]	[8M]
8.	a)	Determine the value of capacitance to be used in a capacitor filter connected to a full wave rectifier operating at a standard aircraft power frequency of 400 Hz, if the ripple factor is 10% for a load of $500\Omega$ .	[L3][CO5]	[4M]
	b)	Explain the working principle of rectifiers with and without capacitors.	[L2][CO1]	[8M]
9.	a)	Demonstrate the working principle of LC filter with neat diagram and derive the expression for its ripple factor.	[L3][CO2]	[8M]
	b)	Design a filter for full wave circuit with LC filter provides an output voltage of 10V with a load current of 200mA and the ripple is limited to 2%.	[L3][CO4]	[4M]
10.	a)	Explain the construction and working principle of CLC or $\pi$ section filter along with derivation for its ripple factor.	[L3][CO2]	[8M]
	b)	Compare various types of filters.	[L2][CO1]	[4M]

**UNIT –IV**  
**BIPOLAR JUNCTION TRANSISTOR (BJT)**

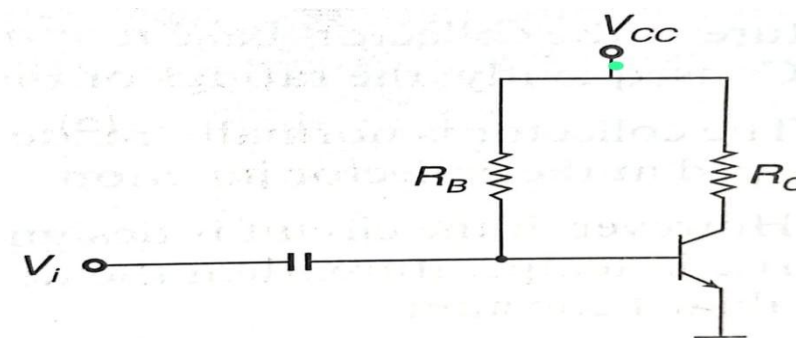1.	a)	i) Describe the construction of BJT, List different types of BJTs and draw the symbols.	[L1][CO1]	[2M]
		ii) Discuss the operation of NPN transistor with neat diagram.	[L2][CO1]	[6M]
	b)	If the base current in a transistor is $20\mu\text{A}$ when the emitter current is $6.4\text{mA}$ What are the values of $\alpha$ and $\beta$ ? Also calculate the collector current.	[L3][CO4]	[4M]
2.	a)	Explain the current components of PNP transistor.	[L2][CO2]	[6M]
	b)	Draw the Input and Output characteristics of a BJT in CB Configuration.	[L1][CO1]	[6M]
3.	a)	Explain the Input and Output characteristics of a BJT in CE Configuration.	[L2][CO1]	[6M]
	b)	For a transistor, the leakage current is $0.1\mu\text{A}$ in CB configuration, While it in CE configuration. Calculate $\alpha$ & $\beta$ of the same transistor?	[L3][CO2]	[6M]
4.	a)	Explain the Input and Output characteristics of a BJT in CC Configuration.	[L2][CO1]	[6M]
	b)	Derive the relation between $\alpha$ , $\beta$ and $\gamma$ of a Transistor.	[L3][CO2]	[6M]
5.	a)	Compare the configuration of CE, CB and CC.	[L2][CO1]	[6M]
	b)	With a neat diagram, Explain how a transistor acts as an amplifier?	[L2][CO2]	[6M]
6.	a)	Define Transistor Biasing and explain the need for Biasing.	[L2][CO2]	[8M]
	b)	List the different types of Biasing.	[L1][CO1]	[4M]
7.	a)	Explain the concept of DC and AC Load lines and discuss the criteria for Fixing the Q-point.	[L2][CO2]	[6M]
	b)	Define Stability Factor S. Derive the expressions for the stability factors S and S' of a BJT bias.	[L1][CO2]	[6M]
8.	a)	Discuss about the different types of biasing	[L2][CO2]	[6M]
	b)	Explain the operation of self-bias circuit of BJT and its advantages.	[L2][CO2]	[6M]
9.	a)	Design the circuit shown in figure given Q-point values are to be $I_{CQ} = 1\text{mA}$ and $V_{CEQ} = 6\text{V}$ . Assume that $V_{CC} = 10\text{V}$ , $\beta = 100$ , $V_{BE\text{sat}} = 0.7\text{V}$ .	[L4][CO6]	[6M]
				
	b)	Interpret Diode Compensation Technique for the parameters $V_{BE}$ and $I_{CO}$ .	[L3][CO2]	[6M]
10.	a)	Illustrate Thermistor Compensation Technique.	[L3][CO1]	[6M]
	b)	Discuss about Sensistor Compensation Technique.	[L2][CO1]	[6M]

**UNIT –V**  
**FIELD EFFECT TRANSISTOR (FET)**

1.	a)	Classify the types of JFET and Draw its symbols.	[L2][CO1]	[4M]
	b)	Explain the construction and working principle of N-channel JFET.	[L2][CO1]	[8M]
2.	a)	Sketch the drain characteristics N-channel JFET.	[L3][CO1]	[6M]
	b)	Explain the different regions of operation of N-Channel JFET.	[L2][CO1]	[6M]
3.	a)	Explain the construction and working principle of P-channel JFET.	[L3][CO1]	[6M]
	b)	Sketch the transfer characteristics of N-channel JFET and explain.	[L2][CO1]	[6M]
4.	a)	List the differences between N-channel JFET and P-channel JFET.	[L2][CO1]	[6M]
	b)	Sketch the transfer characteristics of P-channel JFET.	[L2][CO1]	[6M]
5.	a)	Derive the Drain to Source resistance, Trans-conductance and amplification factor from Characteristics of JFET.	[L4][CO2]	[8M]
	b)	Classify types of MOSFET and Draw their symbols.	[L2][CO1]	[4M]
6.	a)	List the differences between depletion and enhancement MOSFET.	[L1][CO1]	[4M]
	b)	With the help of neat diagram, Explain the operation and characteristics of N-channel Depletion type MOSFET under Depletion mode.	[L2][CO1]	[8M]
7.	a)	With the help of neat diagram, explain the operation of N-channel Depletion type MOSFET under Enhancement mode.	[L2][CO1]	[6M]
	b)	Explain the characteristics of N-channel Depletion type MOSFET under Enhancement mode.	[L2][CO1]	[6M]
8.	a)	Explain construction and working principle of E-only MOSFET.	[L2][CO1]	[8M]
	b)	Sketch the transfer and drain characteristics of E-only MOSFET.	[L2][CO1]	[4M]
9.	a)	Compare the performance of BJT with JFET.	[L2][CO1]	[6M]
	b)	List the types of JFET Biasing and Explain Briefly the setting of Operating Point.	[L1][CO6]	[6M]
10.	a)	Explain voltage divider bias of JFET with neat circuit diagram.	[L4][CO6]	[8M]
	b)	Discuss the merits of the voltage divider bias	[L2][CO1]	[4M]

**Prepared By: ECE Faculty - SIETK**