



**SIDDHARTH GROUP OF INSTITUTIONS:: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code: Electronic Measurements
& Instrumentation (18EC0413)
Year & Sem: III-B.Tech & I Sem

Course & Branch: B.Tech - ECE
Regulation: R18

**UNIT –I
PERFORMANCE CHARACTERISTICS OF INSTRUMENT**

1	a)	What is the difference between accuracy and precision of measurement?	[L2] [CO1]	[2M]
	b)	Define speed of response and fidelity.	[L2] [CO1]	[2M]
	c)	State the limitations of thermocouples.	[L1] [CO1]	[2M]
	d)	Define sensitivity and resolution.	[L1] [CO1]	[2M]
	e)	List the salient features of voltage ohm meter.	[L1] [CO1]	[2M]
2	a)	Explain the construction of multi-range voltmeter & Range extension DC voltmeter.	[L2] [CO2]	[5M]
	b)	A D'Arsonval movement with a full-scale deflection current of 50 μ A and internal resistance of 500 Ω is to be converted into a multirange voltmeter. Define the value of multiplier required for 0-20V, 0-50V, 0-100V.	[L6] [CO2]	[5M]
3	a)	Explain different types of errors that occur in measurements.	[L2][CO1]	[5M]
	b)	Explain about Differential type voltmeter.	[L2] [CO2]	[5M]
4	a)	How do we determine the performance characteristics (static & dynamic) of an instrument?	[L2] [CO1]	[7M]
	b)	Explain the process of calibration.	[L2] [CO1]	[3M]
5	a)	Define sensitivity. Calculate the sensitivity of a 200 μ A meter movement which is to be used as a dc voltmeter.	[L4] [CO1]	[4M]
	b)	Draw and explain solid state DC Voltmeter.	[L2] [CO2]	[6M]
6	a)	With neat sketch explain thermocouple type RF ammeter.	[L2] [CO2]	[5M]
	b)	Explain the fundamental principle of AC voltmeter.	[L2] [CO2]	[5M]
7	a)	Explain with the help of circuit diagram, the construction & working of a series type ohm meter.	[L2] [CO2]	[5M]
	b)	Discuss about basic DC Ammeters.	[L2] [CO2]	[5M]
8		Explain how a multi-meter can be used as a) DC voltmeter & AC volt meter b) DC ammeter & ohmmeter.	[L2] [CO2]	[10M]
9	a)	Explain with the help of circuit diagram the construction & working of a series type ohm meter.	[L2] [CO2]	[5M]
	b)	A shunt type ohmmeter uses a 5 mA basis D'Arsonval movement with an internal resistance of 50 Ω . The battery voltage is 3V. It is desired to modify the circuits by adding appropriate shunt resistance across the movement so that the instrument indicates 5 Ω at the midpoint scale. Calculate: i) The value of shunt resistance. ii) Value of current limiting resistance R1.	[L6][CO2]	[5M]
10	a)	Explain about static characteristics of measuring instrument.	[L2] [CO1]	[5M]
	b)	Define the terms in dynamic characteristics i) Speed of Response ii) Fidelity iii) Lag.	[L2] [CO1]	[5M]

11	a) What are the different dynamic characteristics of an instrument.	[L2] [CO2]	[5M]
	b) Explain about multirange AC voltmeter.	[L2] [CO1]	[5M]

UNIT –II OSCILLOSCOPES

1	a) Mention the standard specifications of a simple CRO.	[L1][CO2]	[2M]
	b) Mention various applications of CRO.	[L1][CO2]	[2M]
	c) What is the principle of CRO?	[L1][CO2]	[2M]
	d) Differentiate between dual beam and dual trace CRO.	[L1][CO2]	[2M]
	e) State the need of a time base generator.	[L1][CO2]	[2M]
2	a) Discuss about important CRT features.	[L2][CO3]	[4M]
	b) Draw the block diagram of a dual beam CRO, explain its operation.	[L4][CO3]	[6M]
3	a) State the various applications of an oscilloscope.	[L2][CO3]	[5M]
	b) Explain the function of trigger circuit.	[L2][CO3]	[5M]
4	a) Explain with the block diagram how the digital frequency and time period can be measured using counter/meter instrument.	[L2][CO3]	[5M]
	b) What are the different types of CRO probes?	[L1][CO3]	[5M]
5	Draw the block diagram of a general-purpose oscilloscope (CRO) and explain function of each block.	[L4][CO3]	[10M]
6	a) Explain the major parts of CRT with a block diagram.	[L2][CO3]	[5M]
	b) Explain Two electron beam (dual beam) CRO.	[L3][CO3]	[5M]
7	a) Draw the block diagram of Delay line circuit and explain its working.	[L2][CO3]	[5M]
	b) With neat sketch explain about vertical amplifier.	[L6][CO3]	[5M]
8	a) Discuss in detail, the construction and working of a Trigger sweep generator.	[L2][CO3]	[5M]
	b) Explain with a diagram how phase can be measured using a Lissajous method	[L3][CO2]	[5M]
9	a) Explain with a diagram how frequency can be measured using a Lissajous method.	[L2][CO2]	[5M]
	b) Briefly discuss about dual trace CRO.	[L2][CO3]	[5M]
10	a) Draw the neat diagrams of horizontal deflection systems and explain briefly about their working.	[L2][CO2]	[6M]
	b) State the standard specifications of a sample CRO.	[L2][CO3]	[4M]
11	a) Describe in details the construction and working of a digital storage oscilloscope.	[L2][CO3]	[5M]
	b) Construct delayed line sweep circuit and explain its operation.	[L6][CO3]	[5M]

UNIT –III
SIGNAL GENERATORS

1	a	Define the basic operating principle of signal generator.	[L1][CO3]	[2M]
	b	Mention the applications of function generator.	[L1][CO3]	[2M]
	c	State the principle of heterodyne wave analyser.	[L1][CO3]	[2M]
	d	Mention the applications of wave analyser.	[L1][CO3]	[2M]
	e	State the principle of basic sine wave generator.	[L1][CO3]	[2M]
2	a)	With the help of block diagram explain the functioning of a conventional standard signal generator.	[L2][CO3]	[5M]
	b)	Write about fixed AF oscillator and variable AF oscillator.	[L2][CO3]	[5M]
3	a)	Draw the block diagram of a function generator and explain its operation.	[L4][CO3]	[5M]
	b)	List the applications of random noise generator.	[L1][CO4]	[5M]
4		With a neat diagram discuss the operation of a pulse generator.	[L4][CO4]	[10M]
5	a)	Discuss in detail about pulse generator .	[L2][CO4]	[5M]
	b)	Explain the method of generating Random noise.	[L2][CO4]	[5M]
6	a)	Explain the working of a standard sweep generator with diagram.	[L2][CO4]	[5M]
	b)	What is sweep generator? Explain in detail.	[L2][CO4]	[5M]
7	a)	With help of a neat sketch, explain the working of any one of wave analyzer.	[L2][CO4]	[5M]
	b)	What is the function of wave analyzer?	[L2][CO4]	[5M]
8	a)	Describe with diagram the operation of a Logic analyzer.	[L2][CO4]	[5M]
	b)	List the application of wave analyzers.	[L1][CO4]	[5M]
9	a)	Draw the circuit diagram and explain the working of a spectrum analyzer.	[L2][CO4]	[5M]
	b)	What is distortion? What does a distortion analyzer measure?	[L2][CO4]	[5M]
10	a)	What is the function of harmonic distortion analyzer?	[L2][CO4]	[5M]
	b)	Describe the diagram with operation of a harmonic distortion analyzer using Wein bridge and frequency selective type.	[L2][CO4]	[5M]
11	a)	With a neat sketch explain the operation of arbitrary waveform generator.	[L2][CO4]	[5M]
	b)	What are the different specifications of arbitrary waveform generator?	[L2][CO4]	[5M]

UNIT –IV
REVIEW OF DC & AC BRIDGES

1	a	What is a bridge? What is the importance of a bridge?	[L1][CO4]	[2M]
	b	What is the balance condition for a basic kelvin bridge?	[L1][CO4]	[2M]
	c	What is meant by q-meter?	[L1][CO4]	[2M]
	d	Draw the circuit of Kelvin's Double Bridge.	[L1][CO4]	[2M]
	e	What are the different errors occurred in bridges?	[L1][CO4]	[2M]
2	a)	Discuss the working principle of Q-meter & its applications.	[L2][CO3]	[5M]
	b)	Write short note on interference & explain noise reduction techniques.	[L2][CO6]	[5M]
3		Explain any Two ac bridges to measure unknown Inductance.	[L2][CO5]	[10M]
4		Explain the operation of Kelvin Bridge and derive necessary equation.	[L2][CO5]	[10M]
5		What is the function of bridge? Draw the Anderson's bridge circuit and derive necessary equations & explain it.	[L2][CO5]	[10M]
6	a)	Explain the Schering bridge circuit & its applications.	[L2][CO5]	[5M]
	b)	An A.C bridge as the following constants Arm AB-capacitor of $0.1\mu\text{F}$ in parallel with $2\text{K}\Omega$ resistor, Arm AD-resistance of $5\text{K}\Omega$, Arm BC capacitor of $0.25\mu\text{F}$, Arm CD-unknown capacitor CX and RX in series f-2KHz. Determine the unknown capacitance and dissipation factor.	[L6][CO5]	[5M]
7	a)	Explain how a Maxwell bridge can be used for measuring an unknown inductance.	[L2][CO5]	[5M]
	b)	What is interference & explain noise reduction techniques.	[L2][CO6]	[5M]
8		Describe the operation of the Wheatstone bridge & derive the expression for current when the bridge is unbalanced.	[L2][CO5]	[10M]
9	a)	Explain how a Maxwell bridge can be used for measuring an unknown inductance.	[L2][CO5]	[5M]
	b)	A Maxwell bridge is used to measure an inductive impedance the bridge constants at balance are $C_1=0.01\mu\text{F}$, $R_1=470\text{K}\Omega$, $R_2=5.1\text{K}\Omega$ and $R_3=100\text{K}\Omega$. Find the series equivalent of the unknown impedance.	[L6][CO5]	[5M]
10	a)	What are the applications of Wheatstone bridge? And list out its limitations.	[L4][CO6]	[5M]
	b)	Describe the operation of the Wheatstone bridge and derive the expression for DC resistance.	[L2][CO5]	[5M]
11	a)	Describe in detail about EMI & EMC with suitable examples.	[L2][CO3]	[5M]
	b)	Explain the working principle & operation of Capacitance & Inductance bridge circuit.	[L2][CO5]	[5M]

UNIT –V
SENSORS AND TRANSDUCERS

1	a	Define sensor and transducers.	[L1][CO5]	[2M]
	b	Mention the disadvantages of LVDT.	[L1][CO5]	[2M]
	c	What is the basic principle involved in piezoelectric transducers?	[L1][CO5]	[2M]
	d	Name one passive and active sensors.	[L1][CO5]	[2M]
	e	What are the merits & demerits of Thermocouple?	[L1][CO5]	[2M]
2	With a neat sketch explain the operation of LVDT. What are the advantages & disadvantages?		[L1][CO5]	[10M]
3	Explain strain gauge for resistance measurement & its applications.		[L2][CO5]	[10M]
4	a)	What are the differences between the active & passive transducers?	[L2][CO5]	[5M]
	b)	Explain the operation of potentiometric transducer.	[L2][CO5]	[5M]
5	a)	Define a transducer.	[L1][CO5]	[3M]
	b)	Explain about any one of transducer to measure displacement.	[L2][CO5]	[7M]
6	a)	Draw the diagram of Resistance Thermometer & explain briefly.	[L2][CO5]	[5M]
	b)	Explain the operation of Thermistor.	[L2][CO5]	[5M]
7	a)	With a neat sketch, explain the operation of piezo-electric transducers in detail.	[L2][CO5]	[5M]
	b)	Briefly discuss about Velocity transducers.	[L2][CO5]	[5M]
8	a)	Discuss about Accelerometer.	[L2][CO5]	[5M]
	b)	Explain about vibration.	[L2][CO5]	[5M]
9	a)	Discuss about Sensors and Transducers.	[L1][CO5]	[5M]
	b)	How to convert linear variable displacement into electrical voltage using transducer.	[L2][CO5]	[5M]
10	Describe the operation of i) resistive transducers ii) capacitive transducers iii) Inductive transducers.		[L2][CO5]	[10M]
11	Explain the operation of Thermocouple.		[L2][CO5]	[10M]

Prepared by:

1. J.JHANSI

Assistant Professor/ECE

2. DR.P.G.KUPPASWAMY

Professor/ECE

3. D.JITHENDRA REDDY

Assistant Professor/ECE