



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)**

**Siddharth Nagar, Narayanavanam Road – 517583**

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code:** Switching Theory and Logic Design  
(20EC0403)

**Course & Branch:** B.Tech & ECE

**Year & Sem:** II B.Tech & I Sem

**Regulation:** R20

**UNIT-I**

**BOOLEAN ALGEBRA AND LOGIC GATES**

1.	a) Define Boolean Algebra and list the postulates used in it.	[L1][CO1]	[6M]
	b) State and prove any four Boolean theorems of Boolean algebra.	[L3][CO1]	[6M]
2.	State and prove the following Boolean laws: i) Commutative                      ii) Associative                      iii) Distributive	[L3][CO1]	[12M]
3.	a) Prove De Morgan's theorems using Perfect Induction Method. b) Simplify the given Boolean expression to a sum of 3 terms. $A'C'D' + AC' + BCD + A'CD' + A'BC + AB'C'$	[L3][CO1] [L4][CO2]	[6M] [6M]
4.	Simplify the following Boolean expressions: i) $(X'+Z')(X+Y'+Z')$ ii) $(X'Y' + Z)' + Z + XY + WZ$ iii) $A'B(D' + C'D) + B(A + A'CD)$ iv) $(A'+C)(A'+C')(A+B+C'D)$	[L4][CO2]	[12M]
5.	a) Simplify the following Boolean functions to minimum number of literals: i) $F_1 = (a + b)' (a' + b')'$ ii) $F_2 = y(wz' + wz) + xy$	[L4][CO2]	[6M]
	b) State and prove Consensus Theorem and Absorption Theorem of Boolean algebra.	[L3][CO1]	[6M]
6.	Identify the Dual of the following Boolean expressions. (i) $AB'C+AB'D+A'B'$ (ii) $A'B'C+ABC'+A'B'C'D$	[L2][CO1]	[12M]
7.	Find the complement of the following Boolean expressions. i) $B'C'D + (B + C + D)' + B'C'D'E$ ii) $AB + (AC)' + (AB + C)$ iii) $A'B'C' + A'BC' + AB'C' + ABC'$ iv) $AB + (AC)' + AB'C$	[L3][CO1]	[12M]
8.	a) Express the following functions in Sum of Minterms and Product of Maxterms. i) $F_1(A,B,C,D) = B'D + A'D + BD$ ii) $F_2(x,y,z) = (xy + z)(xz+y)$	[L2][CO1]	[6M]
	b) Express the following Boolean functions into Canonical form. i) $F_1=AB+BC+CA$ ii) $F_2= XY+Z+YZ+XYZ$	[L2][CO1]	[6M]
9.	a) Simplify the given Boolean function, F to minimum number of literals using Boolean algebra. $F=XY'Z + X'Y'Z + W'XY + WX'Y + WXY$	[L4][CO1]	[6M]
	b) Draw the logic diagram for the simplified expression of the above using AOI logic.	[L1][CO2]	[6M]
10	a) List the different Boolean expressions for Two binary Variables.	[L1][CO1]	[6M]
	b) What are Universal Gates? Give their truth tables and Graphic symbols.	[L1][CO1]	[6M]

**UNIT –II**  
**GATE – LEVEL MINIMIZATION**

1.	a) List the steps involved in simplification of K-Map.	[L1][CO1]	[6M]
	b) Simplify the Boolean expression, $F=A'+AB+ABD'+AB'D'+C'$ using Four Variable K-Map and draw the logic diagram using AOI.	[L4][CO2]	[6M]
2.	a) Simplify the Boolean function using Five Variable K-Map. $F=\sum m(0, 1,2, 4, 7, 8, 12, 14, 15, 16, 17, 18, 20, 24, 28, 30, 31)$	[L4][CO2]	[6M]
	Apply the K-Map technique to simplify the given Boolean expression in POS form using K-Map $F(A,B,C,D) = \Sigma(1,2,4,5,9,12,13,14)$	[L4][CO2]	[6M]
3.	a) Analyze the following Boolean function for minimal POS form using K-Map $F(X,Y,Z) = X'YZ + XY'Z' + XYZ + XYZ'$	[L4][CO4]	[6M]
4.	b) Deduce the given Boolean function using K-Map. $F(A,B,C,D)=\sum(1,3,7,11,15)+d(0,2,5)$	[L4][CO2]	[6M]
	a) Simplify using K-Map and express the reduced expression in SOP and POS form. $F = \Sigma m (0, 6, 8, 13, 14) + \Sigma d (2, 4, 10)$	[L4][CO2]	[6M]
5.	b) Develop the logic diagram for the following Boolean function using NAND and NOR gates. $Y=(AB'+A'B)(C+D')$ .	[L3][CO5]	[6M]
	a) Explain the disadvantage of K-Map method of reducing a Boolean function and how to overcome it.	[L2][CO1]	[6M]
6.	Simplify the following expression using K-Map and realize with NAND and NOR gates. $F = \pi M (1, 2, 3, 8, 9, 10, 11, 14). \pi d (7,15)$	[L4][CO2]	[12M]
7.	a) Explain the structure of Ex-OR gate by K-Map using 4 Variable.	[L2][CO1]	[6M]
	b) Explain the Quine-Mc Cluskey method of minimizing the Boolean functions. Also mention its limitation.	[L2][CO1]	[6M]
8.	Simplify the following Boolean function by using Tabulation method. $F = \Sigma (0, 1,2,8,10,11,14, 15)$	[L4][CO2]	[12M]
9.	Determine the prime-implicants, essential prime implicants and simplified expression for the following function. $F ( w,x,y,z)= \Sigma (1,3,4,5,9,10,11) + \Sigma d( 6,8 )$	[L4][CO2]	[12M]
10.	Simplify the following Boolean function using Tabulation method, and realize its logic circuit with NAND gates and NOR gates. $Y(A, B,C,D) = \Sigma(1,3,5,8,9,11,15)$	[L4][CO2]	[12M]

**UNIT –III**  
**COMBINATIONAL LOGIC**

1	a) Define Combinational Circuit and Explain the analysis procedure of a combinational logic circuit using suitable example.	[L2][CO1]	[6M]
	b) Explain the procedure of designing a combinational logic circuit with an example.	[L2][CO1]	[6M]
2	a) Define a Full Adder and realize it with use of truth table.	[L3][CO5]	[6M]
	b) Design a Full Subtractor using truth table.	[L3][CO5]	[6M]
3	a) Design a 4 bit parallel adder/ Subtractor using full adders.	[L3][CO5]	[6M]
	b) Design & implement a 4-bit Binary-to-Gray code converter.	[L3][CO4]	[6M]
4	a) Design a 4 bit Binary-to-BCD code converter.	[L3][CO4]	[6M]
	b) Construct a BCD Adder-circuit using 4-bit binary adders.	[L3][CO5]	[6M]
5	Explain Binary Multiplier with an example.	[L2][CO3]	[12M]
6	a) Explain a 2-bit Magnitude comparator and write down its design procedure.	[L2][CO3]	[6M]
	b) Design & implement Full Adder using Decoder.	[L3][CO4]	[6M]
7	a) Define Decoder and explain in detail about a 2 to 4 line binary decoder.	[L2][CO5]	[6M]
	b) Draw the circuit for 3 to 8 decoder and explain.	[L2][CO5]	[6M]
8	a) Illustrate the following Boolean functions using decoder and OR gates. $F1(A,B,C,D)=\sum(2,4,7,9)$ $F2(A,B,C,D)=\sum(10,13,14,15)$	[L3][CO5]	[6M]
	b) What is an encoder? Design an octal to binary encoder.	[L3][CO6]	[6M]
9	a) Define Multiplexer. Construct 4:1 multiplexer with logic gates and truth table.	[L3][CO4]	[6M]
	b) Represent the following Boolean function with an 8:1 multiplexer. $F(A,B,C,D) = A'BD'+ACD+B'CD+A'C'D.$	[L2][CO4]	[6M]
10	a) What is Demultiplexer? Design an 1:8 demultiplexer using two 1:4 demultiplexer.	[L3][CO4]	[6M]
	b) Design a 32:1 Mux using two 16:1 MUXs and one 2:1 MUX.	[L3][CO4]	[6M]

**UNIT –IV**  
**SYNCHRONOUS SEQUENTIAL LOGIC**

1.	a) Define a sequential logic circuit and sketch its block diagram.	[L1][CO1]	[4M]
	b) Differentiate between combinational and sequential circuits.	[L2][CO1]	[4M]
	c) Differentiate between synchronous and asynchronous sequential circuits.	[L2][CO1]	[4M]
2.	a) Define Latch and list different types of Latches.	[L1][CO1]	[4M]
	b) Define Flip-Flop. What are the different types of Flip-Flops?	[L1][CO1]	[4M]
	c) Explain the working principle of RS Flip-Flop with the help of logic diagram and give its Characteristic Table and Graphic symbol.	[L2][CO3]	[4M]
3.	a) With the help of logic diagram, obtain the characteristic table of D & T Flip-Flops. Also draw their graphic symbols.	[L2][CO3]	[6M]
	b) Explain the working principle of JK Flip-Flop in detail. Also give its characteristic equation, Graphic symbol and Excitation equation.	[L2][CO3]	[6M]
4.	a) Derive the characteristic equations for D & T Flip-Flops.	[L3][CO2]	[6M]
	b) Convert SR flip flop into JK Flip-Flop. Draw and explain its logic diagram.	[L2][CO4]	[6M]
5.	a) Design T Flip Flop using JK Flip-Flop and explain its logic diagram.	[L3][CO5]	[6M]
	b) Explain the steps involved in analysis of the clocked sequential circuits.	[L2][CO3]	[6M]
6.	a) Derive the excitation tables for SR, D, JK, and T Flip-Flops.	[L3][CO3]	[6M]
	b) Define a Shift register and explain its types.	[L2][CO1]	[6M]
7.	Design a 4 bit Decade counter.	[L4][CO6]	[12M]
8.	a) Define a counter and design a 4-bit Ripple counter.	[L1][CO6]	[8M]
	b) Explain in brief about a 2-bit synchronous up-counter.	[L2][CO6]	[4M]
9.	What is a synchronous counter? Design a 3-bit synchronous up/down counter.	[L4][CO6]	[12M]
10.	Explain about the following counters in detail. i) Ring counter                      ii) Johnson counter	[L2][CO3]	[12M]

**UNIT –V**  
**FINITE STATE MACHINES AND PROGRAMMABLE MEMORIES**

1.	a) Define Mealy model and explain it with neat diagram.	[L1][CO1]	[4M]																																												
	b) Define Moore model. Explain it with neat diagram.	[L1][CO1]	[4M]																																												
	c) Distinguish between Mealy & Moore machines.	[L2][CO1]	[4M]																																												
2.	Explain the following related to sequential circuits with suitable examples: a) State diagram                      b) State table                      c) State assignment	[L2][CO1]	[12M]																																												
3.	Derive the simplified sequential circuit for the following state table.	[L3][CO6]	[12M]																																												
	<table border="1" style="margin-left: 40px;"> <thead> <tr> <th rowspan="2">PS</th> <th colspan="2">Next State</th> <th colspan="2">Output</th> </tr> <tr> <th>X=0</th> <th>X=1</th> <th>X=0</th> <th>X=1</th> </tr> </thead> <tbody> <tr> <td>A</td> <td>a</td> <td>b</td> <td>0</td> <td>0</td> </tr> <tr> <td>B</td> <td>c</td> <td>d</td> <td>0</td> <td>0</td> </tr> <tr> <td>C</td> <td>a</td> <td>d</td> <td>0</td> <td>0</td> </tr> <tr> <td>D</td> <td>e</td> <td>f</td> <td>0</td> <td>1</td> </tr> <tr> <td>E</td> <td>a</td> <td>f</td> <td>0</td> <td>1</td> </tr> <tr> <td>F</td> <td>g</td> <td>f</td> <td>0</td> <td>1</td> </tr> <tr> <td>G</td> <td>a</td> <td>f</td> <td>0</td> <td>1</td> </tr> </tbody> </table>			PS	Next State		Output		X=0	X=1	X=0	X=1	A	a	b	0	0	B	c	d	0	0	C	a	d	0	0	D	e	f	0	1	E	a	f	0	1	F	g	f	0	1	G	a	f	0	1
	PS				Next State		Output																																								
				X=0	X=1	X=0	X=1																																								
	A			a	b	0	0																																								
	B			c	d	0	0																																								
	C			a	d	0	0																																								
	D			e	f	0	1																																								
E	a	f	0	1																																											
F	g	f	0	1																																											
G	a	f	0	1																																											
4.	Determine the minimal state equivalent of the state table given.	[L3][CO6]	[12M]																																												
	<table border="1" style="margin-left: 40px;"> <thead> <tr> <th rowspan="2">PS</th> <th colspan="2">Next State</th> <th colspan="2">Output</th> </tr> <tr> <th>X=0</th> <th>X=1</th> <th>X=0</th> <th>X=1</th> </tr> </thead> <tbody> <tr> <td>A</td> <td>a</td> <td>b</td> <td>0</td> <td>0</td> </tr> <tr> <td>B</td> <td>c</td> <td>g</td> <td>0</td> <td>1</td> </tr> <tr> <td>C</td> <td>a</td> <td>d</td> <td>0</td> <td>0</td> </tr> <tr> <td>D</td> <td>e</td> <td>f</td> <td>0</td> <td>1</td> </tr> <tr> <td>E</td> <td>c</td> <td>g</td> <td>0</td> <td>1</td> </tr> <tr> <td>F</td> <td>a</td> <td>b</td> <td>0</td> <td>0</td> </tr> <tr> <td>G</td> <td>E</td> <td>f</td> <td>0</td> <td>1</td> </tr> </tbody> </table>			PS	Next State		Output		X=0	X=1	X=0	X=1	A	a	b	0	0	B	c	g	0	1	C	a	d	0	0	D	e	f	0	1	E	c	g	0	1	F	a	b	0	0	G	E	f	0	1
	PS				Next State		Output																																								
				X=0	X=1	X=0	X=1																																								
	A			a	b	0	0																																								
	B			c	g	0	1																																								
	C			a	d	0	0																																								
	D			e	f	0	1																																								
E	c	g	0	1																																											
F	a	b	0	0																																											
G	E	f	0	1																																											
5.	Explain in brief about Programmable Read Only Memory (PROM) with a suitable example.	[L2][CO2]	[12M]																																												
6.	a) Compare ROM and RAM.	[L2][CO1]	[6M]																																												
	b) Classify various types of RAMs.	[L2][CO1]	[6M]																																												
7.	Illustrate the PLA for the following Boolean function. (i) $F_1 = \sum m(0,1,3,4)$ (ii) $F_2 = \sum m(0,1,2,3,4,5)$ .	[L3][CO5]	[12M]																																												
8.	Illustrate PLA for the following Boolean function. $F_1(A,B,C) = \sum m(3,5,7)$ $F_2(A,B,C) = \sum m(4,5,7)$	[L3][CO5]	[12M]																																												
9.	Illustrate the PAL for the following Boolean functions. (i) $F(A,B,C,D) = \sum m(2,3,8,9,10,12,13)$ (ii) $G(A,B,C,D) = \sum m(1,3,4,6,9,12,14)$	[L3][CO5]	[12M]																																												
10.	Illustrate the PAL for the following Boolean functions. (i) $A(w,x,y,z) = \sum m(0,2,6,7,8,9,12,13)$ (ii) $B(w,x,y,z) = \sum m(0,2,6,7,8,9,12,13,14)$	[L3][CO5]	[12M]																																												