



**SIDDHARTH GROUP OF INSTITUTIONS:: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code: 20EC0446-Analog Electronic circuits
Year & Sem: II-B.Tech & I-Sem

Course & Branch: B.Tech EEE
Regulation: R20

**UNIT –I
FEEDBACK AMPLIFIERS**

- | | | | |
|----|--|-----------|-------|
| 1 | a) What is feedback Amplifier?.Illustrate the basic concept of Feedback amplifier with suitable block diagram | [L3][CO1] | [6M] |
| | b) Explain in detail about basic Amplifiers used in Feedback amplifiers. | [L2][CO1] | [6M] |
| 2 | a) Interpret Feedback amplifier topologies with necessary diagram. | [L3][CO1] | [6M] |
| | b) List the characteristics of negative feedback amplifiers. | [L1][CO1] | [6M] |
| 3 | a) Prove that bandwidth of an amplifier can be extended by using negative feedback amplifier. | [L5][CO1] | [6M] |
| | b) An amplifier has voltage gain with feedback of 100. If the gain without feedback changes by 20% and the gain with feedback should not vary more than 2%, solve the value of open-loop gain, A and feedback ratio, β . | [L3][CO4] | [6M] |
| 4 | Summarize the expressions of Gain, input and output resistances for a Voltage Shunt FBA with necessary derivations. | [L2][CO4] | [12M] |
| 5 | Summarize the expressions of Gain, input and output resistances for a Voltage Series FBA with necessary derivations.. | [L2][CO4] | [12M] |
| 6 | a) Determine the input and output resistances of Current Shunt feedback amplifier. | [L3][CO1] | [6M] |
| | b) An amplifier has midband voltage gain of 1000 with $F_L = 50\text{Hz}$, $F_H = 50\text{KHz}$, if 5% of feedback is applied then determine F_L , F_H . | [L3][CO3] | [6M] |
| 7 | Determine the voltage gain, input and output impedance with feedback for voltage series having $A = -100$, $R_i = 10\text{kohm}$, $R_o = 10\text{kohm}$ for feedback of i) $\beta = -0.1$ ii) $\beta = -0.5$ | [L3][CO3] | [12M] |
| 8 | Summarize the expressions of Gain, input and output resistances for a Current Series FBA with necessary derivations. | [L2][CO4] | [12M] |
| 9 | a) Compare positive feedback and negative feedback amplifiers | [L2][CO2] | [6M] |
| | b) Show that negative feedback reduces gain of an Amplifier. | [L1][CO1] | [6M] |
| 10 | a) Compare and Contrast the various types of feedback amplifiers. | [L2][CO1] | [6M] |
| | b) An amplifier has open loop gain 1000 and feedback ratio of 0.04, if the open loop gain changes by 10% due to temperature, find the percentage change in the gain of the amplifier feedback. | [L3][CO3] | [6M] |

Prepared by Dr R Gomalavalli,
professor, ECE,SIETK

UNIT –II
OSCILLATORS

- | | | | |
|---|---|------------|--------------|
| 1 | a) What is an Oscillator? Explain the principle of operation of an oscillator. | [L2][CO1] | [6M] |
| | b) Illustrate the Barkhausen criterion condition for oscillation with suitable diagram. | [L2][CO1] | [6M] |
| 2 | a) Interpret the various types of oscillators. | [L3][CO1] | [6M] |
| | b) Determine the frequency of oscillations when a RC phase shift oscillator has $R=100\text{ k}\Omega$, $C=0.01\text{ }\mu\text{F}$ and $R_C = 2.2\text{ K}\Omega$. | [L3][CO4] | [6M] |
| 3 | a) Determine the condition for sustained oscillations for an RC phase shift Oscillator with necessary circuit diagrams. | [L3][CO2] | [6M]
[6M] |
| | b) Design a RC phase shift oscillator to generate 5 KHz sine wave with 20V peak to peak amplitude. Draw the designed circuit. Assume $h_{fe} = 150$. | [L3][CO3] | |
| 4 | a) Explain the working principle of Wein-bridge oscillator using BJT and derive its frequency expression for sustained oscillations. | [L2][CO5] | [6M]
[6M] |
| | b) In a Wein-bridge oscillator, if the value of R is $100\text{ K}\Omega$, and frequency of oscillation is 10 KHz, estimate the value of capacitor C. | [L2][CO4] | |
| 5 | a) Compare RC phase shift oscillator and Wein-bridge oscillator. | [L2][CO2] | [6M] |
| | b) Derive the generalized equation of a LC Oscillator with its circuit. | [L3][CO6] | [6M] |
| 6 | a) Draw the circuit diagram of Hartley oscillator using BJT and derive the expression for frequency of oscillations. | [L3] [CO1] | [6M] |
| | b) A In a transistorized Hartley oscillator, the two inductances are 2 mH and $20\text{ }\mu\text{H}$ while the frequency is to be changed from 950 KHz to 2050 KHz. Find the range over which the capacitor is to be varied. | [L3][CO4] | [6M] |
| 7 | Draw the circuit diagram of Colpitts oscillator using BJT and derive the | [L3][CO1] | [6M] |
| | a) expression for frequency of oscillations.
Colpitts oscillator is designed with $C_1 = 100\text{ pF}$ and $C_2 = 7500\text{ pF}$. The | | |
| | b) inductance is variable. Identify the range of inductance values, if the frequency of oscillation is to vary between 950 KHz to 2050 KHz. | [L2][CO4] | [6M] |
| 8 | a) Compare piezoelectric effect and inverse piezoelectric effect with a neat diagram | [L2] [C06] | [4M] |
| | b) Explain in detail about the crystal oscillator and derive the expression for its frequency of oscillation. | [L2][CO1] | [8M] |
| 9 | a) Summarize the difference between Hartley and Colpitts oscillators. | [L2][CO4] | [6M] |
| | b) In the Colpitts oscillator, $C_1 = 0.2\text{ }\mu\text{F}$ and $C_2 = 0.02\text{ }\mu\text{F}$. If the frequency of oscillation is 10kHz, Examine the value of inductor | [L3][CO4] | [6M] |
| 1 | a) Summarize the difference between Colpitts and Crystal oscillators. | [L2][CO4] | [6M] |
| 0 | b) Explain the concept of stability in Oscillators in detail. | [L2][CO6] | [6M] |

UNIT –III
OPERATIONAL AMPLIFIER

1	a) Explain the basic information and pin configuration of an op-amp b) List out the ideal characteristics of an operational amplifier.	[L2] [CO1] [L1][CO3]	[6M] [6M]
2	a) Discuss the electrical characteristics of an op-amp in detail. b)What is level translator? Explain the necessity of level translator stage in cascading differential amplifiers.	[L2][CO1] [L2][CO2]	[6M] [6M]
3	a) Draw the equivalent circuit diagram of op-amp and derive the expression for gain of inverting amplifier. b)Design an inverting amplifier with gain $A= 10$	[L3][CO5] [L3][CO5]	[6M] [6M]
4	a)) Derive the voltage gain of non-inverting op-amp. b) What is voltage follower? What are its features and applications?	[L3][CO5] [L1][CO1]	[6M] [6M]
5	a) Differentiate inverting and noninverting op-amp. b) Design a noninverting amplifier with gain $A=21$.	[L2][CO1] [L3][CO5]	[6M] [6M]
6	a) Estimate the gain of a Differential amplifier b) Define the terms CMRR, common mode gain, differential mode gain.	[L4][CO2] [L1][CO2]	[6M] [6M]
7	a) Explain DC characteristics of op-amp b) What is frequency compensation and explain how the frequency response is varied with respect to Compensation network?	[L2][CO3] [L2][CO6]	[6M] [6M]
8	a) Illustrate the following terms with neat diagram i)Input bias current ii)Input offset current b)Explain briefly i)virtual ground concept b)Thermal Drift	[L3][CO1] [L2][CO1]	[6M] [6M]
9	a)Draw and explain frequency response of practical op-amp b)Define the terms drift,offset voltage,PSRR,offset current	[L2][CO1] [L1][CO2]	[6M] [6M]
10	c) a)Explain the term slew rate and illustrate the importance in op-amp circuits? d) b)An op-amp has a slew rate of $2V/\mu s$. What is the maximum frequency of an output sinusoidal its peak value of 5V at which the distortion sets in due to the slew rate limitation	[L2][CO3] [L1][CO4]	[6M] [6M]

Prepared by Dr R Gomalavalli,
professor, ECE,SIETK

UNIT –IV
APPLICATIONS OF THE OP-AMP

- | | | | |
|-----------|---|-----------|-------|
| 1 | a) Design and explain the operation of inverting summing amplifier. | [L3][CO3] | [6M] |
| | b) Design an inverting adder circuit using an op-amp to get the output expression as $V_o = -(0.1V_1 + V_2 + 10V_3)$, Where V_1, V_2 and V_3 are the inputs. | [L3][CO3] | [6M] |
| 2 | a) Design and explain the operation of non-inverting summing amplifier. | [L3][CO3] | [6M] |
| | b) The op-amp non-inverting summing circuit has the following parameters $V_{CC} = +15\text{ V}$, $V_{EE} = -15\text{ V}$, $R = R_1 = 1\text{ k}\Omega$, $R_f = 2\text{ k}\Omega$, $V_1 = +2\text{ V}$, $V_2 = -3\text{ V}$, $V_3 = +4\text{ V}$. Determine the output voltage V_o . | [L3][CO3] | [6M] |
| 3 | a) Draw the circuit of a subtractor using op-amp and derive the expression for voltage gain. | [L3][CO1] | [6M] |
| | b) Draw an op-amp circuit whose output is $V_o = (V_3 + V_4) - (V_1 + V_2)$. | [L3][CO1] | [6M] |
| 4 | a) Explain the operation of differentiator using op-amp with a neat circuit diagram. | [L3][CO5] | [6M] |
| | b) Draw the input-output waveforms and frequency response of differentiator. | [L3][CO1] | [6M] |
| 5 | a) Explain the operation of integrator using op-amp with a neat circuit diagram. | [L3][CO5] | [6M] |
| | b) Draw the input-output waveforms and frequency response of integrator. | [L3][CO1] | [6M] |
| 6 | a) Explain sample and hold circuit using op-amp. | [L2][CO1] | [6M] |
| | b) Design a differentiator to differentiate an input signal that has $f_{\max} = 100\text{ Hz}$. | [L3][CO5] | [6M] |
| 7 | a) Draw a neat circuit of astable multivibrator using op-amp and explain operation with waveforms. | [L2][CO2] | [6M] |
| | b) Define the duty cycle. Identify the percentage of duty cycle if $T_{\text{on}} = 0.6\text{ msec}$, $T_{\text{off}} = 0.4\text{ msec}$ | [L3][CO4] | [6M] |
| 8 | a) Derive the equation for frequency of oscillation of astable multivibrator using op-amp. | [L3][CO4] | [6M] |
| | b) Calculate the frequency of oscillation for an astable multivibrator having $R_2 = 10\text{ kohm}$, $R_1 = 8.6\text{ kohm}$, $R_f = 100\text{ kohm}$ and $C = 0.01\text{ }\mu\text{F}$. | [L4][CO4] | [6M] |
| 9 | a) Explain the operation of monostable multivibrator using op-amp, with a neat circuit and its waveforms | [L2][CO2] | [6M] |
| | b) Derive the equation for pulse width of the monostable multivibrator using op-amp. | [L3][CO4] | [6M] |
| 10 | Explain the operation of triangular wave generator using op-amp, with a neat circuit diagram and its waveforms. | [L2][CO3] | [12M] |

Prepared by Dr R Gomalavalli,
professor, ECE, SIETK

UNIT –V
ACTIVE FILTERS AND CONVERTERS USING OP-AMP

1	a) Define active filter and give its characteristics.	[L4][CO2]	[6M]
	b) Explain the first order low pass butter worth filter with a neat circuit diagram.	[L2][CO2]	[6M]
2	a) Draw the frequency response of filters .	[L3][CO1]	[6M]
	b) Explain the first order high pass butter worth filter with a neat circuit diagram.	[L2][CO2]	[6M]
3	Design a lowpass filter at a cut-of frequency of 15.9kHz with passband gain of 1.5 and draw the frequency response .	[L3][CO3]	[12M]
4	Design a highpass filter at a cut-of frequency of 10kHz with passband gain 1.5 and draw the frequency response .	[L3][CO3]	[12M]
5	a) Explain the weighted resistor DAC with a neat diagram.	[L2][CO2]	[6M]
	b) An 8-bit Analog to Digital converter has a supply voltage of +12 volts. Calculate: (i) The voltage step size for LSB. (ii) The value of analog input voltage for a digital output of 01001011.	[L4][CO4]	[6M]
6	a) Explain in detail about R-2R DAC with a neat diagram.	[L2][CO3]	[6M]
	b). The basic step of a 9 bit DAC is 10.3 mV. If “000000000” represents 0 V. What output is produced if the input is “101101111”?	[L1][CO4]	[6M]
7	a) Draw the circuit diagram of inverted R-2R DAC and explain its operation.	[L2][CO2]	[6M]
	b) Design an inverted R-2R ladder DAC for digital input word 001.	[L3][CO4]	[6M]
8	a) Explain about the flash type ADC using op-amp.	[L2][CO1]	[6M]
	b) Summarize the truth table for a flash type opamp ADC using 8 by 3 priority encoder.	[L2][CO4]	[6M]
9	Draw the circuit diagram of Dual Slope ADC and explain its working with neat sketches	[L2][CO2]	[12M]
10	Discuss the parameters specifications of DAC/ADC .	[L2][CO1]	[12M]

**Prepared by Dr R Gomalavalli,
professor, ECE,SIETK**