



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** Digital Logic Design(18CS502 )

**Course & Branch:** B.Tech - CSE

**Year & Sem:** I-B.Tech & II-Sem

**Regulation:** R18

**UNIT –I**

**Binary Systems, Boolean Algebra & Logic Gates**

**2 MARKS QUESTIONS**

1. What are the characteristics of Digital Systems. (2M)
2. Convert  $(15)_{10}$  to Binary (2M)
3. Explain about Diminished Radix complement (2M)
4. What is meant by parity bit? (2M)
5. Define duality property. (2M)
6. Define binary logic? (2M)
7. Which gates are called as the universal gates? What are its advantages? (2M)
8. State the associative property of Boolean algebra. (2M)
- 9 Explain classification of Number system (2M)
10. What is a prime implicate? (2M)

**10 MARKS QUESTIONS**

- 1 a) Convert the following numbers (L5) (5M)
  - i)  $(163.789)_{10}$  to Octal number
  - ii)  $(11001101.0101)_2$  to base-8 and base-4
  - iii)  $(4567)_{10}$  to base2
  - iv)  $(4D.56)_{16}$  to Binary
- b) Subtract  $(111001)_2$  from  $(101011)$  using 1's complement? (L5) (5M)
2. a) Represent the decimal number 3452 in i)BCD ii)Excess-3 (L5) (5M)
  - b) perform  $(-50)-(-10)$  in binary using the signed-2's complement (L4) (2M)
  - c) Determine the value of base x if  $(211)_x = (152)_8$  (L4) (2M)
3. a) Convert the following numbers (L5) (3M)
  - i)  $(250.5)_{10} = ( )_2$
  - ii)  $(673.23)_{10} = ( )_8$
  - iii)  $(101110.01)_2 = ( )_8$
- b) Convert the following to binary and then to gray code  $(AB33)_{16}$  (L2) (2M)

- c) Perform the following Using BCD arithmetic  $(7129)_{10} + (7711)_{10}$  (L3) (3M)
4. Explain the Binary codes with examples? (L5) (10M)
5. a) What is Digital System? Characteristics of digital systems. (L5)(5M)
- b) Explain the difference between analog and digital systems (L5) (5M)
6. a) Design the circuit by Using NAND gates  $F = ABC' + DE + AB'D'$  (L5) (5M)
- b) Simplify and implementation the following SOP function using NOR gates (L3) (5M)
- $F(A,B,C,D) = \sum m(0,1,4,5,10,11,14,15)$
7. Convert the following (L2) (5M)
- a)  $(1AD)_{16} = ( )_{10}$  b)  $(453)_8 = ( )_{10}$  c)  $(10110011)_2 = ( )_{10}$  d)  $(5436)_{10} = ( )_3$ .
8. a) Explain binary to Gray & Gray to binary conversion with example? (L5) (5M)
- b) State and Explain the DeMorgan's Theorem and Consensus Theorem (L3) (5M)
- 9) Convert the following numbers (L2) (5M)
- i)  $(615)_{10} = ( )_{16}$  ii)  $(214)_{10} = ( )_8$  iii)  $(0.8125)_{10} = ( )_2$
- iv)  $(658.825)_{10} = ( )_8$  v)  $(54)_{10} = ( )_2$
- 10) Explain the Excess-3 code? Write about Error correction & Detection? (L5) (5M)

**UNIT –II****Gate Level Minimization****2 MARKS QUESTIONS**

1. What is meant by karnaugh map or K-Map method? (2M)
2. Define Pair, Quad, and Octet (2M)
3. What are called don't care conditions? (2M)
4. What are the 2 forms of Boolean expression? (2M)
5. Define Minterm & Maxterm (2M)
6. Explain SOP and POS form (2M)
7. Explain Canonical SOP form (2M)
8. State De Morgan's theorem (2M)
9. Explain demorgan's law (2M)
10. What is an essential prime implicant? (2M)

**10 MARKS QUESTIONS**

1. Simplify the Boolean expression using K-MAP (L5) (10M)  

$$F(A,B,C,D,E) = \sum m(0,1,4,5,16,17,21,25,29)$$
2. Simplify the Boolean expression using K-MAP (L5) (10M)  

$$F(A,B,C,D) = \sum m(1,2,3,8,9,10,11,14) + d(7,15)$$
3. Simplify the Boolean expression using K-map and implement using NAND gates  

$$F(A,B,C,D) = \sum m(0,2,3,8,10,11,12,14)$$
 (L4) (10M)
4. Simplify the Boolean expressions to minimum number of literals
  - i)  $(A + B)(A + C')(B' + C')$  (L3) (3M)
  - ii)  $AB + (AC)' + AB'C (AB + C)$  (L3)(4M)
  - iii)  $(A+B)' (A'+B')'$  (L5) (3M)
5. Reduce the expression  $f(x,y,z,w) = \pi M(0,2,7,8,9,10,11,15)$  .d (3,4) using K-Map? (L5) (10M)
6. Simplify the Boolean expression using K-map? (L5) (10M)  

$$F(A,B,C,D,E) = \sum m(0,2,4,6,9,11,13,15,17,21,25,27,29,31)$$

7. Obtain the a) SOP b) POS expression for the function given below (L5) (10M)  
 $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$
8. a) Simplify the Boolean expressions to minimum number of literals (L4) (5M)  
 i)  $X' + XY + XZ' + XYZ'$     ii)  $(X+Y)(X+Y')$
9. b) Obtain the Complement of Boolean Expression (L4) (5M)  
 i)  $A+B+A'B'C$     ii)  $AB + A(B+C) + B'(B+D)$
10. Determine the minimal sum of product form of (L4) (5M,5M)  
 a)  $f(w,x,y,z) = \sum m(4,5,7,12,14,15) + d(3,8,10)$   
 b)  $F(A,B,C,D) = \pi M(0,3,5,6,8,12,15)$

**UNIT –III**  
**Combinational Logic**

**2 MARKS QUESTIONS**

1. Define combinational logic. (2M)
2. Explain the design procedure for combinational circuits (2M)
3. Define Half adder and full adder (2M)
4. What is Decoder (2M)
5. Define Encoder? (2M)
6. Construct 2:1 multiplexer? (2M)
7. Define subtractor? (2M)
8. Difference between encoder and decoder (2M)
9. Define de-multiplexer? (2M)
10. Explain Applications of Multiplexer (2M)

**10 MARKS QUESTIONS**

1. Implement BCD to 7-segment decoder for cathode type using 4:16 decoder? (L5) (10M)
2. A) Implement the following Boolean function using 8:1 multiplexer (L5) (5M)  

$$F(A, B, C, D) = A'BD' + ACD + A'C'D + B'CD$$
 B) Explain about Full Adder? (L2) (5M)
3. A) Explain about 2-bit Magnitude Comparator? (L2) (5M)  
 B) Explain Full binary subtractor in detail? (L2) (5M)
4. Design the combinational circuit binary to gray code? (L5) (10M)
5. A) Explain about Binary Multiplier ? (L2) (5M)  
 B) What is memory decoding? Explain about the construction of 4 X 4 RAM ? (L2) (5M)
6. A) Implement the following Boolean function using 8:1 multiplexer (L5)(5M)  

$$F(A,B,C,D) = \sum m (0,1,2,5,7,8,9,14,15)$$
 B) Explain about Decimal Adder? (L2) (5M)
7. A) Design a 4 bit adder-subtractor circuit and explain the operation in detail? (L5) (5M)  
 B) Explain the functionality of a Multiplexer? (L2) (5M)

8. Explain The Half adder? Implement the full adder using two half adders (L5) (10M)
9. A) Design a 4 bit binary parallel subtractor and the explain operation in detail? (L5) (5M)  
B) Design the combinational circuit of 4 Bit Parallel Adder? (L5) (5M)
10. a) What is the truth table of Half-subtractor? (L1) (2M)  
b) Define priority encoder? (L1) (2M)  
c) Explain the design procedure for combinational circuit? (L1) (2M)  
d) Design 4 bit parallel Adder? (L5) (2M)  
e) Define Multiplexer and applications of multiplexer? (L1) (2M)

**UNIT –IV****Synchronous Sequential Logic****2 MARKS QUESTIONS**

1. What are the classifications of sequential circuits? (2M)
2. What is the operation of D flip-flop? (2M)
3. What is flip-flop (2M)
4. Define Race Around Condition (2M)
5. Difference between latch and flip-flop (2M)
6. Define Propagation Delay (2M)
7. What is Master Slave Flip-flop (2M)
8. Explain Shift Registers (2M)
9. What are the applications of Flip-flops (2M)
10. What is state diagram (2M)

**10 MARKS QUESTIONS**

1. A) Explain the Logic diagram of JK flip-flop? (L2) (5M)  
B) Write difference between Combinational & Sequential circuits? (L4) (5M)
2. A) Explain the Logic diagram of SR flip-flop? (L2) (5M)  
B) Design and draw the 3 bit up-down synchronous counter? (L5) (5M)
3. A) Draw and explain the operation of D Flip-Flop? (L5) (5M)  
B) Explain about Shift Registers? (L2) (5M)
4. A) Draw and explain the operation of SR LATCH? (L5) (5M)  
B) Explain about Ring counter? (L2) (5M)
5. A) Explain about ripple counter? (L2) (5M)  
B) What is state assignment? Explain with a suitable example? (L2) (5M)
6. Explain the working of the following (L2 & L5) (10M)
  - i) J-K flip-flop
  - ii) S- R flip-flop
  - iii) D flip-flop
7. Explain the design of a 4 bit binary counter with parallel load in detail? (L2) (10M)

8. How does it set eliminate is a Master –slave J-K flip-flop? (L2)(10M)
9. A) Explain synchronous and ripple counters compare their merits and demerits? (L2) (5M)
- B) Design a 4 bit binary synchronous counters with D-flip flop? (L5 (5M)
10. a)Write the truth table of clocked T- Flip Flop? (L1) (2M)
- b) Define shift registers? (L1) (2M)
- c) Write the differences between latches and flip flops? (L1)(2M)
- d) Write the differences between synchronous and asynchronous counters? (L1) (2M)
- e)Define Flip-flop and various types of flip flops? (L1) (2M)



**UNIT –V****Memory and Programmable Logic , Digital Logic Circuits****2 MARKS QUESTIONS**

1. Explain the Classification of memory (2M)
2. Define ROM (2M)
3. What is Read and Write Operations (2M)
4. List the major differences between PLA and PAL (2M)
5. Define PLA (2M)
6. Differentiate volatile and non-volatile memory (2M)
7. What are the different types of ROM (2M)
8. Define the Static RAM and Dynamic RAM (2M)
9. What is BIT,BYTE and WORD (2M)
10. What is Cache Memory (2M)

**10 MARKS QUESTIONS**

1. A) Write difference between PROM ,PLA &PAL? (L4) (5M)  
 B) Explain about Hamming code? (L2) (5M)
2. Encode the 11-bit code 10111011101 into 15 bit information code? (L3)(10M)
3. Implement the following function using PLA (L5)(10M)  
 $A(x,y,z)=\sum m(1,2,4,6)$   $B(x,y,z)=\sum m(0,1,6,7)$   $C(x,y,z)=\sum m(2,6)$
4. Design PAL for a combinational circuit that squares a 3 bit number? (L5)(10M)
5. Write about the following (L2)(10M)
  - i) Transistor-transistor Logic (TTL)
  - ii) Emitter – coupled Logic (ECL)
  - iii) CMOS Logic
6. Construct the PROM using the conversion from BCD code to Excess-3 code? (L5)(10M)
7. Implement the following functions using PLA. (L5)(10M)  
 $A(x,y,z) = \sum m(1,2,4,6)$   $B(x,y,z) = \sum m(0,1,6,7)$   $c(x,y,z) = \sum m(2,6)$
8. A)Construct the PROM using the conversion from BCD code to Excess-3 code? (L5)(10M)
9. A)Explain about TTL family ? (L2)(5M)  
 B) Explain about memory decoding error detection and correction? (L2)(5M)

10.    a) Write the difference between PLA & PAL? (L1) (2M)  
      b) Define fan out of a logic gate ? (L1) (2M)  
      c) What is the function of EAROM? (L1) (2M)  
      d) Define CMOS? (L1) (2M)  
      e) Write a short notes on Programmable array Logic? (L1) (2M)

Prepared by: P Nirupama, G Prasad Babu, V Balaji


**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**

Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (OBJECTIVE)**
**Subject with Code :** Digital Logic Design(18CS502)

**Course & Branch:** B.Tech - CSE

**Year & Sem:** I-B.Tech & II-Sem

**Regulation:** R18

**UNIT – I**
**Binary Systems, Boolean Algebra & Logic Gates**

1. (75.23) is a Octal number convert to it equivalent binary number [     ]  
 A) 1110111.110111    B) 111110.010110    C) 1111111.110110    D) 111101.010011
2. 9's complement of 1234 is [     ]  
 A) 8764                      B) 8765                      C) 7886                      D) 7768
3. Find 2's complement of (11000100)\_\_\_\_\_ [     ]  
 A) 00111100                B) 110000100                C) 1010101010                D) none
4. Non-weighted code is \_\_\_\_\_ [     ]  
 A) Gray code                B) Decimal                      C) Binary                      D) octal
5. Decimal value base is \_\_\_\_\_ [     ]  
 A) 10                          B) 8                              C) 16                              D) 2
6.  $A^1 B^1 =$  \_\_\_\_\_ [     ]  
 A)  $A^1 + B^1$                 B)  $(A+B)^1$                       C) AB                              D) A+B
9. BCD code for 92 [     ]  
 A) 011010010010    B) 000100000101    C) 10010010    D) 10010011
10. 10's complement of (52520)<sub>10</sub> is \_\_\_\_\_ [     ]  
 A) 42479                      B) 47479                      C) 47480                      D) 47481
11. (1217)<sub>8</sub> is equivalent to [     ]  
 A) (1217)<sub>16</sub>                B) (028F)<sub>16</sub>                      C) (2297)<sub>10</sub>                      D) (0B17)<sub>16</sub>
12. A decimal number 19 is in excess 3 code is written as [     ]  
 A) 00110                      B) 10110                      C) 10110                      D) 0011
13. The higher significant bit of this result is called \_\_\_\_\_ [     ]  
 A) Sum                          B) carry                          C) 0                              D) none
14. Distributive law is \_\_\_\_\_ [     ]

- A)  $A(B+C) = AB+AC$       B)  $AB=BA$       C)  $A+(B+C)=(A+B)+C$       D) none
15.  $A+1 =$  \_\_\_\_\_ [      ]  
 A) A      B) 1      C) 0      D) none
16.  $ABC+ABC' =$  \_\_\_\_\_ [      ]  
 A) A      B) AB      C) C      D) AC
17.  $A+AB =$  \_\_\_\_\_ [      ]  
 A) 1      B) 0      C) A      D) none
18. Decimal 12 is in binary number system is [      ]  
 A) 1010      B) 1111      C) 1011      D) 1100
19. Find 1's complement of (11010100) \_\_\_\_\_ [      ]  
 A) 00101011      B) 11010100      C) 101010100      D) none
20. What is the maximum number of different boolean functions involving  $n$  Boolean variables? [      ]  
 A)  $n^2$       B)  $2^n$       C)  $2*n$       D)  $2^{2n}$
21. \_\_\_\_\_ bit represent the sign of the number [      ]  
 A) MSB      B) LSB      C) both      D) none
22. Which gate is generate complement of output to given input \_\_\_\_\_ [      ]  
 A) NOT      B) NAND      C) OR      D) XNOR
23. \_\_\_\_\_ codes are non weighted codes [      ]  
 A) Gray      B) decimal codes      C) binary      D) none
24.  $(A+B)+C=A+(B+C)$  is \_\_\_\_\_ law [      ]  
 A) Associative law      B) commutative law      C) Distributive law      D) none
25. Example of weighted code \_\_\_\_\_ [      ]  
 A) gray      B) 8421      C) excess-3      D) none
26. 111001 is a binary value convert to it equivalent octal \_\_\_\_\_ [      ]  
 A) 71      B) 70      C) 15      D) none
27. 7 is a octal value convert to it equivalent decimal \_\_\_\_\_ [      ]  
 A) 8      B) 10      C) A      D) none
28. ASCII stand for \_\_\_\_\_ [      ]  
 B) American standard coded for information interchange  
 C) American standard coded for interchange information      C) both      D) none
29. \_\_\_\_\_ theorem states that  $AB+(AC)^1+BC=AB+(AC)^1$  [      ]  
 B) Consensus theorem      B) duality      C) associative law      D) none
30.  $A.A^1 =$  \_\_\_\_\_ [      ]

- B) 1                      B)0                      C) A                      D) none
31.  $A + A^1B =$  \_\_\_\_\_ [      ]
- A)  $A+B$                       B)  $A+BA$                       C) 0                      D) none
32. Convert AB6 to binary [      ]
- A) 101011010010      B) 101010110110      C) 10101010101      D) 10101111
33. SOP denotes \_\_\_\_\_ [      ]
- A)  $\Sigma$                       B)  $\pi$                       C) both      A&B                      D) none
34. 1's complement is also called as [      ]
- A) Radix                      B) Diminished radix                      C)2      D)15
35. Which gate is generate complement of output to given input \_\_\_\_\_ [      ]
- A) NOT                      B) NAND                      C)OR                      D) XNOR
36. The \_\_\_\_\_ of digital logic gate refers to the number of inputs [      ]
- A) Fan-in                      B) fan-out                      C) both                      D) none
37. POS denotes \_\_\_\_\_ [      ]
- A)  $\Sigma$                       B) $\pi$                       C) both                      D) none
38.  $(A+B)+C=A+(B+C)$  is \_\_\_\_\_ law [      ]
- Associative law                      B) commutative law      C) Distributive law      D) none
39. 231 base is 4 convert to decimal value [      ]
- A) 45                      B) 43                      C) 42                      D) none
40. 53 is decimal value convert to its binary value [      ]
- A) 110101                      B) 110010                      C) 110101                      D) 11001

**UNIT – II**

**Gate Level Minimization**

1. Vietch diagram also known as \_\_\_\_\_ [     ]  
 A) Karnaugh map    B) logic gate    C) BSD    D) none
2. 2 variable k map contains \_\_\_\_\_ cells [     ]  
 A) 8    B) 4    C) 2    D) none
3. The map method is first proposed by \_\_\_\_\_ [     ]  
 A) Vietch    B) charlas    C) karnaugh    D) none
4. A grouping of 8 bits in K-map known as \_\_\_\_\_ [     ]  
 A) byte    B) octet    C) quad    D) none
5. Example of UNIVERSAL GATE is \_\_\_\_\_ [     ]  
 A) NAND    B) NOT    C) OR    D) none
6. The code used for labeling the cells of k map is \_\_\_\_\_ [     ]  
 A) gray    B) octal    C) BCD    D) none
7. AND Gate requires \_\_\_\_\_ Minimum number of inputs. [     ]  
 A) 2    B) 1    C) 4    D) none
8. A pair is a group of \_\_\_\_\_ adjacent cells in a k-map [     ]  
 A) 2    B) 4    C) 8    D) 16
9. 3 variable k map contains \_\_\_\_\_ cells [     ]  
 A) 6    B) 8    C) 5    D) 3
10. \_\_\_\_\_ is a group of 8 adjacent cells in K-Map [     ]  
 A) octet    B) pair    C) quad    D) none
11. don't care condition represented label as \_\_\_\_\_ [     ]  
 A) S    B) X    C) d    D) both B&C
12. The output levels are indicated by "X" or "d" in the truth tables and are called \_\_\_\_ [     ]  
 A) don't care conditions    B) minterms    C) output    D) none
13. Which gate is not universal gate \_\_\_\_\_ [     ]  
 A) NAND    B) NOR    C) XOR    D) none
14. Consider the following Boolean function of four variables  $f(w,x,y,z) = \sum m(1,3,4,11,12,14)$  The function is [     ]  
 A) independent of one variable    B) independent of two variables  
 C) independent of three variables    D) Dependant on all the variables

15. 4 variable k map contains \_\_\_\_\_ cells [     ]  
 A) 12                      B) 16                      C) 15                      D) 3
16. In K-map Pair eliminates \_\_\_\_\_ variable from output expression. [     ]  
 A) One                      B) Two                      C) Three                      D) Zero
17. In K-map Quad eliminates \_\_\_\_\_ variable from output expression. [     ]  
 A) One                      B) Two                      C) Three                      D) Zero
18. In K-map octet eliminates \_\_\_\_\_ variable from output expression. [     ]  
 A) One                      B) Two                      C) Three                      D) Zero
19. 5 variable k map contains \_\_\_\_\_ cells [     ]  
 A) 32                      B) 36                      C) 15                      D) 3
20. The sum of all the minterms of a given Boolean function is equal to [     ]  
 A) Zero                      B) One                      C) Two                      D) Three
21. The product of all the maxterms of a given Boolean function is equal to [     ]  
 A) Zero                      B) One                      C) Two                      D) Three
22. Let  $f(A,B) = A+B$ , simplified expression for function  $f(f(x+y,y),z)$  is [     ]  
 A)  $x+y+z$                       B)  $xyz$                       C) 1                      D)  $xy+z$
23. Maximum number of prime implicants with n binary variable in the reduced expression is [     ]  
 A)  $2^n$                       B)  $2*n$                       C)  $2^{n-1}$                       D)  $2+n$
24. The Logical expression  $y = \sum m(0,3,6,7,10,12,15)$  is equivalent to [     ]  
 A)  $Y = \pi M(0,3,6,7,10,12,15)$                       B)  $y = \pi M(1,2,4,5,8,9,11,13,14)$   
 C)  $Y = \sum M(0,3,6,7,10,12,15)$                       B)  $y = \sum M(1,2,4,5,8,9,11,13,14)$
25. The minimum number of 2 input NAND gates required to implement the following Boolean function  $f = (x'+y')(z+w)$  [     ]  
 A) 3                      B) 4                      C) 5                      D) 6
26. What is the value of  $A+A'B$  [     ]  
 A) A                      B) B                      C) 0                      D)  $A+B$
27. \_\_\_\_\_ method is used for to simplify the boolean expressions [     ]  
 A) K-map                      B) Algebraic rules                      C) Tabular method                      D) ALL

28. The pictorial representation of truth table is also called as\_\_\_\_\_ [     ]  
 A) K-Map                      B) Tabular map                      C) Both A&B                      D) None
29. The map method is modified by\_\_\_\_\_ [     ]  
 A) Vietch                      B) charlas                      C) karnaugh                      D) none
30. The Sum of product Boolean expression represented the symbol is\_\_\_\_\_ [     ]  
 A)  $\pi$                       B)  $\Sigma$                       C)  $\epsilon$                       D)  $\infty$
31. The Product of sum Boolean expression represented the symbol is\_\_\_\_\_ [     ]  
 A)  $\pi$                       B)  $\Sigma$                       C)  $\epsilon$                       D)  $\infty$
32. \_\_\_\_\_ method is also called as Quine-Mc Cluskey method [     ]  
 A) K-map                      B) Tabular                      C) Graph                      D) None
33. The minimized expression of  $Y = A'B'C + A'BC$  is\_\_\_\_\_ [     ]  
 A)  $A'B$                       B)  $A'C$                       C)  $AB$                       D)  $BC$
34. The minimized expression of  $Y = A'B'C + A'BC + ABC + ABC'$  is\_\_\_\_ [     ]  
 A)  $AC + BC$                       B)  $A + C$                       C)  $A'C + AB$                       D)  $AB$
35. The Boolean expression is  $f(A, B, C, D)$  of  $m_7$  representation is [     ]  
 A)  $ABCD$                       B)  $ABC'D'$                       C)  $A'BCD$                       D)  $A'B'C'D'$
35. The Boolean expression is  $f(A, B, C, D)$  of  $M_{12}$  representation is [     ]  
 A)  $A + B + C + D$                       B)  $A + B + C + D'$                       C)  $A' + B + C + D$                       D)  $A' + B' + C + D$
36. In K-map using the sequences codes are [     ]  
 A) Excess-3                      B) Gray                      C) Binary                      D) BCD
37. 2 NAND gates equivalent to\_\_\_\_\_ function. [     ]  
 A) AND                      2) OR                      C) Ex-OR                      D) Ex-NOR
38. 3 NAND gates equivalent to\_\_\_\_\_ function. [     ]  
 A) AND                      2) OR                      C) Ex-OR                      D) Ex-NOR
39. 2 NOR gates equivalent to\_\_\_\_\_ function. [     ]  
 A) AND                      2) OR                      C) Ex-OR                      D) Ex-NOR
40. 3 NOR gates equivalent to\_\_\_\_\_ function. [     ]  
 A) AND                      2) OR                      C) Ex-OR                      D) Ex-NOR



**UNIT – III****Combinational Logic**

1. A Combinational circuits consists of \_\_\_\_\_ [      ]  
A) Input variables      B) logic gates      C) output variables      D) all of these
2. \_\_\_\_\_ circuits needs two binary inputs and two binary outputs. [      ]  
A) Full adder      B) half adder      C) sequential      D) counter
3. In half adder circuit the inputs are high sum is\_\_\_\_ and carry\_\_\_\_. [      ]  
A) 0,0      B) 0,1      C) 1,0      D) 1,1
4. A \_\_\_\_\_ is a combinational circuit that converts binary information from n inputs lines to a maximum of  $2^n$  unique output lines. [      ]  
A) Encoder      B) Decoder      C) both A & B      D) none of these
5. \_\_\_\_\_ circuits needs three binary inputs and two binary outputs. [      ]  
A) Full adder      B) half adder      C) combinational logic      D) none
6. A decoder with n inputs then it produce \_\_\_\_\_ out puts [      ]  
A)  $2n$       B)  $2^n$       C) n      D)  $n+2$
7. A \_\_\_\_\_ is a combinational circuit that converts binary information from n inputs lines to a of  $2^n$  unique output lines. [      ]  
A) Encoder      B) Decoder      C) both A & B      D) none of these
8. In which circuits memory is not required [      ]  
A) Sequential circuits      B) synchronous circuits      C) both      D) none
9. In full adder circuit, the inputs are high sum is\_\_\_\_ and carry\_\_\_\_. [      ]  
A) 0,0      B) 0,1      C) 1,0      D) 1,1
10. In full subtractor circuit, the inputs are high sum is\_\_\_\_ and carry\_\_\_\_. [      ]  
A) 0,0      B) 0,1      C) 1,0      D) 1,1
11. A\_\_\_\_\_ is a special combinational circuit designed to compare the binary variables. [      ]  
A) Multiplexer      B)Decoder      C)Comparator      D)Demultiplexer
12. A\_\_\_\_\_ circuit with n inputs and produce  $2^n$  outputs. [      ]  
A) Multiplexer      B)Decoder      C)Comparator      D)Demultiplexer
13. \_\_\_\_\_ circuit acts as inverse operation of a decoder. [      ]  
A) Decoder      B)Multiplexer      C)Encoder      D)ALL
14. A \_\_\_\_\_ circuit with  $2^n$  inputs and produce n data outputs. [      ]  
A) Multiplexer      B) Encoder      C)Decoder      D)None
15. In\_\_\_\_\_, if two or more inputs are equal to 1 at the same time, the input having the highest Priority will take precedence. [      ]

- A)Encoder    B)priority encoder    C)Decoder    D)priority encod6er
16. In \_\_\_\_\_ circuits consists of  $2^n$  inputs with one output [    ]  
 A) Multiplexer    B) Encoder    C)Decoder    D)None
17. In Multiplexer consists of  $2^n$  input lines and \_\_\_\_\_ selection lines [    ]  
 A)  $2n$     B)  $n$     C) 1    D)  $2+n$
18. The number of  $4 \times 1$  multiplexer require to implement  $16 \times 1$  mux [    ]  
 A) 5    B) 4    C) 3    D) 8
19. The method of speeding up the process by eliminating inter stage carry delay is called \_\_\_\_\_ addition [    ]  
 A) Binary    B) Carry Look Ahead    C) Parallel    D) None
20. Parallel adder is also called as \_\_\_\_\_ [    ]  
 A) Binary    B) Serial    C) Both A&B    D) None
21. In half Adder sum simplified expression is [    ]  
 A)  $AB+A'B'$     B)  $AB'+A'B$     C) Both A&B    D) None
22. Implementation of full adder requires \_\_\_\_\_ half adders and an \_\_\_\_\_ gate [    ]  
 A) 3, AND    B) 4, AND    C) 2, OR    D) 1, OR
23. In parallel adder or subtractor the mode input  $m=1$  the circuit acts as a \_\_\_\_\_ [    ]  
 A) Adder    B) Subtractor    C) Both A&B    D) Multiplayer
24. In parallel adder or subtractor the mode input  $m=0$  the circuit acts as a \_\_\_\_\_ [    ]  
 A) Adder    B) Subtractor    C) Both A&B    D) Multiplayer
25. The \_\_\_\_\_ adder is a sequential circuit [    ]  
 A) Serial    B) parallel    C) Both A & B    D) None
26. The \_\_\_\_\_ adder is a Combinational circuit [    ]  
 A) Serial    B) parallel    C) Both A & B    D) None
27. The \_\_\_\_\_ adder is work as slower [    ]  
 A) Serial    B) parallel    C) Both A & B    D) None
28. The \_\_\_\_\_ adder is work as faster [    ]  
 A) Serial    B) parallel    C) Both A & B    D) None
29. A \_\_\_\_\_ is a multiple input and multiple output logic circuits [    ]  
 A) Multiplexer    B) Demultiplexer    C) Decoder    D) None
30. What are basic gates required to implement a full adder [    ]  
 A) 1-Ex-OR and 1- AND    B) 2-Ex-OR and 1- OR  
 C) 2-Ex-OR , 2- AND and 1- OR    D) 1-Ex-OR , 2- AND and 2- OR
31. In half adder circuit the inputs are 1, 0 then sum is \_\_\_\_\_ and carry is \_\_\_\_\_. [    ]  
 A) 0,0    B) 0,1    C) 1,0    D) 1,1
32. In full subtractor the inputs are low then difference is \_\_\_\_\_ & barrow is \_\_\_\_\_ [    ]  
 A) 0,0    B) 0,1    C) 1,0    D) 1,1

33. In full subtractor the inputs are high then difference is \_\_\_\_\_ & barrow is\_\_\_\_ [      ]  
 A) 0,0                      B) 0,1                      C) 1,0                      D) 1,1
34. Decimal adder is also called as [      ]  
 A) Binary adder      B) BCD Adder      C) Binary Subtractor      D) None
35. \_\_\_\_\_ adder uses shift register [      ]  
 A) Serial                      B) Parallel                      C) Both A&B                      D) None
36. In \_\_\_\_\_ circuit there are no selection lines [      ]  
 A) Multiplexer              B) Demultiplexer      C) Decoder      D) None
37. In \_\_\_\_\_ circuit the selection of specific output line is control by the value of selection lines [      ]  
 A) Multiplexer              B) Demultiplexer      C) Decoder      D) None
38. In full adder the simplified carry output is [      ]  
 A)  $AB+AC+BC$       B)  $AB'+A'C+BC'$       C)  $A'B+A'C+BC$       D) None
39. In Half adder the simplified carry output is [      ]  
 A)  $BC$                       B)  $AB$                       C)  $A'B$                       D) None
40. \_\_\_\_\_ adder uses register with parallel load capacity [      ]  
 A) Serial                      B) Parallel                      C) Both A&B                      D) None

**UNIT – IV**  
**Synchronous Sequential Logic**

1. In D-flip flop the input  $D=0$  the output is \_\_\_\_\_ [     ]  
A) 1                                  B) 0                                  C) X                                  D) 10
2. In asynchronous are \_\_\_\_\_ to design [     ]  
A) easy                                  B) difficult                                  C) both A&B                                  D) medium
3. In SR latch the S referred to \_\_\_\_\_ [     ]  
A) Synchronous                                  B) set                                  C) start                                  D) none
4. In T flip flop the input  $T=1$  then  $Q_{n+1}$  is \_\_\_\_\_ [     ]  
A)  $Q_n$                                   B)  $Q_n'$                                   C)  $Q_{n+1}$                                   D) 0
5. In SR latch  $s=1, r=1$  the state is \_\_\_\_\_ [     ]  
A) No change                                  B) reset                                  C) set                                  D) indeterminate
6. In synchronous counter , if \_\_\_\_\_ then flip flop complements the input at the time of clock edges [     ]  
A)  $T=1$                                   B)  $J=K=1$                                   C) both A & B                                  D) none
7. In Binary counter counts in binary coded decimal from 0000 to \_\_\_\_\_ and back to 0000. [     ]  
A) 1001                                  B) 1111                                  C) 1000                                  D) 0000
8. 10. In SR latch the S referred to \_\_\_\_\_ [     ]  
A) Synchronous                                  B) set                                  C) start                                  D) none
9. A \_\_\_\_\_ is a circular shift register with only one flip flop being set at any particular time, all others are cleared. [     ]  
A) ring counter                                  B) shift register                                  C) binary counter                                  D) none of these
10. A sequential circuits consists of \_\_\_\_\_ [     ]  
A) storage element                                  B) logic gates                                  C) both A& B                                  D) all of these
11. D-flip flop is also known as \_\_\_\_\_ [     ]  
A) Delay flip flop                                  B) SR latch                                  C) JK flip flop                                  D) none
12. Flip flops are used for \_\_\_\_\_ [     ]  
A) Memory element                                  B) delay element                                  C) both                                  D) none
13. A J-K flip flop is in “ No Change “ condition when the value of \_\_\_\_\_ [     ]  
A)  $J=0, K=0$                                   B)  $J=1, K=1$                                   C)  $J=0, K=1$                                   D)  $J=1, K=0$
14. How is a JK Flip flop made to toggle state [     ]  
A)  $J=0, K=0$                                   B)  $J=1, K=1$                                   C)  $J=0, K=1$                                   D)  $J=1, K=0$
15. In \_\_\_\_\_ counter all the flip flops are clocked simultaneously [     ]  
A) Asynchronous                                  B) Synchronous                                  C) Ripple                                  D) none of these
16. A J-K flip flop is in “ No Change “ condition when the value of \_\_\_\_\_ [     ]  
A)  $J=0, K=0$                                   B)  $J=1, K=1$                                   C)  $J=0, K=1$                                   D)  $J=1, K=0$
17. A \_\_\_\_\_ is a register for counting the no of clock pulses arriving at its clock inputs. [     ]

- A) Counter      B) Register      C) Flip Flop      D) Decoder
18. How is a JK Flip flop made to toggle state [   ]  
 A) J=0 K=0      B) J=1 K=1      C) J=0 K=1      D) J=1 K=0
19. In \_\_\_\_\_ counter all the flip flops are clocked simultaneously [   ]  
 A) Asynchronous      B) Synchronous      C) Ripple      D) none of these
20. A \_\_\_\_\_ is a group of flip flops [   ]  
 A) Register      B) latches      C) counter      D) none of these
21. In SR flip flop S=1,R=0 then the state is \_\_\_\_\_ [   ]  
 A) set      B) reset      C) nochange      D) indeterminate state
22. D-flip flop is also known as \_\_\_\_\_ [   ]  
 A) Delay flip flop      B) SR latch      C) JK flip flop      D) none
23. How is a JK Flip flop made to toggle state [   ]  
 A) J=0 K=0      B) J=1 K=1      C) J=0 K=1      D) J=1 K=0
24. In \_\_\_\_\_ counter all the flip flops are clocked simultaneously [   ]  
 A) Asynchronous      B) Synchronous      C) Ripple      D) none of these
25. In SR latch s=1,r=1 the state is \_\_\_\_\_ [   ]  
 A) No change      B) reset      C) set      D) indeterminate
26. In which circuits memory is required [   ]  
 A) Sequential circuits      B) synchronous circuits      C) both A&B      D) none
27. Flip flops are used for \_\_\_\_\_ [   ]  
 A) Memory element      B) delay element      C) both      D) none
28. 64 GB= \_\_\_\_\_ [   ]  
 A)  $2^{30}$       B)  $2^{36}$       C)  $2^{32}$       D) none of these
29. In JK flip flop j=1,k=1 then the state is \_\_\_\_\_ [   ]  
 A)  $Q_n^1$       B)  $Q_n$       C) both      D) none of these
30. In which circuits memory is not required [   ]  
 A) Sequential circuits      B) synchronous circuits      C) both      D) none
31. In synchronous counter , if \_\_\_\_\_ then flip flop complements the input at the time of clock edges [   ]  
 A) T=1      B) J=K=1      C) both A & B      D) none
32. Binary counter counts in binary coded decimal from 0000 to \_\_\_\_\_ and back to 0000 [   ]  
 A) 1001      B) 1111      C) 1000      D) 0000
33. In SR latch the S referred to \_\_\_\_\_ [   ]  
 A) Synchronous      B) set      C) start      D) none
34. In the binary synchronous counter if the present state of a 4-bit counter is  $A_3A_2A_1A_0=0011$ , then the next count is \_\_\_\_\_ [   ]  
 A) 0010      B) 0100      C) 0101      D) none of these
35. A \_\_\_\_\_ is a circular shift register with only one flip flop being set at any particular time, all others are cleared. [   ]  
 A) ring counter      B) shift register      C) binary counter      D) none of these
36. The characteristic equation of SR Flipflop is  $Q_{n+1}=$  \_\_\_\_\_ [   ]

- A)  $S+R'Q_n$       B)  $S'+RQ_n$       C)  $S+R$       D)  $Q_n$
37. The characteristic equation of JK Flipflop is  $Q_{n+1} = \underline{\hspace{2cm}}$  [      ]  
 A)  $JQ_n'+KQ_n$       B)  $JQ_n'+K'Q_n$       C)  $JQ_n+KQ_n$       D) None
38. The characteristic equation of T Flipflop is  $Q_{n+1} = \underline{\hspace{2cm}}$  [      ]  
 A)  $TQ_n'+T'Q_n$       B)  $TQ_n'+T'Q_n'$       C)  $TQ_n+TQ_n$       D) None
39. The characteristic equation of D Flipflop is  $Q_{n+1} = \underline{\hspace{2cm}}$  [      ]  
 A)  $DQ_n$       B)  $D'Q_n'$       C)  $D'$       D)  $D$
40. \_\_\_\_\_ sequential circuit is easier to design [      ]  
 A) Asynchronous      B) Synchronous      C) Ripple      D) none of these

**UNIT – V**  
**Memory and Programmable Logic , Digital Logic Circuits**

1. The \_\_\_\_\_ is a programmable logic device with a fixed OR array and a programmable AND array. [      ]  
A) PAL                                      B) PLA                                      C) PROM                                      D) none of these
2. \_\_\_\_\_ stores the binary information permanently. [      ]  
A) RAM                                      B) ROM                                      C) both A & B                                      D) none of these
3. In Hamming code technique, if the data does not have any error, then C = \_\_\_\_\_ [      ]  
A) 10001                                      B) 0000                                      C) 1001                                      D) 1111
4. The process of retrieving the information from the memory is called \_\_\_\_\_ operation. [      ]  
A) Read                                      B) Write                                      C) Both A & B                                      D) None
5. A group of eight bits is called a \_\_\_\_\_. [      ]  
A) Bits                                      B) byte                                      C) kilobyte                                      D) none of these
6. The read only memory is a \_\_\_\_\_ device [      ]  
A) Programmable logic                      B) combinational logic C) A & B                                      D) none
7. ROM performs \_\_\_\_\_ operation. [      ]  
A) Read                                      B) Write                                      C) Both A & B                                      D) None
6. Types of ROM memories are \_\_\_\_\_ [      ]  
A) EPROM    B) EEPROM                                      C) PROM                                      D) All of these.
7. EEPROM abbreviated as \_\_\_\_\_ [      ]  
A) Erasable – Erasable PROM                      B) Electrically Erasable PROM  
C) Electrically- Electrically PROM                      D) none of these
8. \_\_\_\_\_ is a nonsaturated digital logic family. [      ]  
A) ECL                                      B) TTL                                      C) both A & B                                      D) none of these
9. The \_\_\_\_\_ is a programmable logic device with a fixed OR array and a programmable AND array. [      ]  
A) PAL                      B) PLA                      C) PROM                      D) none of these
13. \_\_\_\_\_ stores the binary information permanently. [      ]  
A) RAM                      B) ROM                      C) both A & B D) none of these
14. In Hamming code technique, if the data does not have any error, then C = \_\_\_\_\_ [      ]  
A) 10001                      B) 0000                      C) 1001                      D) 1111
15. The process of retrieving the information from the memory is called \_\_\_\_\_ operation. [      ]  
A) Read                      B) write                      C) both read & write    D) none
16. In the binary synchronous counter if the present state of a 4-bit counter is  $A_3A_2A_1A_0=0011$ , then the next count is \_\_\_\_\_ [      ]  
A) 0010                      B) 0100                      C) 0101                      D) none of these
17. RAM performs \_\_\_\_\_ operations [      ]  
A) Read                                      B) write                                      C) both A & B                                      D) none
18. PAL stands \_\_\_\_\_ [      ]

- A) Programmable logic array B) programmable array logic C) both A & B D) none of these
19. A memory write stores binary information in group of bits called \_\_\_\_\_ [     ]  
 A) Words B) bytes C) GB D) none
20. SRAM is made of with \_\_\_\_\_ [     ]  
 A) capacitors B) register C) latches D) counter
21. How many types of memories are used in digital systems? [     ]  
 A) 2 B) 3 C) 4 D) 5
22. DRAM abbreviated as \_\_\_\_\_ [     ]  
 A) Delay RAM B) Determinate RAM C) Dynamic RAM D) none
23. To construct  $2^k \times n$  ROM is required \_\_\_\_\_ OR gates. [     ]  
 A)  $2^n$  B)  $2 \times n$  C)  $n+1$  D)  $n$
24. When the memory enable input is active, and read/write input value is 1 then which indicates \_\_\_\_\_ operation to be performed [     ]  
 A) read B) write C) both A & B D) none of these
25. In Hamming code method if the data bits are 11 range then the parity bits size is \_\_\_\_\_ [     ]  
 A) 5 B) 4 C) 3 D) none of these
26. \_\_\_\_\_ information is stored in memory [     ]  
 A) Binary B) decimal C) octal D) none
27. The process of storing data into the memory is called \_\_\_\_\_ [     ]  
 A) read B) write C) delete D) none of these
28. TTL is \_\_\_\_\_ [     ]  
 A) Transistor- Transistor Logic B) Transistor- Transfer Logic  
 C) Transistor- Transmitter Logic D) none of these
29. The \_\_\_\_\_ is a programmable logic device with a fixed OR array and a programmable AND array. [     ]  
 A) PAL B) PLA C) PROM D) none of these
30. \_\_\_\_\_ stores the binary information permanently. [     ]  
 A) RAM B) ROM C) both A & B D) none of these
31. In Hamming code technique, if the data does not have any error, then  $C =$  \_\_\_\_\_ [     ]  
 A) 10001 B) 0000 C) 1001 D) 1111
32. The process of retrieving the information from the memory is called \_\_\_\_\_ operation. [     ]  
 A) Read B) Write C) Both A & B D) None
33. A group of eight bits is called a \_\_\_\_\_ [     ]  
 A) Bits B) byte C) kilobyte D) none of these
34. The read only memory is a \_\_\_\_\_ device [     ]  
 A) Programmable logic B) combinational logic C) A & B D) none
35. The \_\_\_\_\_ is a programmable logic device with a fixed OR array and a programmable AND array. [     ]  
 A) PAL B) PLA C) PROM D) none of these
36. \_\_\_\_\_ stores the binary information permanently. [     ]  
 A) RAM B) ROM C) both A & B D) none of these



37. In Hamming code technique, if the data does not have any error, then C =\_\_\_\_ [     ]  
A)10001     B)0000     C) 1001     D) 1111
38. The process of retrieving the information from the memory is called\_\_\_\_\_ operation. [     ]  
A) Read     B) write     C) both read & write     D) none
39. A group of eight bits is called a \_\_\_\_\_ [     ]  
A)Bits     B) byte     C) kilobyte     D) none of these
40. The read only memory is a \_\_\_\_\_ device [     ]  
A)Programmable logic     B) combinational logic     C) A & B     D) none

Prepared by: \_Prepared by: P Nirupama, G Prasad Babu, V Balaji