



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code : Basic Electrical Engineering(18EE0239)


Course & Branch: B.Tech–(ECE,CSE & CSIT)

Year & Sem: I-B.Tech& II-Sem


Regulation: R18

UNIT –I
DC CIRCUITS

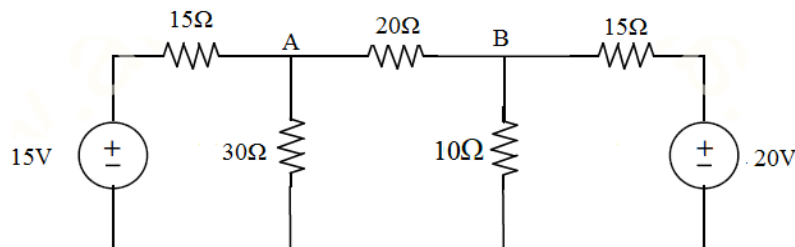
1. (a) State and explain Kirchoff's laws? [4M]
(b) Determine the current in branch A-B by using KVL [6M]



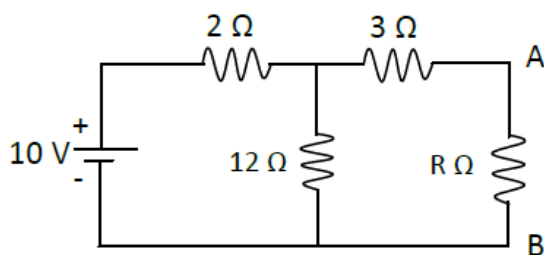
2. a) State and explain Norton's theorem? [5M]
b) Draw the Norton's equivalent circuit for the circuit shown in figure. [5M]



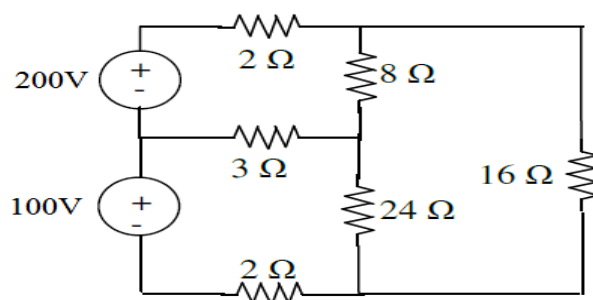3. Determine the mesh currents for the circuit shown below. [10M]




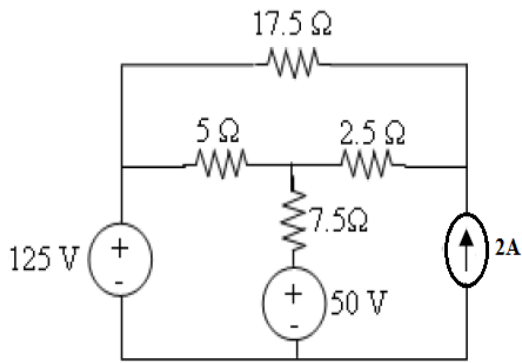4. Use nodal analysis to find the node voltages for the below circuit. [10M]




5. a) State and Explain Thevenin's Theorem [5M]

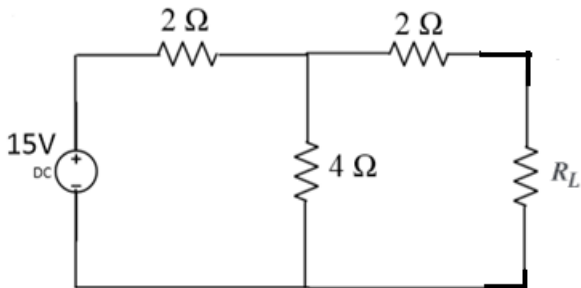b) Find load current by using Thevenin's theorem for the following circuit where $R_L=3\Omega$ [6M]




6 a) Derive the time response of RL circuit [5M]

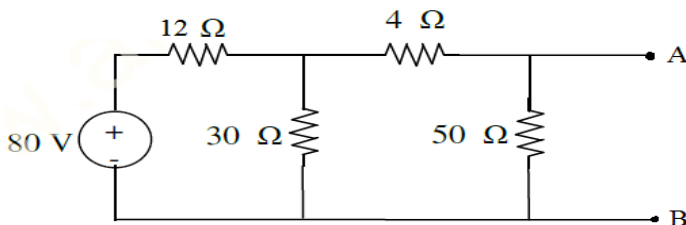b) find the Thevenin's equivalent for the circuit shown below [5M]




7. a) Derive the time response of RC circuit [5M]

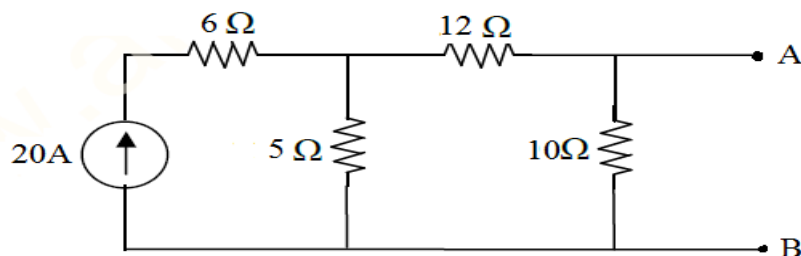b) find the Norton's equivalent for the circuit shown below. [5M]



8.a) State and explain Superposition theorem? [4M]

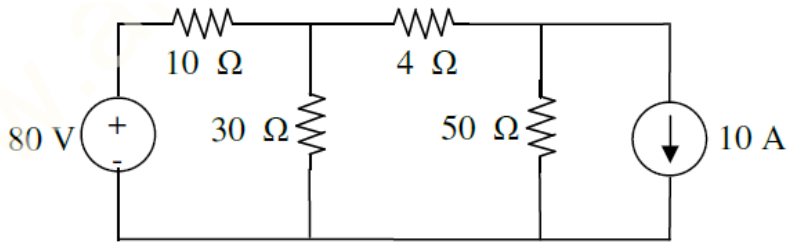
b) Verify Superposition theorem for 4Ω resistor for the following circuit. [6M]




9. a) explain the circuit elements R,L &C. [4M]

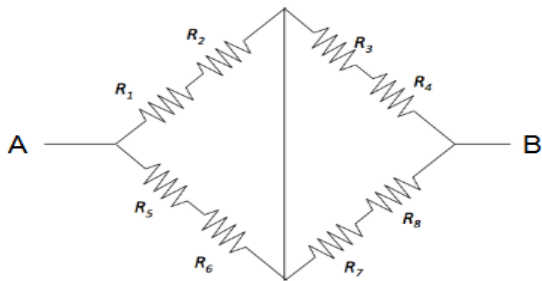b) i) Find the equivalent resistance between AB for the circuit shown below. [3M]


$R_1=4\Omega, R_2=2\Omega, R_3=8\Omega, R_4=1\Omega, R_5=12\Omega, R_6=3\Omega, R_7=10\Omega$ & $R_8=5\Omega$



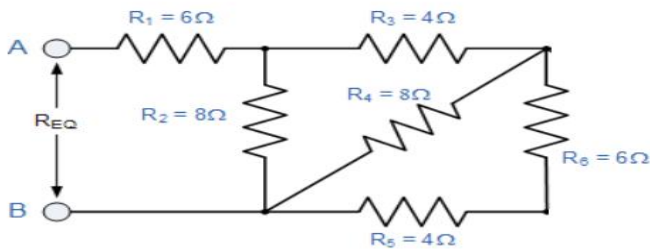ii) Find the equivalent resistance for the circuit shown below. [3M]



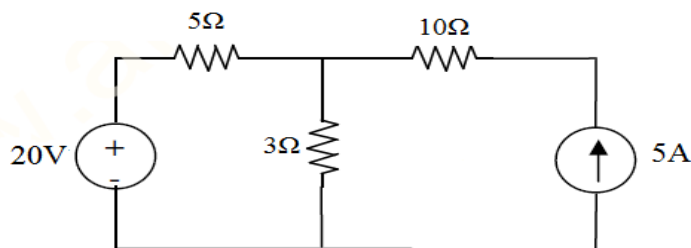10. State and Explain the Super position theorem. And By using superposition theorem find the current flowing through the 3 ohm resistor. [10M]




- 11.(a) What is Circuit and Network? [2M]
- (b) Define Inductance ? [2M]
- (c) Define Capacitor and represent symbolically ? [2M]
- (d) State Ohm's law and write its expression ? [2M]
- (e) A electric kettle takes a current of 12.5A at 240V. What is the resistance of heating Element ? [2M]


UNIT-II

AC CIRCUITS

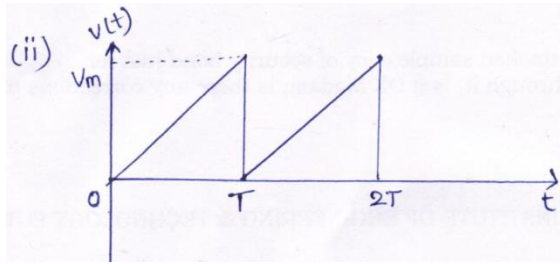1. (a) Derive an expression for RMS values of sine wave form. [6M]
- (b) An alternating current is expressed as $I = 14.14 \sin 314t$. Determine. [4M]
- i. Maximum current ii. rms current iii. Frequency
- iv. Instantaneous current when $t = 0.02\text{msec}$.
2. Derive an expression for the current and impedance for a series RL and RC circuit excited by a sinusoidally alternating voltage. Draw the phasor diagrams. [10M]
3. a) Define Admittance and impedance [4M]
- b) The impedances of series circuit are $Z_1 = (6+j8)$ ohms and $Z_2 = (8-j6)$ ohms. If the applied voltage is 120V, find total impedance, current and power factor. Draw the phasor diagram. [6M]
4. (a) Explain parallel RL and RC circuits with phasor diagrams. [6M]
- (b) A 120V AC circuit contain 10Ω resistance and 30Ω inductive reactance in series. What is average power of this circuit. [4M]
5. (a) Define power factor, apparent power, active power and reactive power [4M]
- (b) Z_1 and Z_2 are in parallel where currents corresponding impedances are $I_1 = 50 \angle 10$ and $I_2 = 20 \angle 30$. If the applied voltage is $100 \angle 15V$, find true power, reactive power and apparent power in each branch. [6M]
6. a) Derive an expression for the voltage and impedance for a series RLC circuit excited by a sinusoidally alternating voltage. [5M]
- (b) A series circuit consisting of a 10Ω resistor, a $100\mu\text{F}$ capacitor and a 10 mH inductor is driven by a 50 Hz a.c. voltage source of maximum value 100 volts. Calculate the equivalent impedance, Current in the circuit and the phase angle. [5M]
7. (a) Derive the voltage and current relations in three phase balanced circuits for delta connection. [6M]
- (b) Find the rms value for the following waveform [4M]



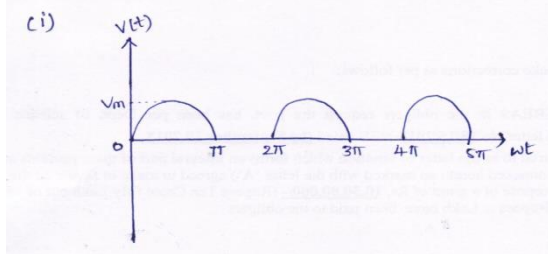8. (a) Explain the phasor relation for R, L & C elements. [4M]
- (b) A resistor of 50Ω and inductance of 100mH are connected in series across 200V , 50Hz supply. Determine the following [6M]
- (i) Impedance (ii) current flowing through the circuit (iii) power factor
9. (a) Derive the voltage and current relations in three phase balanced circuits for star connection. [10M]
- (b) Find the rms value for the following waveforms [4M]



10. (a) Explain resonance for series RLC circuit and derive the equation for resonant frequency. [5M]
- (b) A series RLC circuit of $R=50$ ohms, $L= j25$ ohms. Determine the value of capacitive reactance and impedance at resonance [5M]
11. (a) Define Form Factor and Peak Factor? [2M]
- (b) Define vector and phasor? [2M]
- (c) Define resonance? [2M]
- (d) Draw Star and Delta Connections of Three Phase circuit? [2M]
- (e) Write Expressions for Voltages and Current in Three Phase balanced system? [2M]

Unit-III
TRANSFORMERS

- 1.(a) Explain the briefly the construction and working of a single phase transformer [6M]

- (b) A 200 KVA, 1100/415V, 50Hz single phase transformer has 80 turns of secondary.
Calculate the primary number of turns. [4M]
- 2.(a) Write a short notes on regulation and Efficiency of the transformer. [5M]
(b) The efficiency of a 200 KVA, 1- Φ transformer is 98.7% when operating at full-load, 0.8 p.f lagging, the iron loss in the transformer is 200 W. Calculate: (i) Full load copper loss
(ii) Half load copper loss. [5M]
3. (a) Explain the various losses in a transformer. [5M]
(b) a single phase transformer with a ratio of 440/110V takes a no load current of 5A at 0.2 p.f. lagging. If the secondary supplies a current of 120A at a p.f. of 0.8 lagging. find the current taken by the primary. [5M]
4. (a) Explain BH characteristics. [5M]
(b) A 100KVA transformer has primary and secondary turns of 400 and 100 respectively. Its primary and secondary resistance and reactance are: $R_1=0.3\Omega$, $R_2=0.015\Omega$, $X_1=1.1\Omega$, $X_2=0.055\Omega$, supply voltage is 2400V. Calculate equivalent resistance and reactance on the primary side. [5M]
5. (a) Explain about magnetic materials. [4M]
(b) A 1- Φ , 50 HZ transformer has 80 turns on the primary winding and 400 turns on the secondary winding. The net cross sectional area of the core is 200 cm^2 . If the primary winding is connected to a 240V, 50 HZ supply, determine (i) The emf induced in the secondary winding.
(ii) The maximum value of the flux density in the core. [6M]
- 6.(a) Explain about ideal transformer and derive the EMF equation of the transformer. [6M]
(b) A 10KVA, 2200/220V, 50Hz single phase transformer has a net core area of 300 cm^2 and a maximum flux density of 1.5 wb/m^2 . Calculate the number of turns in primary and secondary winding. [6M]
7. Explain the practical transformer on load and draw the phasor diagrams. [10M]
8. Obtain the equivalent circuit of single phase transformer referred to primary and secondary. [10M]
9. What is meant by auto transformer? What are the advantages of Auto transformer when compared to two winding transformer? [10M]
10. What are three phase transformer connections and explain it? [10M]
11. (a) Define Transformer? [2M]
(b) Write Transformation ratio? [2M]
(c) Why Transformer doesn't work on DC? [2M]
(d) Why Transformer rating will be in kVA? [2M]

- (e) What is the condition for maximum efficiency in a Transformer and expression for load current at maximum efficiency? [2M]

Unit-IV

ELECTRICAL MACHINES

1. What is rotating magnetic field? Explain in brief? [10M]
2. Explain the construction of three phase induction motor? [10M]
3. Sketch and explain the torque slip characteristics of 3 phase induction motor? [10M]
4. Explain the construction of three phase alternator? [10M]
5. Explain the construction single phase induction motor [10M]
6. Explain the working principle of single phase induction motor [10M]
7. Explain the construction of DC motor? [10M]
8. Sketch and explain the torque speed characteristics of DC motor? [10M]
9. Explain the various method of speed control of separately excited DC motor? [10M]
10. Explain the working principle of synchronous generator? [10M]
11. (a) Define Torque and slip? [2M]
- (b) Why is an induction motor called a rotating transformer? justify [2M]
- (c) why single phase induction motor is not self starting? [2M]
- (d) What is commutation & commutator? [2M]
- (e) Define Alternator ? [2M]

UNIT 5

ELECTRICAL INSTALLATIONS

1. Explain different types of wiring system. [10M]
2. Explain the following electrical wiring system with necessary diagrams. [10M]
 - (a) CTS wiring and (b) Concealed wiring
3. With relevant diagrams explain in detail about various types of fuses used in electrical wiring systems. [10M]
4. Explain briefly about earthing and how it plays an important role in installation. [10M]
5. a) How many types of batteries are there? [5M]
 - b) Explain the characteristics of batteries. [5M]
6. Explain different methods used for improvement of power factor. [10M]
7. a) Explain battery backup. [5M]
 - b) How many types of cables are there? Explain them with neat sketch. [5M]
8. What is energy consumption and Explain how it is calculated by an example. [10M]
9. a) What is the importance of wiring. [5M]
 - b) Explain how wiring system is classified. [5M]
10. Explain about
 - a) pvc cables and b) wheather proof cables [10M]
11. (a) Define Switch Gear? [2M]

- (b) Define Battery? [2M]
- (c) Define Energy and write it's expression? [2M]
- (d) Define Fuse and Circuit Breaker? [2M]
- (e) What is Earthing? [2M]