



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR**  
Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** AEC(16EC411)

**Course & Branch:** B.Tech –EEE


**Year & Sem:** II B.Tech & II-Sem

**Regulation:** R16

**UNIT 1**

**MULTI STAGE AMPLIFIES**

- Derive the equation for the overall voltage gain of a multistage amplifier in terms of the individual voltage gains. [10M]
  - What are multi-stage amplifiers. [2M]
- Describe different methods used for coupling multistage amplifiers with their frequency response. [12M]
- Draw the block diagram of CE-CC cascaded amplifier and analyze its various parameters. [12M]
- Draw the cascode amplifier circuit and derive expressions for voltage gain, current gain, input impedance and output impedance. [12M]
- With neat diagram, analyze the two stage RC coupled amplifier. [12M]
- The following figure shows CE-CE cascade amplifier with their biasing arrangements. Calculate  $R_i$ ,  $A_i$ ,  $A_v$ ,  $R_o$ ,  $A_{vs}$  and  $A_{is}$  if circuit parameters are:  $R_s=1K$ ,  $R_{C1} = 15K$ ,  $R_{E1}= 100\Omega$ ,  $R_{C2} = 4 K\Omega$ ,  $R_{E2} = 330\Omega$  with  $R_1 = 200K$  and  $R_2 = 20K$  for first stage &  $R_1 = 47K$  and  $R_2 = 4.7K$  for second stage. Assume that  $h_{ie} = 1.2k\Omega$ ,  $h_{fe} = 50$ ,  $h_{re} = 2.5 \times 10^{-4}$  and  $h_{oe} = 25 \times 10^{-6} A/V$ . [12M]

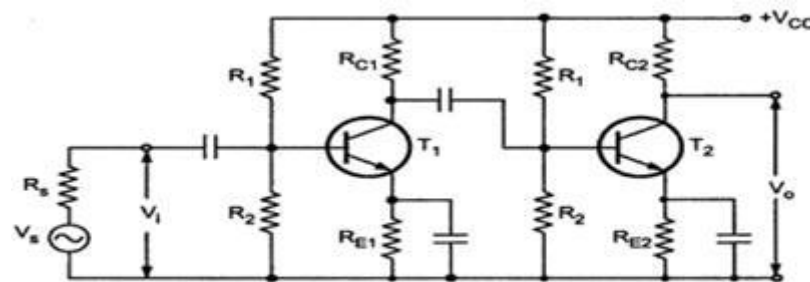

**Fig. CE-CE Cascade amplifier**

- Discuss the concept of gain-bandwidth product. [12M]
- Explain the calculation of bandwidth of single and multi stage amplifier. [12M]
- Draw the block diagram of two stage RC coupled using FET amplifier and its frequency response. [12M]
- Let us consider the two stage amplifier, the first stage in the circuit is a CE amplifier and second stage is CC amplifier, calculate  $R_i$ ,  $A_i$ ,  $A_v$ ,  $R_o$ ,  $A_{vs}$  and  $A_{is}$  if circuit parameters are:  $R_s=1K$ ,  $R_{C1} = 3.3K$ ,  $R_{E2}= 4.7k\Omega$ . Assume that  $h_{ie}= 2k$ ,  $h_{fe} = 50$ ,  $h_{re} = 0$  and  $h_{oe} = 0$ . [12M]

**UNIT-II**  
**FEEDBACK AMPLIFIERS**

1. Explain the characteristics of negative feedback amplifiers. [12M]
2. Calculate the gain, input impedance and output impedance of voltage series feedback Amplifier having gain  $A = -300$ ,  $R_{in} = 1.5 \text{ k}\Omega$  and  $R_{out} = 50 \text{ k}\Omega$ ,  $\beta = 0.05$ . [12M]
3. a) Explain Feedback topologies. [5M]  
b) Give the detailed analysis of Current Series feedback amplifier. [7M]
4. Derive the expressions of input and output resistances for Voltage Shunt Feedback amplifiers. [12M]
5. a) Draw the block diagram of an amplifier with feedback and explain its concept. [6M]  
b) Derive the stabilization gain of negative feedback amplifier. [6M]
6. An amplifier has voltage gain with feedback of 100. if the gain without feedback changes by 20% and the gain with feedback should not vary more than 2%, determine the values of open loop gain  $A$  and feedback ratio  $\beta$ . [12M]
7. Derive the expressions of input and output resistances for current series Feedback amplifiers. [12M]
8. a) A voltage series negative feedback amplifier has a voltage gain without feedback of  $A = 500$ , input resistance  $R_i = 3 \text{ k}\Omega$ , output resistance  $R_o = 20 \text{ k}\Omega$  and feedback ratio  $\beta = 0.01$ . calculate the voltage gain  $A_f$ , input resistance  $R_{if}$  and output resistance  $R_{of}$  of the amplifier with feedback. [5M]  
b) Give the detailed analysis of voltage Series feedback amplifier. [7M]
9. Derive the expressions of input and output resistances for current shunt Feedback amplifiers. [12M]
10. a) Give the detailed analysis of voltage shunt feedback amplifier. [7M]  
b) An amplifier has an open loop gain of 1000 and a feedback ratio of 0.04. if the open loop gain changes by 10% due to temperature, find the percentage change in gain of the amplifier with feedback. [5M]

**UNIT-III**  
**SINUSOIDAL OSCILLATORS**

1. a) Draw the circuit diagram of RC phase shift Oscillator and Explain its working. [7M]  
b) Explain the concept of frequency stability of Oscillators. [5M]
2. a) State and explain Barkhausen criterion of Oscillations. [7M]  
b) In a Hartley oscillator, the value of the capacitor in the tuned circuit is 500 pF and the two sections of coil have inductances 38  $\mu$ H and 12  $\mu$ H. Find the frequency of oscillations and the feedback factor  $\beta$ . [5M]
3. a) Find the frequency of the oscillations of a transistorized Colpitts oscillator having  $C_1 = 150$  pF,  $C_2 = 1.5$ nF and  $L = 50$   $\mu$ H . [5M]  
b) Draw the circuit diagram of a Colpitts Oscillator and explain the principle of operation. [7M]
4. Derive the expression for frequency of Oscillations of a Wein - Bridge Oscillator. [12M]
5. a) In a Hartley oscillator,  $L_2 = 0.4$  mH and  $C = 0.004$   $\mu$ F. if the frequency of the oscillator is 120kHz , find the value of  $L_1$  . Neglect the mutual inductance. [7M]  
b) What is piezoelectric effect? Draw and explain a.c equivalent circuit of a crystal. [5M]
6. Draw the circuit of Hartley oscillator and explain its working. Derive the expressions for frequency of oscillation. [12M]
7. a) Explain the principle of operation of clapp oscillator. [7M]  
b) A tank circuit contains an inductance of 1 mH. Find out the range of tuning capacitor value if the resonant frequency ranges from 540 – 1650 kHz. [5M]
8. a) Draw the circuit diagram of Colpitts oscillator and explain its working. [7M]  
b) In Colpitts oscillator,  $C_1 = 0.2$   $\mu$ F and  $C_2 = 0.02$   $\mu$ F. if the frequency of the oscillator is 10 KHz , find the value of the inductor .Also find the required gain for oscillation. [5M]
9. a) Draw the circuit diagram of tuned collector oscillator and explain its working. [7M]  
b) A tuned collector oscillator in a radio receiver has a fixed inductance of 60  $\mu$ H and has to be tunable over the frequency band of 400 to 1200 kHz. Find the range of variable capacitor to be used. [5M]
10. a) Draw the circuit diagram of Wien- bridge oscillator and explain its working. [7M]  
b) In a Wien – bridge oscillator , if the value of R is 100 K $\Omega$ , and frequency of oscillations is 10 kHz, Find the value of capacitor C. [5M]

**UNIT – IV****LARGE SIGNAL AMPLIFIERS**

1. a) Explain the classification of amplifiers based on the based on biasing condition. [7M]  
b) Write short note on class A amplifiers. [5M]
2. a) Compare series fed and transformed coupled class A amplifiers. [7M]  
b) write short note on power output and efficiency of class A power amplifiers. [5M]
3. a) Explain about transformed coupled class A amplifier. [7M]  
b) Calculate the effective resistance  $R_L'$  seen looking into the primary of a 10:1 transformer connected to an output load of  $16\Omega$ . [5M]
4. a) Draw the circuit diagram of push pull class B amplifier and explain its working principle. [7M]  
b) What are the Advantages & disadvantages of push pull class B amplifier. [5M]
5. A class A power amplifier has zero signal collector current of 100mA. If the collector supply voltage is 5V, determine . [12M]  
a) Maximum a.c power output  
b) Power rating of transistor  
c) Maximum collector efficiency.
6. a) Draw the circuit diagram of complementary symmetry class B amplifier and explain its working principle. [7M]  
b) What are the Advantages & disadvantages of complementary symmetry class B amplifier. [5M]
7. a) Discuss the primary function of phase inverters. [7M]  
b) For a transistor,  $T_j = 160^{\circ}\text{C}$ ,  $T_A = 40^{\circ}\text{C}$ , and  $\Theta_{j-A} = 80^{\circ}\text{C/W}$ . Calculate the power that the transistor can safely dissipate in free air. [5M]
8. a) What are the types of Heat sinks and Explain the concept of power dissipation thermal stability. [7M]  
b) Determine the power dissipation capability of a transistor which has been mounted with a heat sink having thermal resistance  $\Theta_{Hs-A} = 8^{\circ}\text{C/w}$ ,  $T_A = 40^{\circ}\text{C}$ ,  $T_j = 160^{\circ}\text{C}$ ,  $\Theta_{j-A} = 85^{\circ}\text{C/W}$ . [5M]
9. a) Explain about Power dissipation thermal stability for a transistor. [7M]  
b) In a class B amplifier,  $V_{CE}(\text{min}) = 2\text{V}$  and supply voltage  $V_{CC} = 15\text{ v}$ . Find the collector circuit efficiency. [5M]
10. a) what is crossover distortion? Explain. [7M]  
b) In a class B amplifier,  $V_{CE}(\text{min}) = 1\text{V}$  and supply voltage  $V_{CC} = 18\text{ v}$ . Find the collector circuit efficiency. [5M]

**UNIT – V****Linear Wave shaping & Multivibrators**

1. a) Draw a high pass RC circuit and its frequency response . [7M]  
b) How Low pass RC circuit be used as a Integrator. [5M]
2. a) Derive the response of a high pass RC circuit for step Input. [7M]  
b) How High pass RC circuit be used as a Differentiator. [5M]
3. a) Derive the Response of a low pass RC circuit for Step input. [7M]  
b) Determine the upper 3-dB frequency for low pass RC circuit, if a pulse of 0.4  $\mu$ sec is required to pass without distortion. Find the value of resistance if the capacitor is 0.001 $\mu$ F. [5M]
4. a) A Pulse generator with an output resistance  $R_s=500\Omega$  is connected to an oscilloscope with an input capacitance of  $C_i=30$  pF. Determine the fastest rise time that can be displayed. [7M]  
b) Derive the response of a high pass RC circuit for square wave Input. [5M]
5. A 10Hz square wave is fed to an amplifier. Calculate and plot the output waveform under the following conditions: The lower 3 dB frequency is i) 0.3 Hz      ii) 3 Hz      iii) 30 Hz [12M]
6. Explain the basic series clipper above and below reference voltage. [12M]
7. a) Explain the negative clamper circuit with wave forms. [7M]  
b) Explain the positive clamper circuit with wave forms. [5M]
8. a) what is multivibrator? How multivibrators are classified. [7M]  
b) With help of diagram explain the operation of Mono stable Multivibrator. [5M]
9. a) With help of diagram explain the operation of Bi-stable Multivibrator. [7M]  
b) Write a note on free running multivibrator. [5M]
10. With help of diagram explain the operation of Schmitt Tigger circuit using transistors. [12M]