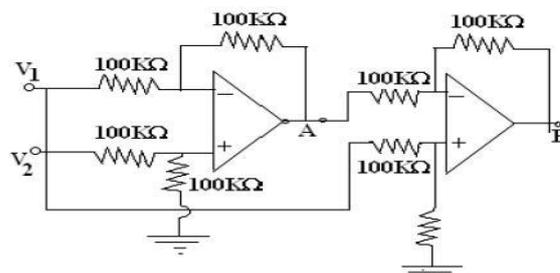


-
- b). Explain about the virtual ground concept. [L2][CO1][4M]
c). Draw the pin configuration of the IC 741 and explain each pin? [L2][CO1][4M]
- 10.a) Explain the importance of TL082 dual JFET input Op-Amp [L2][CO1][6M]
b) Draw the pin configuration of TL081 & TL082 Op-Amp. [L2][CO1][6M]

UNIT -II**FEEDBACK AMPLIFIERS & FREQUENCY RESPONSE**

1. a) Derive the input resistance and output resistance for a voltage shunt feedback Amplifier. [L2][CO2][7M]
 b) In Non-inverting inverting feed back op-amp $R_1 = 10\text{K}\Omega$, $R_f = 100\text{K}\Omega$ and $V_{in} = 1\text{V}$ then the load of $25\text{K}\Omega$ is connected to the output terminal, calculate I_1 , V_o , I_L and I_o . [L2][CO2][5M]
2. a) Explain about the op-amp non-inverting amplifier and derive the voltage gain? [L1][CO2][5M]
 b) Explain voltage series feed back amplifier with Voltage gain and input resistance? [L1][CO2][7M]
3. a) Explain voltage shunt feed back amplifier with Voltage gain and input resistance? [L4][CO2][6M]
 b) Draw the circuit of differential amplifier with one Op-Amp and derive the expression voltage gain? [L1][CO3][6M]
4. a) Define input bias current, input offset current and input offset voltage? [L2][CO2][6M]
 b) Explain about the pole zero frequency compensation network? [L2][CO2][6M]
5. a) Explain about the dominant pole frequency compensation network? [L2][CO2][6M]
 b) Write the difference between compensating and un compensating networks? [L2][CO2][6M]
6. Explain in detail about external frequency compensation techniques with neat sketches.? [L2][CO2][12M]
7. a) Draw and Explain the high frequency equivalent model of the op-amp? [L2][CO2][6M]
 b) Explain about the unity gain bandwidth product that how influences the frequency response? [L2][CO2][6M]
8. a) Derive the expression for closed-loop gain for practical inverting op amp? [L2][CO2][6M]
 b) What is the voltage at point A and B for the circuit shown in figure below, if $V_1 = 5\text{V}$ and $V_2 = 5.1\text{V}$? [L2][CO2][6M]



9. a) Explain the importance of the stability criterion of the op-amp? [L2][CO2][6M]
 b) Define the total input offset voltage and thermal drift? [L2][CO2][6M]
10. a) Explain and derive slew rate and write the importance in op-amp circuits? [L2][CO2][8M]
 b) Compare the open loop and closed loop op-amp? [L2][CO2][4M]

UNIT –III**LINEAR APPLICATIONS AND ACTIVE FILTERS**

- 1.a) Design and explain the operation of inverting summing amplifier? [L2][CO3][6M]
 b) The op-amp non-inverting summing circuit has the following parameters $V_{CC} = +15\text{ V}$, $V_{EE} = -15\text{ V}$, $R_1 = 1\text{ k}\Omega$, $R_f = 2\text{ k}\Omega$, $V_1 = +2\text{ V}$, $V_2 = -3\text{ V}$, $V_3 = +4\text{ V}$. Determine the output voltage V_o . [L2][CO3][6M]
2. Explain & Derive the expression for 3 input non-inverting summing amplifier with circuit diagram? [L2][CO3][12M]
3. a) What is voltage follower? What are its features and applications? [L1][CO3][5M]
 b) Explain & Derive the expression for 2 input subtractor amplifier with circuit diagram? [L2][CO3][7M]
4. Draw the circuit diagram of the instrumentation amplifier and derive the gain? [L1][CO3][12M]
5. a) Write short notes on V-I and I-V converters using op-amps? [L1][CO3][6M]
 b) Derive the expression of Current to Voltage Converter? [L1][CO3][6M]
6. a) Draw a neat circuit of an integrator circuit. Explain the functioning with the input-output Waveforms? [L2][CO3][6M]
 b) Derive the output voltage V_o of practical integrator circuit? [L1][CO3][6M]
7. a) Derive the output voltage V_o of practical differentiator circuit? [L1][CO3][6M]
 b) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 kHz? [L2][CO3][6M]
8. Draw the frequency responses of ideal & practical integrator and differentiator circuits? [L2][CO3][12M]
9. Explain the operation of first order low pass Butterworth filter & derive the expression for filter gain & draw a neat sketch of frequency response? [L2][CO3][12M]
- 10.a) Write the design steps of the second order low pass filter and draw its circuit? [L1][CO3][6M]
 b) Design a second order low pass filter for a cutoff frequency of 100 Hz and draw the circuit diagram? [L1][CO3][6M]

UNIT IV**NON LINEAR APPLICATIONS & SPECIALIZED APPLICATIONS**

- 1.a)What are the conditions to be satisfied by a circuit to produce oscillations? [L1][CO4][5M]
 b)Draw the block diagram of Oscillator and explain its operation? [L3][CO4][7M]
2. Draw the circuit diagram of RC phase shift oscillator and derive the expression for its frequency of oscillations? [L3][CO4][12M]
3. a) Draw and explain the operation of Wein bridge oscillator and derive its frequency expression? [L2][CO4][6M]
 b) Generate a triangular wave from the square wave with a neat expressions? [L1][CO4][6M]
- 4.a) Explain the square wave generator with neat circuit diagram? [L2][CO4][6M]
 b) Explain the saw tooth wave generator with neat circuit diagram? [L2][CO4][6M]
- 5.a) Explain the comparator and zero crossing detector? [L2][CO4][6M]
 b) Explain the operation of Schmitt trigger.Discuss its characteristics and limitations? [L1][CO4][6M]
6. a) Explain in which the 555 timer can be used as monostablemultivibrator? [L1][CO4][6M]
 b) Explain in which the 555 timer can be used as Astablemultivibrator? [L2][CO4][6M]
- 7.a) Discuss the applications of Astablemultivibrator? [L1][CO4][6M]
 b) Draw the block diagram of PLL and explain its operation? [L1][CO4][6M]
- 8.a) Draw the circuit of PLL as frequency multiplier and explain its working? [L1][CO4][6M]
 b) Explain frequency translation and FSK demodulation using 565PLL? [L2][CO4][6M]
- 9.a) What is the purpose of low pass filter in a phase Locked Loop? Describe different types of low pass filters used in a PLL? [L1][CO4][6M]
 b) Explain the performance parameters of multiplier & its characteristics? [L2][CO4][6M]
- 10.Explain in detail about wide bandwidth Precision Multiplier and its Applications? [L2][CO4][12M]

UNIT- V CONVERTERS

- 1.a) Draw and explain the weighted resistor DAC? [L1][CO5][6M]
 b) Explain about ladder type DAC? [L1][CO5][6M]
- 2.a) Explain the operation of Weighted Resistor DAC with the help of circuit Diagram? [L2][CO5][7M]
 b) The basic step of a 9 bit DAC is 10.3 mV. If “000000000” represents 0 V. What output is produced if the input is “101101111”? [L1][CO5][5M]
- 3.LSB of a 9 - bit DAC is represented by 19.6 mv. If an input of 9 zero bits is Represented by 0 volts.
 i. Find the output of the DAC for an input 10110 1101 and 01101 1011?
 ii. What is the full scale reading (FSR) of this DAC? [L1][CO5][12M]
4. Draw and explain in detail about R-2R DAC with an example? [L1][CO5][12M]
- 5.a) Calculate the no. of bits required to represent a full scale voltage of 10 V with a resolution of 5mV approximately? [L1][CO5][4M]
 b) An 8-bit Analog to Digital converter has a supply voltage of +12 volts. Calculate:
 (i) The voltage step size for LSB?
 (ii) The value of analog input voltage for a digital output of 01001011 ? [L1][CO5][8M]
- 6.a) Explain about the sample and hold circuits? [L2][CO5][5M]
 b) Explain about flash type ADC? [L2][CO5][7M]
7. Explain about counter type ADC with neat block diagram? [L2][CO5][12M]
- 8.Draw and explain successive approximation type ADC with an example? [L1][CO5][12M]
- 9.Draw the circuit diagram of single Slope ADC and explain its working with neat Sketches? [L2][CO5][12M]
- 10.Draw the circuit diagram of Dual Slope ADC and explain its working with neat Sketches? [L1][CO5][12M]

Prepared by:

1. **J.Rajanikanth**
Associate Professor/ECE
2. **U.Srinivasulu**
Assistant Professor/ECE
3. **LeenaKumari**
Assistant Professor/ECE