



SIDDHARTH GROUP OF INSTITUTIONS: PUTTUR

Siddharth Nagar, Narayanavanam Road – 517583

Subject: POWER ELECTRONIC CONVERTERS(19EE2112)

Course& Branch: M.Tech -PE


Year & Sem: I-M.Tech & II-Sem

Regulation: R19

UNIT –I

THYRISTORS

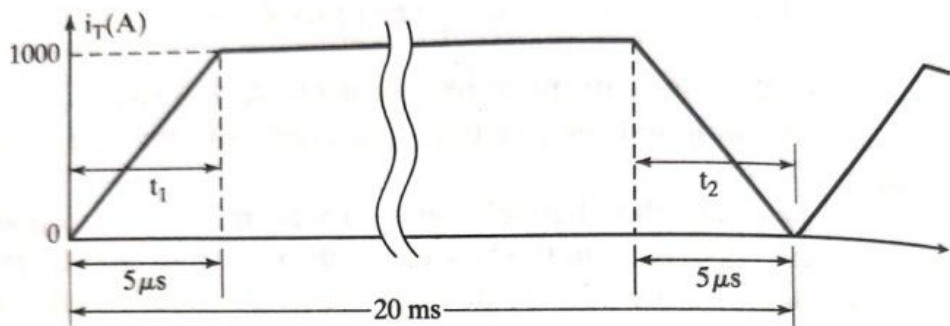1. Explain briefly about Silicon controlled Rectifiers. [12M]
2. What are the turn-off and turn-on characteristics of SCR? [12M]
3. What are the output and transfer characteristics of IGBTs. [12M]
4. a) What is a bipolar transistor and what is the difference between SCR and BJT? [6M]
b) Explain about steady state characteristics of BJT with neat sketch. [6M]
5. a) What is the purpose of shunt snubber and series snubber in transistor? [6M]
b) A thyristor carries a current as shown in figure and the current pulse is repeated at a frequency of $f_s=50\text{hz}$. Determine the average on-state current I_T .



[6M]

6. a) What are the turn-off and turn-on characteristics of MOSFET? [6M]
b) What is the switching model of n-channel MOSFET? [6M]
7. What is meant by commutation? Draw the line commutation and forced commutation circuit for Thyristors. [12M]
8. a) Draw and explain the turn-off and turn-on characteristics of MOSFET? [6M]
b) Two MOSFETs that are connected in parallel, carry a total current of $I_T=20\text{A}$. The drain to source voltage of MOSFET M_1 is $V_{DS1}=2.5\text{V}$ and that of MOSFET M_2 is $V_{DS2}=3\text{V}$. Determine the drain current of each transistor and difference in current sharing if the current sharing series resistances are a) $R_{S1}=0.3\text{ ohm}$ and $R_{S2}=0.2\text{ ohm}$, and b) $R_{S1}=R_{S2}=0.5\text{ohm}$. [6M]
9. Draw and Explain the dynamic characteristics of SCR? [12M]

10. a) Derive an expression for two transistor analogy of a thyristor and explain briefly. [6M]
 b) Explain the construction of IGBT with neat diagram. [6M]

UNIT -II

SINGLE-PHASE & THREE-PHASE AC TO DC CONVERTER

1. Explain about single phase full converter with RL load. [12M]
2. Explain about three-phase dual converter. [12M]
3. a) What is the pulse-width-modulation control of converters? [6M]
 b) The single phase full converter has a RL load having $L=6.5\text{mH}$, $R=0.5\ \text{ohm}$, and $E=10\text{V}$. the input voltage $V_s=120\text{V}$ at (rms) 60hz. Determine a) the load current I_{L0} at $\omega t = \alpha = 60^\circ$ b) the average thyristor current, c) the rms thyristor current d) rms output current e) the critical delay angle. [6M]
4. Explain the principle of operation of phase-controlled converter. [12M]
5. Explain the principle of operation of three-phase half-wave converters. [12M]
6. How does a 12 pulse converter works? and draw the circuit. [12M]
7. State and explain different methods of control of converters. [12M]
8. Derive an output voltage equation for a three phase semi converter with neat circuit and waveforms. [12M]
9. a) The single phase dual converter is operated from a 120v, 60hz supply and load resistance is $R=10\ \text{ohm}$. The circulating inductance is $L_r=40\ \text{mH}$, delay angles are $\alpha_1=60^\circ$ and $\alpha_2=120^\circ$. calculate the peak circulating current and the peak current of converter 1. [6M]
 b) What are the extinction angle controls of converters? [6M]
10. a) Derive an expression for average output current for single phase full converter with RL-Load. [6M]
 b) What are the reactive power considerations of ac-dc converters? [6M]

UNIT -III

DC-DC CONVERTERS

1. Explain the principle of step-down converter with RL-load. [12M]
2. Explain the principle and operation of the step-up converter with RL-load. [12M]
3. Classify the converters based on quadrant operation and explain in detail with neat diagrams. [12M]
4. Analyse the output voltage equation for operation of the step-up converter with neat circuit diagram. [12M]
5. a) What is a dc-dc converter? [6M]
 b) Derive an output voltage equation for a step down converter. [6M]

6. Explain the principle and operation of Buck converter. [12M]
7. With neat circuit diagram and waveforms explain the principle and operation of the Boost converter. [12M]
8. Draw the waveforms for operation of the Buck-Boost converter and explain. [12M]
9. With neat circuit diagram and waveform explain the principle and operation of the cuk converter. [12M]
10. Explain three phase controlled converters with neat sketch. [12M]

UNIT –IV
SINGLE-PHASE INVERTERS

1. Explain the principle of the Three-Phase bridge Inverter with neat circuit diagram and waveforms [12M]
2. a) Classify the inverters based on different aspects. [6M]
b) What is the difference between half-bridge and full-bridge inverters? [6M]
3. Explain the principle and operation of the Voltage source inverters. [12M]
4. Draw the waveforms for three-phase current source inverter and explain in detail. [12M]
5. Explain the principle and operation of the current source inverters. [12M]
6. Draw the waveforms for three-phase inverter when each transistor conducts for 120° . [12M]
7. What are the techniques used for harmonic reductions in inverters? [12M]
8. Evaluate the voltage control of Three-Phase inverters? [12M]
9. Explain briefly about difference between space vector modulation and PWM technique. [12M]
10. Compare the different types of modulation techniques used in inverters. [12M]

UNIT –V
THREE PHASE INVERTERS

1. Explain the principle of the Three-Phase Inverter. [12M]
2. a) What are the types of inverters? explain in detail. [6M]
b) What is the difference between single-Phase and Three-Phase inverters? [6M]
3. With neat circuit diagram explain the principle and operation of the series inverters. [12M]
4. Explain the operation of single-phase inverter and draw the waveforms? [12M]
5. What is parallel inverter ? and explain the operation with neat waveforms. [12M]
6. Draw the waveforms for three-phase inverter when each transistor conducts for 180° . [12M]
7. What are the voltage control techniques of three-phase inverters? [12M]

8. Draw the waveforms for three-phase inverter when each thyristor conducts for 120° . [12M]
9. Explain briefly about difference between voltage control and PWM technique. [12M]
10. Explain the Pulse width modulation techniques used in inverters [12M]

PREPARED BY K.SONIYA

