

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. I Year II Semester Regular & Supplementary Examinations June-2025

ELECTRICAL CIRCUITS ANALYSIS-I

(Electrical & Electronics Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions $10 \times 2 = 20$ Marks)


- | | | | | | |
|---|---|--|-----|----|----|
| 1 | a | Define Independent source and Dependent sources | CO1 | L2 | 2M |
| | b | Write the characteristics of series connection of resistances. | CO1 | L2 | 2M |
| | c | What is Magnetic Motive Force (MMF) in Electrical Engineering? | CO2 | L2 | 2M |
| | d | State dot rule for coupled coils. | CO2 | L1 | 2M |
| | e | Write the impedance equation for series RL, RC, RLC and parallel RL, RC, RLC. | CO3 | L1 | 2M |
| | f | A load consisting of 3Ω resistance and 4Ω inductive reactance draw a current of 10 A when connected to a sinusoidal source. Determine the voltage and power in the load. | CO3 | L2 | 2M |
| | g | How is the resonant frequency related to half-power frequencies in RLC series/parallel circuits? | CO4 | L1 | 2M |
| | h | Write the expression for the quality factor of the series and parallel RLC circuit. | CO4 | L2 | 2M |
| | i | State superposition theorem. | CO5 | L2 | 2M |
| | j | Draw the equivalent circuit of Norton's Theorem and Thevenin's theorem. | CO5 | L1 | 2M |

PART-B

(Answer all Five Units $5 \times 10 = 50$ Marks)


UNIT-I

- | | | | | | |
|---|---|---|-----|----|----|
| 2 | a | Develop transformation formulae for Star to Delta transformation. | CO1 | L1 | 5M |
| | b | Find the voltage V_0 in the circuit shown in | CO1 | L2 | 5M |

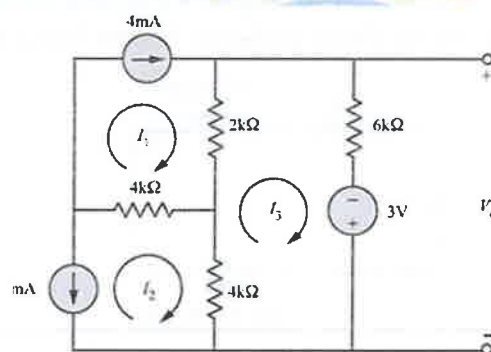

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 3 | a | Explain about Source transformation technique. | CO1 | L2 | 5M |
| | b | Convert the current source into equivalent voltage sources | CO1 | L4 | 5M |

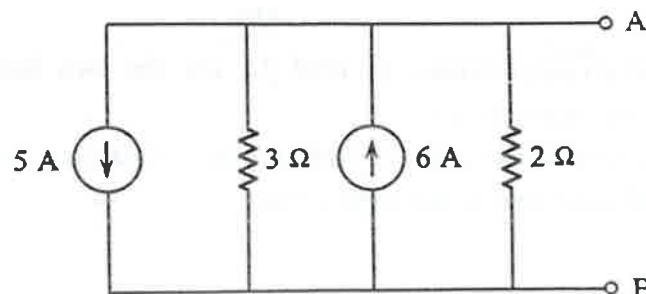

UNIT-II

- 4 a Derive an expression for coefficient coupling. CO2 L3 5M
 b Two coils connected in a series-aiding manner have a total inductance of 275 mH. When connected in a series-opposing configuration, the coils have a total inductance of 125 mH. If the inductance of one coil (L1) is three times the other, find L1, L2, and M. What is the coupling coefficient? CO2 L2 5M

OR


- 5 a Explain the concept of Series and Parallel Magnetic Circuits. CO2 L2 5M
 b A coil having an inductance of 100mH is magnetically coupled to another coil having an inductance of 900mH. The coefficient of coupling between the coils is 0.45. calculate the equivalent inductance if the two coils are connected in (i) series aiding, (ii) series opposing, (iii) parallel aiding, and (iv) parallel opposing. CO2 L2 5M

UNIT-III

- 6 a Determine the series RLC circuit excited by a sinusoidal source CO3 L4 5M
 b A 230V, 50Hz ac supply is applied to a coil of 0.06H inductance and 2.5Ω resistance connected in series with a 6.8μF capacitor. Calculate (i) impedance (ii) current (iii) phase angle between current and voltage (iv) power factor (v) power consumed. CO3 L2 5M

OR


- 7 a Describe the sinusoidal function and explain the phasor and phasor diagram concepts. CO3 L5 6M
 b A resistance of 7Ω is connected in series with a pure inductance of 31.8 mH and the circuit is connected to a 100 V, 50 Hz sinusoidal supply. Calculate i) circuit current ii) Phase angle iii) Power factor iv) Power. CO3 L2 4M

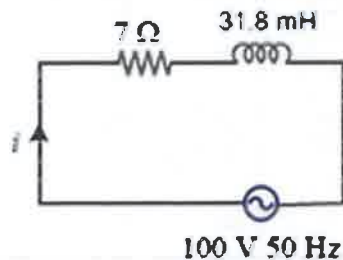**UNIT-IV**

- 8 a Draw the Locus diagram of a Series RL Circuit. CO4 L2 6M
 b Obtain an expression for resonant frequency in a parallel resonant circuit. CO4 L2 4M
- OR**
- 9 a Prove that $f_0 = \sqrt{f_l f_h}$ where f_l and f_h are the two half power frequencies of a resonant circuit. CO4 L4 5M
 b A RLC series circuit of $R=16\Omega$, $L=5\text{mH}$, $C=2\mu\text{F}$. Calculate the quality factor, bandwidth, and half-power frequencies. CO4 L2 5M


UNIT-V

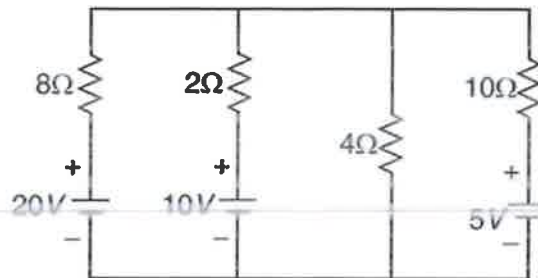- 10 a State Millman's theorem and derive an expression for Millman's equivalent source of n number of parallel connected voltage sources. CO5 L2 5M
- b Using Millman's theorem, find current through 4Ω resistance for the following circuit. CO5 L4 5M




OR

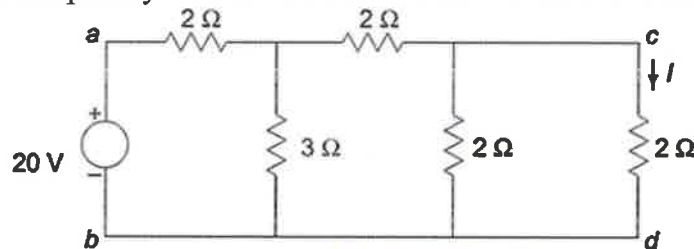- 11 a Verify the reciprocity theorem for the network shown in the circuit. CO5 L2 5M



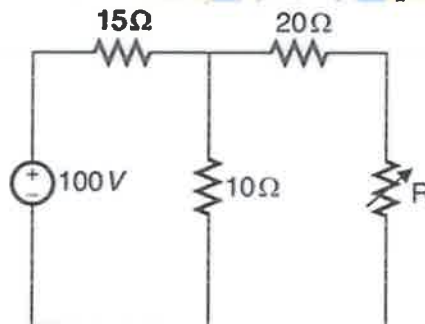- b In the circuit shown, find the value of adjustable resistor R for maximum power transfer to R . Also, calculate the maximum power. CO5 L2 5M



***** END *****

