

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. I Year II Semester Regular & Supplementary Examinations June-2025
NETWORK ANALYSIS

(Electronics & Communications Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions $10 \times 2 = 20$ Marks)


- | | | | | | |
|---|---|---|-----|----|----|
| 1 | a | Define statement of Tellegen's theorem. | CO1 | L1 | 2M |
| | b | Define statement of Reciprocity theorem. | CO1 | L1 | 2M |
| | c | State Final value theorem. | CO2 | L1 | 2M |
| | d | What is the significance of initial conditions. | CO2 | L1 | 2M |
| | e | Draw the impedance triangle of series R-L circuit with sinusoidal supply. | CO3 | L2 | 2M |
| | f | What is the phase of a sine wave? | CO3 | L1 | 2M |
| | g | Define Self-inductance. | CO4 | L1 | 2M |
| | h | Define Q- Factor. | CO4 | L1 | 2M |
| | i | What is the condition for Symmetry in Z and Y parameters. | CO5 | L1 | 2M |
| | j | Draw the equivalent circuit of Z-parameters. | CO5 | L1 | 2M |

PART-B


(Answer all Five Units $5 \times 10 = 50$ Marks)

UNIT-I

- | | | | | | |
|---|---|---|-----|----|----|
| 2 | a | By using source transformation, convert the circuit shown in figure below into a single voltage source and single resistance. | CO1 | L3 | 5M |
|---|---|---|-----|----|----|

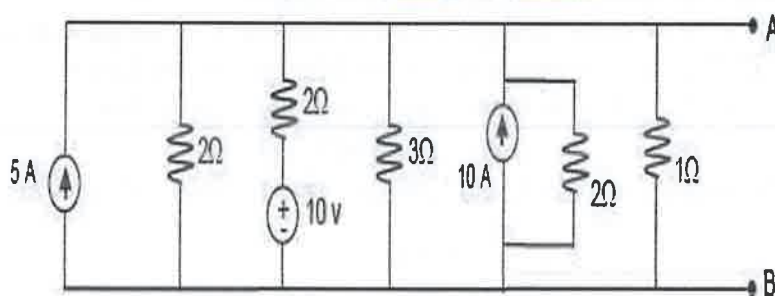


- | | | | | |
|---|---|-----|----|----|
| b | Find the Norton's equivalent across AB for the given circuit. | CO1 | L3 | 5M |
|---|---|-----|----|----|

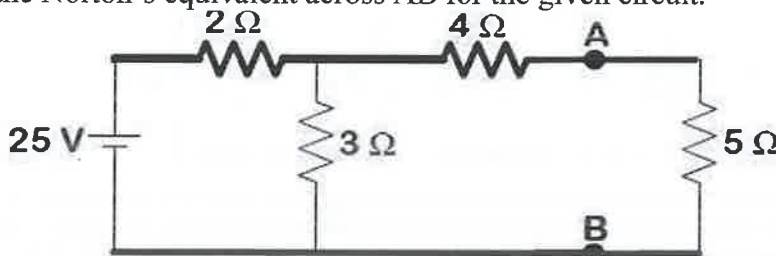

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 3 | a | Define independent source and dependent source, what are the types of dependent sources. | CO1 | L2 | 5M |
| | b | Find the Thevenin's equivalent circuit across AB for the given circuit. | CO1 | L3 | 5M |

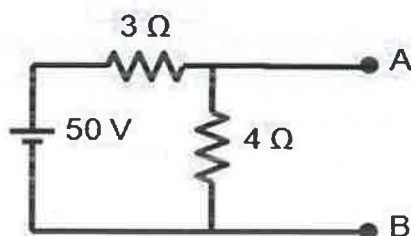

UNIT-II

- 4 a Find the Inverse Laplace transform of given $F(s)$ using Heaviside's expansion theorem. CO2 L3 5M

$$F(s) = \frac{(s+2)}{s(s+3)(s+4)}$$

- b Find the Laplace transform of $\sin \omega t$. CO2 L3 5M

OR

- 5 a A circuit has resistance of 1000Ω and a series capacitance of $0.1\mu F$. At $t = 0$, it is connected to a 12 V battery. CO2 L3 5M

Find the following:


- i) The current at $t = 0$
ii) Rate of change of current at $t = 0$

Rate of change of capacitor voltage at $t = 0$

- b A coil having a resistance of 100Ω and an inductance of 20 H is connected to a 200 V DC source. Suddenly, the coil is disconnected from the battery and short-circuited. Calculate the following: CO2 L3 5M

- i) The current in the coil at $t = 0$
ii) Rate of change of current at $t = 0$

Time constant

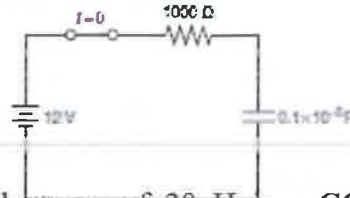

UNIT-III


- 6 Derive the necessary relations for performing star to delta and delta to star transformations CO3 L1 10M

OR

- 7 a Explain phasor representation of series R L circuit CO3 L2 6M
b A voltage of 120 V at 50 Hz is applied to a resistance, R in series with a capacitance, C . The current drawn is 2 A, and the power loss in the resistance is 100 W. Calculate the resistance and the capacitance CO3 L3 4M

UNIT-IV

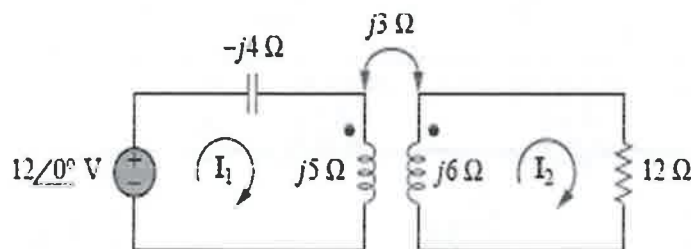- 8 Calculate the phasor currents I_1 and I_2 in the circuit shown in Figure. CO4 L2 10M



OR

- 9 a A parallel resonant circuit is driven by ac mains supply 230V, 50Hz. Find value of C required to be varied to achieve antiresonance in the circuit if it is shunted with a coil of 1mH inductance and 10Ω resistance CO4 L2 5M
b Derive an equation for the resonance frequency of a series resonant circuit in terms of L and C . CO4 L2 5M


UNIT-V

- 10 Obtain the ABCD parameters in terms of Z parameters and find ABCD parameters for the given Z -parameters of a two-port network, $Z_{11} = 10\Omega$, $Z_{22} = 15\Omega$, $Z_{12} = 5\Omega$ and $Z_{21} = 5\Omega$ CO5 L2 10M

OR


- 11 a Find the Short-circuit parameters for the circuit shown in figure.

C05 L3 5M

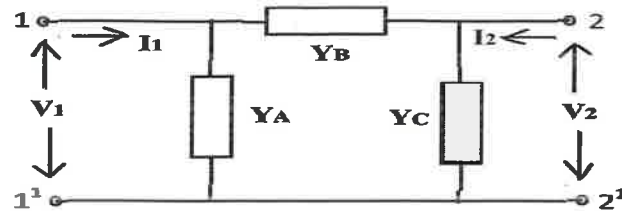

- b Find the transmission parameters for the circuit shown in figure.

C05 L3 5M

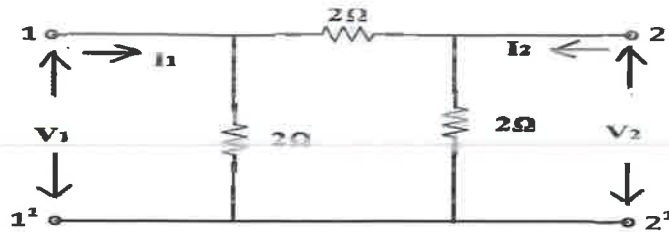

*** END ***



