

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. II Year I Semester Regular Examinations February-2025

DIGITAL CIRCUITS DESIGN

(Electronics & Communications Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- | | | | | | |
|---|---|---|-----|----|----|
| 1 | a | Write the truth table for $F=(A+B)(C+D)$. | CO1 | L2 | 2M |
| | b | List out the types of number systems with one example for each. | CO1 | L2 | 2M |
| | c | Define a Combinational Circuit and draw its block diagram. | CO4 | L1 | 2M |
| | d | List the applications of encoder and decoder. | CO4 | L1 | 2M |
| | e | Explain about the module representation of logic circuits in Verilog. | CO6 | L1 | 2M |
| | f | Differentiate between Verilog and VHDL. | CO6 | L4 | 2M |
| | g | What is sequential circuit? | CO4 | L1 | 2M |
| | h | Difference between Latch and Flip-flop. | CO4 | L4 | 2M |
| | i | State the types of ROM. | CO5 | L1 | 2M |
| | j | List the major differences between PLA and PAL. | CO5 | L1 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|---|---|--|-----|----|----|
| 2 | a | Convert the following numbers:
i) $(AB)_{16}=()_2$ ii) $(1234)_8=()_{16}$ | CO1 | L1 | 5M |
| | b | Explain about the Binary Codes in detail. | CO1 | L2 | 5M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 3 | a | Simplify the expression in S O P form using don't cares.
$Y = \Sigma (4,5,6,8,9) + d \Sigma (3,7,10,11,14,15)$ | CO2 | L4 | 5M |
| | b | State and prove the following Boolean laws:
i) Commutative ii) Associative | CO2 | L3 | 5M |

UNIT-II

- | | | | | | |
|---|---|--|-----|----|----|
| 4 | a | Design & implement Half Adder and Half subtractor logic circuit using truth table. | CO4 | L3 | 5M |
| | b | Explain the working of a Carry- Look ahead adder. | CO4 | L2 | 5M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 5 | a | Define Demultiplexer? Design an 1:8 demultiplexer using two 1:4 demultiplexer. | CO4 | L3 | 5M |
| | b | Draw the circuit for 3 to 8 decoder and explain. | CO4 | L2 | 5M |

UNIT-III

- | | | | | | |
|---|--|--|-----|----|-----|
| 6 | | Explain about the Hierarchical Verilog code with an example. | CO6 | L1 | 10M |
|---|--|--|-----|----|-----|

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 7 | a | Write an Verilog code for Half Adder and Full Subtractor with the help of Truth tables. | CO6 | L1 | 5M |
| | b | State the importance of CAD Tools in HDL. | CO6 | L1 | 5M |

UNIT-IV

- | | | | | | |
|---|---|--|-----|----|----|
| 8 | a | Design T Flip Flop using JK Flip-Flop and explain its logic diagram. | CO4 | L3 | 5M |
| | b | Explain the working principle of RS Flip-Flop with the help of logic Diagram and give its Characteristic Table and Graphic symbol. | CO4 | L2 | 5M |

OR

- | | | | | | |
|---|--|--|-----|----|-----|
| 9 | | Define a Shift register and explain its types. | CO4 | L2 | 10M |
|---|--|--|-----|----|-----|

UNIT-V

- | | | | | | |
|----|--|---|-----|----|-----|
| 10 | | Explain and Design a Sequence Detector. | CO2 | L2 | 10M |
|----|--|---|-----|----|-----|

OR

- | | | | | | |
|----|--|---|-----|----|-----|
| 11 | | Illustrate the PAL for the following Boolean functions.
(i) $A(w,x,y,z) = \Sigma m(0,2,6,7,8,9,12,13)$
(ii) $B(w,x,y,z) = \Sigma m(0,2,6,7,8,9,12,13,14)$ | CO5 | L3 | 10M |
|----|--|---|-----|----|-----|

*** END ***

135
~~135~~