

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. II Year I Semester Regular Examinations February-2025

ELECTRICAL CIRCUIT ANALYSIS-II

(Electrical & Electronics Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- | | | | | | |
|---|---|--|-----|----|----|
| 1 | a | List the advantages of three phase system. | CO1 | L1 | 2M |
| | b | A star connected load consists of 25Ω resistance in series with 15mH inductance in each phase. If the supply is 415V , 60Hz , find line current. | CO1 | L3 | 2M |
| | c | Find the Laplace transform of exponential function $f(t) = e^{at}$. | CO2 | L4 | 2M |
| | d | An RLC series circuit with $R = 5\Omega$ is excited by a dc source of 10V by closing the switch at $t = 0$. Draw the initial and final conditions of the circuit. | CO2 | L3 | 2M |
| | e | Why are the ABCD parameters termed transmission parameters? | CO3 | L1 | 2M |
| | f | Define Z-parameters. | CO3 | L1 | 2M |
| | g | Write the steps for application of Fourier transform to circuit analysis. | CO4 | L1 | 2M |
| | h | Write the equation for an alternative to the trigonometric (or sine-cosine) Fourier series. | CO4 | L1 | 2M |
| | i | Write the characteristic equations of T and II network? | CO5 | L1 | 2M |
| | j | What is a filter? Classify them. | CO5 | L2 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|---|--|---|-----|----|-----|
| 2 | | Show that three-phase power can be measured by two wattmeter's. Draw the phasor diagrams. Derive an expression for power factor in terms of wattmeter readings. | CO1 | L2 | 10M |
|---|--|---|-----|----|-----|

OR

- | | | | | | |
|---|--|---|-----|----|-----|
| 3 | | A three-phase balanced delta-connected load of $4+j8\Omega$ is connected across a 400V , three-phase balanced supply. Determine the phase currents and line currents. Assume the phase sequence to be RYB. Also, calculate the power drawn by the load. Sketch the phasor diagram. | CO1 | L3 | 10M |
|---|--|---|-----|----|-----|

UNIT-II


- | | | | | | |
|---|------|--|-----|----|-----|
| 4 | | Derive shifting theorem of Laplace transform. | CO2 | L4 | 10M |
| | i. | Find the Laplace transform of $e^{at} \sin bt$. | | | |
| | ii. | Find the Laplace transform of $(t+2)^2 e^t$. | | | |
| | iii. | If $u(t) = 1$, for $t \geq 0$ and $u(t) = 0$ for $t < 0$, determine the Laplace transform of $[u(t) - u(t-a)]$. | | | |

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 5 | a | Derive a differentiation of Laplace transform and find the Laplace transform of function $f(t) = t \sin 2t$. | CO2 | L3 | 5M |
| | b | Define of Inverse Laplace Transform and find the function $f(t)$ If $F(s) = \frac{2}{(s+1)(s+5)}$ | CO2 | L3 | 5M |

UNIT-III

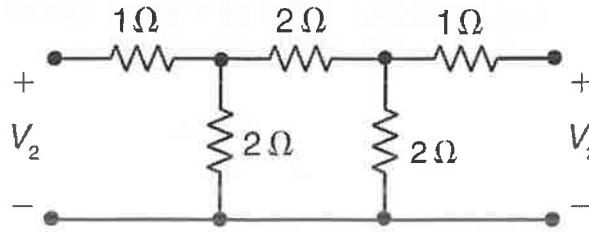- 6 a Find the transmission parameters for the network shown in Figure CO3 L3 5M considering two networks connected in cascade.




- b Two two-port networks are connected in parallel. Prove that the overall y-parameters are the sum of corresponding individual y-parameters. CO3 L4 5M

OR

- 7 a Express Z-parameters in terms of Hybrid-parameters and ABCD parameters for a two-port network. CO3 L4 5M
- b Determine the h-parameter with the following data: CO3 L2 5M
- (i) with the output terminals short-circuited,
 $V_1 = 25 \text{ V}, I_1 = 1 \text{ A}, I_2 = 2 \text{ A}$
- (ii) with the input terminals open-circuited,
 $V_1 = 10 \text{ V}, V_2 = 50 \text{ V}, I_2 = 2 \text{ A}$

UNIT-IV

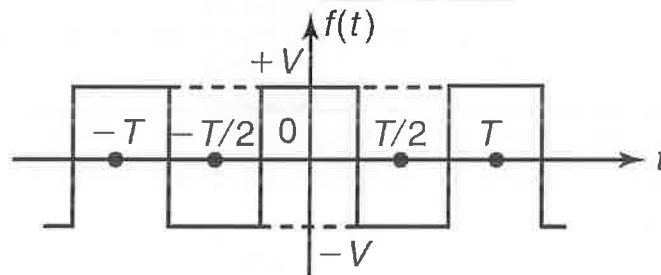- 8 Determine the Fourier series for the square waveform shown below and plot the magnitude and the phase spectra. CO4 L4 10M



OR

- 9 Show that the Fourier series expansion of a periodic function with odd (rotation) symmetry contains only the sine terms and even (mirror) symmetry contains only the cosine terms plus a constant. CO4 L1 10M

UNIT-V

- 10 Explain in the detail with neat illustrations the Constant-k filters of High pass and Low pass network and derive the network parameters. CO5 L2 10M

OR

- 11 a Design a constant K-type HPF having a cut-off frequency of 5500 Hz and a design impedance of 750 Ω. Draw T-section filter and π-Section filter. CO5 L3 5M
- b Design the high pass RL filter and illustrate the frequency-phase response curve. CO5 L1 5M

*** END ***