

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)

B.Tech. II Year I Semester Regular Examinations February-2025

ELECTRONIC DEVICES AND CIRCUITS
(Electronics & Communications Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- | | | | | | |
|---|---|--|-----|----|----|
| 1 | a | Define clipper and list types. | CO4 | L2 | 2M |
| | b | Formulate the Diode current equation. | CO2 | L1 | 2M |
| | c | Define BJT and Draw its symbol. | CO1 | L1 | 2M |
| | d | List applications of BJT. | CO1 | L1 | 2M |
| | e | What is the trans conductance g_m in a BJT? | CO2 | L1 | 2M |
| | f | Name the applications of CC amplifier. | CO1 | L1 | 2M |
| | g | Define Pinchoff Voltage. | CO2 | L1 | 2M |
| | h | Draw the CMOS structure. | CO1 | L1 | 2M |
| | i | List the small-Signal Parameters of MOSFET. | CO1 | L1 | 2M |
| | j | Draw an alternative representation of the T model. | CO5 | L1 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|---|---|---|-----|----|----|
| 2 | a | Discuss about the forward and reverse resistances of a PN junction diode. | CO1 | L2 | 5M |
| | b | Calculate the forward resistance of a PN Junction Diode when the forward current is 5mA at $T = 300$ K. Assume Silicon diode. | CO3 | L3 | 5M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 3 | a | Define the basic principle of Varactor diode and list its applications. | CO1 | L1 | 3M |
| | b | Draw the circuit symbol of Tunnel diode. Explain the VoltAmpere (V-I) characteristics. | CO2 | L2 | 7M |

UNIT-II

- | | | | | | |
|---|---|--|-----|----|----|
| 4 | a | Derive the relation among α , β and γ of a Transistor. | CO2 | L2 | 5M |
| | b | If the base current in a transistor is $20\mu A$ when the emitter current is $6.4mA$, what are the values of α and β ? Also calculate the collector current. | CO3 | L3 | 5M |

OR


- | | | | | | |
|---|---|--|-----|----|----|
| 5 | a | Differentiate among CE, CB & CC configurations. | CO4 | L2 | 5M |
| | b | Discuss the Input and Output characteristics of a BJT in CE Configuration. Indicate the regions of operations in the output characteristics. | CO4 | L3 | 5M |

UNIT-III

- | | | | | | |
|---|---|---|-----|----|----|
| 6 | a | Derive the transconductance g_m for a given collector current I_C . | CO2 | L2 | 5M |
| | b | Determine base current and input resistance at Base of BJT. | CO1 | L3 | 5M |

OR

- | | | | | | |
|---|--|---|-----|----|-----|
| 7 | | For the common emitter amplifier shown in figure $V_{cc} = 9V$, $R_1 = 27 k\Omega$, $R_2 = 15 k\Omega$, $R_E = 1.2 k\Omega$ and $R_c = 2.2 k\Omega$. The transistor has $\beta = 100$, $V_A = 100 V$. Calculate the DC bias current I_E . If the amplifier operates between source for which $R_{sig} = 10 k\Omega$ and a load of $2 k\Omega$, replace the transistor with its hybrid π model, and Compute the values of R_{in} , Voltage gain V_o/V_{sig} . | CO3 | L4 | 10M |
|---|--|---|-----|----|-----|

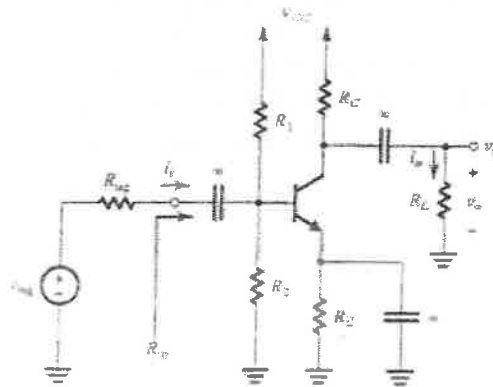


UNIT-IV

- 8 a Discuss the Transfer and output characteristics of N-channel JFET with neat sketches. CO4 L6 5M
b Distinguish between Depletion MOSFET and Enhancement MOSFET. CO6 L5 5M


OR

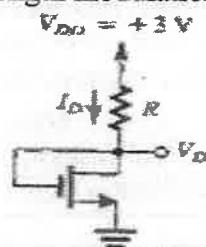- 9 a Distinguish between BJT and FET. CO6 L2 5M
b Design the circuit in Fig. below to obtain a current I_D of $80 \mu A$. Find the value required for R , and find the dc voltage V_D . Let the NMOS transistor have $V_t = 0.6 V$, $\mu_n C_{ox} = 200 \mu A/V^2$, $L = 0.8 \mu m$, and $W = 4 \mu m$. Neglect the channel-length modulation effect (i.e., assume $\lambda = 0$). CO5 L1 5M



UNIT-V

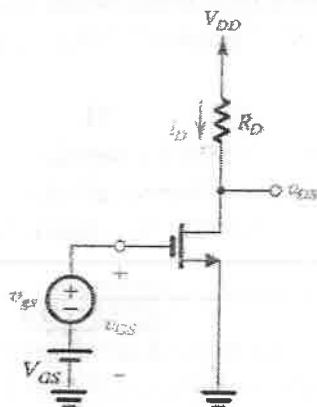- 10 a Explain the separating the DC Analysis and the Signal Analysis CO4 L2 5M
b CO5 L3 5M



For the above amplifier, let $V_{DD} = 5V$, $R_D = 10K\Omega$, $V_t = 1V$, $K'_n = 20 \mu A/V^2$, $W/L = 20$, $V_{GS} = 2V$, and $\lambda = 0$. Determine

- i) the dc current I_D and dc voltage V_{DS}
ii) g_m
iii) Voltage gain iv) If $V_{GS} = 0.2 \sin \omega t$, find V_{DS}

OR

- 11 a Define the MOSFET Transconductance g_m with mathematical expression. CO3 L1 3M
b Develop and Illustrate the T Equivalent-Circuit Model for the MOSFET. CO5 L5 7M

*** END ***