

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. I Year I Semester Regular & Supplementary Examinations December/January-2025/2026
BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Common to CSE, EEE & CSIT)

Time: 3 Hours

*Note: Answer **PART-A** from pages 2 to 20 and **PART-B** from 21 to 39.

Max. Marks: 70

PART-A (ELECTRICAL)

(Answer all the Questions 5 x 1 = 5 Marks)

1 a Define Active Power.	CO1 L2 1M
b Define Faradays law.	CO2 L1 1M
c Which instrument is used to measure the DC quantity?	CO2 L1 1M
d What are the Conventional Energy sources?	CO3 L1 1M
e What is the power rating of Air Conditioner and Fan?	CO3 L1 1M

(Answer all Three Units 3 x 10 = 30 Marks) (ELECTRICAL)

UNIT-I

2 a What are the equations of AC Voltage and Current.	CO1 L1 2M
b Define the following	CO1 L2 8M
i)Waveform, ii) Time period, iii) frequency, iv) Amplitude	

OR

3 a Derive voltage and current relationship with Phasor diagram in resistive circuit.	CO1 L4 5M
b Derive voltage and current relationship with Phasor diagram in inductive circuit	CO1 L4 5M

UNIT-II

4 Draw and Explain the constructional diagram of a single phase transformer.	CO2 L4 10M
--	------------

OR

5 a Explain the operating principles of Moving Iron instruments	CO2 L2 5M
b Determine the unknown resistance using Wheatstone bridge	CO2 L3 5M

UNIT-III

6 What is solar power plant? Explain the operation with layout	CO3 L1 10M
--	------------

OR

7 a What are the functions of electric fuse?	CO3 L1 5M
b What is an electric shock? How to prevent electric shock at home?	CO3 L1 5M

PART-B(ELECTRONICS)

(Answer all the Questions 5 x 1 = 5 Marks)

1 f Define biasing.	CO1 L1 1M
g What is meant by semiconductor?	CO1 L4 1M
h What is a step-down transformer?	CO2 L3 1M
i What is the necessary of the coupling capacitor?	CO2 L4 1M
j Write the names of basic logical operators.	CO3 L3 1M

(Answer all Three Units 3 x 10 = 30 Marks) (ELECTRONICS)

UNIT-IV

8 With the neat sketch ,Explain the operation of an NPN transistor and PNP transistor.	CO1 L3 10M
--	------------

OR

9 With a neat sketch Explain the input and output and current gain characteristics of a transistor in common Emitter (CE) configuration.	CO1 L1 10M
--	------------

UNIT-V

10 Explain the working of a full wave bridge rectifier with a neat diagram with wave forms.	CO2 L1 10M
---	------------

OR

11 Draw the block diagram of Public Addressing System and explain the function of each block.	CO2 L3 10M
---	------------

UNIT-VI

12 Explain about Logic gates with symbols and truth table.	CO3 L1 10M
--	------------

OR

13 Define combinational circuit? Explain Half Adder and Full Adder with truth table.	CO3 L2 10M
--	------------

***** END *****