

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations June-2024

ANALOG ELECTRONIC CIRCUITS

(Common to EEE, CSE & CSIT)

Time: 3 Hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | | | |
|---|---|---|-----|----|----|
| 1 | a | Draw the VI characteristics of PN diode. | CO1 | L1 | 2M |
| | b | Write the relation between β and α . | CO2 | L2 | 2M |
| | c | Write the advantages of FET. | CO3 | L1 | 2M |
| | d | Define an operational amplifier. | CO4 | L1 | 2M |
| | e | Write the specifications of ADC and DAC. | CO5 | L1 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|---|---|--|-----|----|----|
| 2 | a | Explain the formation of depletion layer in a PN junction. | CO1 | L1 | 5M |
| | b | Write the different applications of PN junction diode. | CO1 | L2 | 5M |

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 3 | a | Draw and discuss the VI characteristics of a Zener Diode. | CO1 | L2 | 5M |
| | b | Write notes on Diode Clippers and Clampers with diagram. | CO1 | L1 | 5M |

UNIT-II

- | | | | | | |
|---|---|--|-----|----|----|
| 4 | a | With neat diagram explain the operation of NPN transistor. | CO2 | L2 | 5M |
| | b | Explain the Input and Output characteristics of a BJT in CB configuration. | CO2 | L2 | 5M |

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 5 | a | Write the difference between CB, CE and CC configurations of BJT. | CO2 | L4 | 5M |
| | b | Write the applications of CB, CE and CC amplifiers. | CO2 | L2 | 5M |

UNIT-III

- | | | | | | |
|---|---|--|-----|----|----|
| 6 | a | With the help of neat diagram, explain the operation and characteristics of n-channel enhancement type MOSFET. | CO3 | L2 | 8M |
| | b | Write the difference between FET and BJT. | CO3 | L2 | 2M |

OR

- | | | | | |
|---|--|-----|----|-----|
| 7 | | CO3 | L2 | 10M |
| | Discuss the operation and characteristics of n-channel depletion type MOSFET with diagram. | | | |

UNIT-IV

- 8 a Draw the various functional blocks of an operational amplifier. Explain each block. CO4 L2 6M
- b Compare different configurations of differential amplifier. CO4 L2 4M

OR

- 9 a With the help of diagram, explain frequency response of practical op-amp. CO4 L2 5M
- b Design an inverting amplifier with gain $A=20$ CO4 L3 5M

UNIT-V

- 10 a Draw the circuit of a difference amplifier with one op-amp and derive the expression for voltage gain. CO5 L2 5M
- b With the help of circuit diagram explain instrumentation amplifier and derive the gain. CO5 L2 5M

OR

- 11 a Explain about flash type ADC. CO5 L1 5M
- b Draw and explain in detail about R-2R DAC CO5 L2 5M

***** END *****