

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations June-2024

DIGITAL SYSTEM DESIGN

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | | | |
|---|---|---|-----|----|----|
| 1 | a | Convert decimal 27.315 to binary. | CO1 | L1 | 2M |
| | b | Minimize the following Boolean function using K-map
$F(A, B, C, D) = \sum m(1, 4, 5, 6, 12, 13, 14, 15)$. | CO1 | L1 | 2M |
| | c | Compare Synchronous and Ripple counters. | CO2 | L2 | 2M |
| | d | Briefly Explain about ECL. | CO2 | L2 | 2M |
| | e | Explain the structure of a VHDL program. | CO5 | L2 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|---|---|---|-----|----|----|
| 2 | a | Perform the following subtraction using 9's complement for the given.
i) 54321-41245 ii) 1231-4145 | CO1 | L1 | 5M |
| | b | Subtraction by using 1's complement for the given.
i) 111011-110110 ii) 10001-10011 | CO1 | L1 | 5M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 3 | a | Express the Boolean function $F = A + B'C$ as a sum of minterms. | CO1 | L1 | 5M |
| | b | Express the Boolean function $F = XY + X'Z$ as a product of maxterm. | CO1 | L1 | 5M |

UNIT-II

- | | | | | | |
|---|--|--|-----|----|-----|
| 4 | | Simplify the following Boolean function for minimal SOP & POS form using K-map.
i) $F(A, B, C, D) = \sum (0, 1, 2, 5, 8, 9, 10)$
ii) $F(A, B, C, D) = \pi(1, 3, 5, 7, 12, 13, 14, 15)$. | CO3 | L2 | 10M |
|---|--|--|-----|----|-----|

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 5 | a | Implement the following Boolean function using 4:1 Multiplexer.
$F(A, B, C) = \sum (1, 2, 6, 7)$. | CO4 | L3 | 5M |
| | b | Design a 1:4 Demultiplexer and mention the applications of a DEMUX. | CO4 | L1 | 5M |

UNIT-III

- | | | | | | |
|---|---|---|-----|----|----|
| 6 | a | Draw the logic diagram of a JK – flip flop and explain its operation. | CO3 | L4 | 5M |
| | b | What is the need for Master Slave JK FF and explain its operation with neat diagrams. | CO3 | L2 | 5M |

OR

- | | | | | | |
|---|---|--|-----|----|----|
| 7 | a | Design a Positive edge triggered Master-Slave D flip flop. | CO3 | L2 | 4M |
| | b | Design and implement a BCD Ripple counter using JK Flip Flops. | CO3 | L3 | 6M |

UNIT-IV

- | | | | | | |
|---|--|--|-----|----|-----|
| 8 | | Implement the following functions using a PLA.
i) $f_1(w, x, y) = \sum m(3, 5, 6, 7)$ ii) $f_2(w, x, y) = \sum m(0, 2, 4, 7)$ | CO3 | L4 | 10M |
|---|--|--|-----|----|-----|

OR

- 9 a Derive the PLA programming table for the combinational circuit that squares a 3-bit number. CO4 L2 5M
b Compare three combinational circuits: PLA, PAL and ROM. CO4 L1 5M

UNIT-V

- 10 Explain in detail different modeling styles of VHDL with suitable examples. CO5 L2 10M

OR

- 11 a Write a VHDL program for Full adder. CO5 L5 5M
b Write a VHDL program for 3 to 8 Decoder. CO5 L5 5M

***** END *****