

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year I Semester Supplementary Examinations June-2024**

**ELECTRICAL CIRCUITS-II**

(Electrical & Electronics Engineering)

**Time: 3 Hours**

**Max. Marks: 60**

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- |   |   |  |     |    |    |
|---|---|--|-----|----|----|
| 1 | a | What is star and delta connection?                                       | CO1 | L1 | 2M |
|   | b | Define the time constant of RL circuit.                                  | CO2 | L1 | 2M |
|   | c | Define tree of a network.  | CO3 | L1 | 2M |
|   | d | What are hybrid parameters of two-port network?                          | CO4 | L1 | 2M |
|   | e | What are the advantages of laplace transform in the analysis of circuit? | CO5 | L1 | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |   |   |   |     |    |    |
|---|---|---|-----|----|----|
| 2 | a | Derive the relationship between Phase and Line voltages, currents in delta connected load.  | CO1 | L3 | 5M |
|   | b | A balanced star connected load having an impedance $(15+j20) \Omega$ per phase is connected to a three phase 440 V, 50Hz supply. Find line currents and phase voltages. Assume RYB phase sequence and also calculate power drawn by the load. | CO1 | L3 | 5M |

**OR**

- |   |   |   |     |    |    |
|---|---|---|-----|----|----|
| 3 | a | Explain two watt meter method for power measurement in three phase circuits   | CO1 | L2 | 5M |
|   | b | Three impedances $Z_1=20$ , $Z_2=40$ , $Z_3=10$ are delta connected to a 400V, $3\phi$ System. Determine i) phase currents ii) line currents iii) total power consumed by the load. | CO1 | L3 | 5M |

**UNIT-II**


- |   |  |  |     |    |     |
|---|--|--|-----|----|-----|
| 4 |  | Derive the transient response of an RLC circuit with dc excitation | CO2 | L3 | 10M |
|---|--|--|-----|----|-----|

**OR**


- |   |   |   |     |    |    |
|---|---|---|-----|----|----|
| 5 | a | Derive the transient response of an RL circuit with AC excitation.  | CO2 | L3 | 5M |
|   | b | A series RC circuit consists of resistor of 10 and capacitor of 0.1F has a constant voltage of 20v is applied to the circuit at $t=0$ . obtain the current equation. Determine the voltage across the resistor and the capacitor. | CO2 | L3 | 5M |

**UNIT-III**

- |   |   |  |     |    |    |
|---|---|--|-----|----|----|
| 6 | a | Find the cutset matrix for the followings? | CO3 | L3 | 5M |
|---|---|--|-----|----|----|

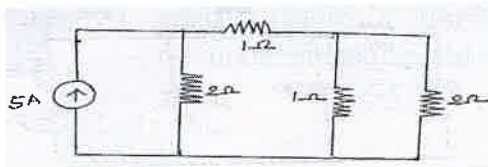


- |  |   |  |     |    |    |
|--|---|--|-----|----|----|
|  | b | Find the tieset matrix for the followings? | CO3 | L3 | 5M |
|--|---|--|-----|----|----|

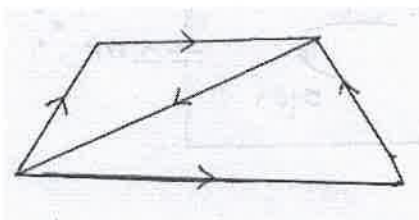


OR

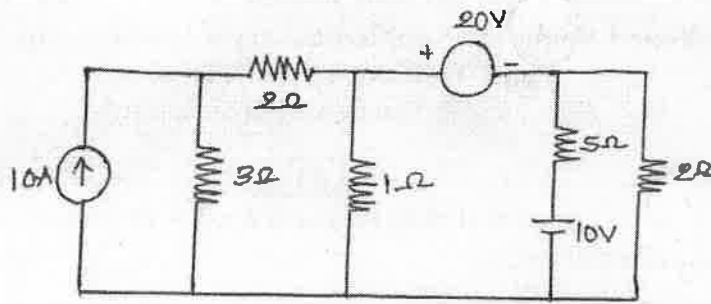- 7 Determine current in  $5\Omega$  resistor for the circuit shown in figure using CO3 L3 10M network topology




UNIT-IV

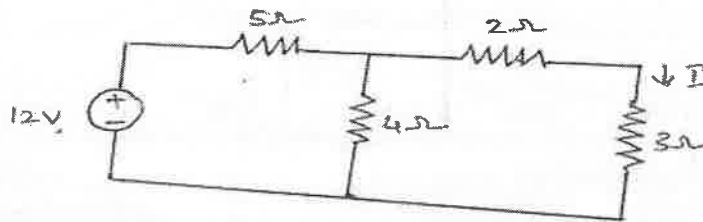- 8 Verify Reciprocity Theorem for the network shown in figure CO4 L2 10M



OR

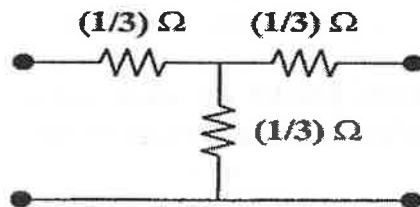- 9 Determine Y parameters of the following network CO4 L3 10M



UNIT-V

- 10 Find the signal  $y(t)$ , the Laplace transform of signal which is  $Y(S) =$  CO5 L3 10M

$$\frac{S^3 + 7S^2 + 18S + 20}{S^2 + 5S + 6}$$

OR

- 11 A  $500\Omega$  resistor, a  $16\text{mH}$  inductor, and a  $25\text{nF}$  capacitor are connected in parallel which is placed in series with a  $2000\Omega$  resistor. Express the impedance of this series combination as a rational function of  $s$

\*\*\* END \*\*\*