

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations June-2024
ELECTRONIC DEVICES

(Electronics and Communications Engineering)

Time: 3 Hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | | | |
|---|---|--|-----|----|----|
| 1 | a | What is depletion region? | CO1 | L1 | 2M |
| | b | Compare half wave rectifier and Full wave rectifier. | CO2 | L2 | 2M |
| | c | What do you mean by Punch through Effect? | CO3 | L3 | 2M |
| | d | Draw the generalized hybrid model for BJT amplifier. | CO4 | L2 | 2M |
| | e | What is transconductance of JFET? | CO5 | L1 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|-----------|---|---|-----|----|----|
| 2 | a | What is a PN Junction? Explain the formation of depletion layer in a PN junction. | CO1 | L2 | 5M |
| | b | Discuss the differences between Ideal Diode and Practical Diode. | CO1 | L2 | 5M |
| OR | | | | | |
| 3 | a | Write notes on Breakdown in PN Junction diodes. | CO1 | L2 | 5M |
| | b | Find the factor by which the reverse saturation current of a silicon diode will get Multiplied when the temperature is increased from 27°C to 82°C. | CO1 | L3 | 5M |

UNIT-II

- | | | | | | |
|-----------|---|--|-----|----|----|
| 4 | a | Draw the circuit diagram of half wave rectifier and explain its operation with the help Of waveforms. | CO2 | L2 | 5M |
| | b | Derive the expressions for Ripple Factor and Efficiency of Half Wave Rectifier. | CO2 | L1 | 5M |
| OR | | | | | |
| 5 | a | Explain the working of capacitor filter and derive the expression for ripple factor of capacitor filter. | CO2 | L3 | 5M |
| | b | Derive the expression for ripple factor of inductor filter. | CO2 | L3 | 5M |

UNIT-III

- | | | | | | |
|---|--|--|-----|----|-----|
| 6 | | Discuss the Input and Output characteristics of a BJT in CE Configuration. Indicate the regions of operations in the output characteristics. | CO3 | L2 | 10M |
|---|--|--|-----|----|-----|

OR

- | | | | | | |
|---|--|--|-----|----|-----|
| 7 | | Derive the stability factors S, S' and S'' of a Transistor Voltage Divider bias. | CO3 | L3 | 10M |
|---|--|--|-----|----|-----|

UNIT-IV

- | | | | | | |
|---|--|--|-----|----|-----|
| 8 | | Using low frequency h-parameter model, derive the expressions for voltage gain, current gain, input impedance and output admittance for a BJT Amplifier in CE configuration. | CO4 | L3 | 10M |
|---|--|--|-----|----|-----|

OR

- 9 A CE amplifier is driven by a voltage source of internal resistance $R_s = 800\Omega$ and the load impedance of $R_L = 1000\Omega$. The h-parameters are $h_{ie} = 1k$, $h_{fe} = 50$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Calculate current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. **CO4 L3 10M**

UNIT-V

- 10 Discuss the operation and characteristics of n-channel depletion type MOSFET with diagram. **CO5 L2 10M**

OR

- 11 Derive input impedance, output impedance and voltage gain of JFET Common Drain amplifier with neat diagram. **CO5 L2 10M**

***** END *****