

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations June-2024

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Mechanical Engineering)

Time: 3 Hours


Max. Marks: 60

(Answer all Six Units, 6*10=60 Marks)

PART-A

UNIT-I

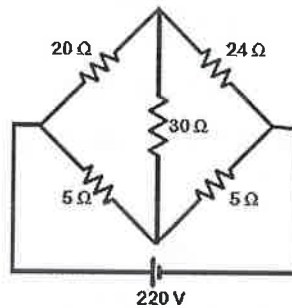- 1 Find the current delivered by the source for the circuit shown in figure. CO1 L3 10M




OR

- 2 a State and explain Ohm's law. CO1 L2 5M
b Explain in detail about passive elements. CO1 L2 5M

UNIT-II

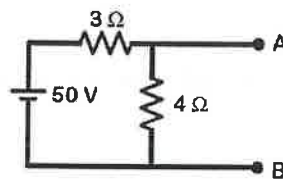- 3 a State Norton's theorem. CO2 L1 2M
b Find Norton's equivalent circuit across AB for the circuit shown. CO2 L3 8M



OR

- 4 Explain in detail about admittance or 'Y' parameters with an example. CO2 L2 10M

UNIT-III

- 5 a Derive Torque equation of a dc motor. CO3 L3 5M
b The counter emf of Shunt motor is 227 V. The field resistance is 160Ω and field current 1.5A. If the line current is 36.5A, find the armature resistance also find armature current when the motor is stationary. CO3 L3 5M

OR

- 6 Explain in detail about various transformer losses. CO3 L2 10M

PART-B

UNIT-IV

- 7 a What is Doping? Explain P and N-type semiconductors in detail. CO4 L2 5M
b Explain Drift and Diffusion currents in a PN Junction Diode. CO4 L2 5M

OR

- 8 a Explain the working principle of Full Wave Rectifier. Draw its input and Output waveforms. CO4 L2 5M
b Derive the expression for Ripple factor and Efficiency of Full Wave Rectifier. CO4 L3 5M

UNIT-V

- 9 a Explain the operation of PNP transistor with a neat diagram. CO5 L2 5M
b Explain the various types of circuit configurations, which can be obtained from a bipolar junction transistor? CO5 L2 5M

OR

- 10 a Explain in detail about the transistor working as a amplifier. CO5 L2 5M
b Write the applications of a transistor and also explain when it is acting as a switch? CO5 L2 5M

UNIT-VI

- 11 a Explain the construction and principle of operation of N-channel JFET. CO6 L2 5M
b Explain the transfer characteristics of JFET. CO6 L2 5M

OR

- 12 a Write the applications of MOSFET. CO6 L1 5M
b Explain the static characteristics of MOSFET and draw its characteristics. CO6 L2 5M

***** END *****