

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations May/June-2024

DIGITAL LOGIC DESIGN

(Common to CSE & CSIT)

Time: 3 Hours

(Answer all Five Units 5 x 12 = 60 Marks)

Max. Marks: 60

UNIT-I

- 1 a (i) Convert $(0.6875)_{10}$ to binary. CO1 L1 6M
 (ii) Using 10's complement, subtract $72532 - 3250$.
 b (i) Draw the graphic symbols and truth tables of the eight digital logic gates. CO1 L2 6M
 (ii) Write short notes on different digital logic families of digital integrated circuits.

OR

- 2 a Express the following function as a sum of minterms CO1 L4 6M
 $F(A,B,C,D) = B'D + A'D + BD$
 b Express the complement of the following function in sum-of-minterms form: CO1 L4 6M
 $F(A,B,C,D) = \Sigma(3,5,9,11,15)$

UNIT-II

- 3 a Draw the logic diagram of a parity generator and checker and explain it. CO2 L3 6M
 b Draw the multi-level NAND circuit for the following expression: CO2 L3 6M
 $w(x+y+z) + xyz$

OR

- 4 a Simplify the following Boolean functions, using three-variable maps: CO2 L2 6M
 (a) $F(x, y, z) = \Sigma(0,2,6,7)$
 (b) $F(x, y, z) = \Sigma(0,2,3,4,6)$
 b Give three possible ways to express the following Boolean function with eight or fewer literals: CO2 L2 6M
 $F = B'C'D' + AB'CD' + BC'D + A'BCD$

UNIT-III

- 5 a Brief Combinational circuit and draw the block diagram of combinational circuit. CO3 L5 6M
 b Elaborate the analysis procedure of a combinational circuit with a logic diagram. CO3 L2 6M

OR

- 6 a Explain how to implement a Half Adder. CO3 L5 6M
 b Construct 4 x 16 decoder with two 3 x 8 decoders CO3 L6 6M

UNIT-IV

- 7 a Reduce the number of states in the following state table, and tabulate the reduced state table: CO4 L6 6M

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

- b What is shift register? Enumerate the types of shift registers. Give few applications of shift registers. CO4 L1 ()

OR

- 8 a Discuss Ring counter and Johnson Counter. CO4 L6 6M
 b Explain JK flip flop and show how the JK Flip Flop removes the drawbacks of SR Flip Flop. CO4 L2 6M

UNIT-V

- 9 a Elucidate Memory unit and its types with a neat block diagram. CO5 L2 6M
 b Discuss types of Read only Memory in detail. CO5 L6 6M

OR

- 10 a Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number. CO5 L6 6M
 b Implement the following two Boolean functions with a PLA: CO5 L2 6M
 $F_1(A, B, C) = \sum(0, 1, 2, 4)$
 $F_2(A, B, C) = \sum(0, 5, 6, 7)$

*** END ***