

✓

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year II Semester Supplementary Examinations May/June-2024**

**ELECTRONIC CIRCUIT ANALYSIS**

(Electronics and Communication Engineering)

**Time: 3 Hours**

**Max. Marks: 60**

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 a Sketch the Hybrid- $\pi$  model and explain the significance of each and every component in it. CO1 L3 6M
- b Deduce the expression for Emitter diffusion capacitance of CE transistor at high frequency. CO1 L4 6M

OR

- 2 With the help of necessary circuit diagrams and approximations, deduce the expression for CE short circuit current gain and derive the relation between  $f\beta$  and  $f_T$ . CO2 L4 12M

**UNIT-II**

- 3 Deduce the expressions of Gain, input and output resistances for a Voltage Shunt feed back amplifier. CO2 L4 12M

OR

- 4 a Explain the effect of negative feedback on input resistance for Current shunt and Voltage shunt Feedback amplifier. CO2 L2 6M
- b Compare various types of feedback amplifiers. CO2 L4 6M

**UNIT-III**

- 5 a Establish the condition for oscillation with suitable diagram. CO2 L3 8M
- b Classify various types of oscillators. CO1 L2 4M

OR

- 6 Analyze an LC Oscillator for a necessary equation to determine criteria for oscillations. CO2 L4 12M

**UNIT-IV**

- 7 a Discuss about Transformer coupled Class A Power Amplifier with diagram and determine its Maximum efficiency. CO4 L3 6M
- b A Class B push pull amplifier drives a load of  $16\Omega$ , connected to the secondary of ideal transformer. The  $V_{cc}$  is 25V. If number of turns on primary is 200 and secondary is 50. Determine maximum power output, DC power input and efficiency. CO4 L3 6M

OR

- 8 Discuss about Double Tuned Amplifier with neat diagram and deduce the expression for its bandwidth. CO2 L4 12M

**UNIT-V**

- 9 a What is a Monostable multivibrator? Explain its working with the help of waveforms. CO2 L2 6M
- b Deduce the expression for pulse width,  $T$  of collector coupled Monostable multivibrator. CO2 L4 6M

OR

- 10 a Calculate the component values of a Monostable multivibrator developing an output pulse of  $140\mu\text{s}$  duration. Assume  $h_{FEmin} = 20$ ,  $I_{c(sat)} = 6\text{ mA}$ ,  $V_{CC} = 6\text{ V}$ ,  $V_{BB} = -1.5\text{ V}$ . CO3 L4 6M
- b Design and draw a saturated collector coupled monostable multivibrator for the following specifications:  $V_{CC} = 10\text{ V}$ ,  $V_{BB} = -5\text{ V}$ , pulse duration =  $12\text{ ms}$ ,  $I_{C(ON)} = 2\text{ mA}$  and two NPN transistors with minimum  $h_{fe} = 100$  and  $I_{CBO} = 0$ . CO3 L6 6M

\*\*\* END \*\*\*