

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations May/June-2024

NETWORK ANALYSIS

(Electronics & Communication Engineering)


Time: 3 Hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)


UNIT-I

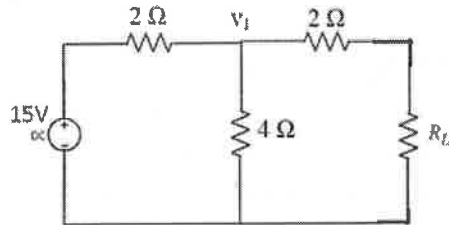- 1 a What is the condition for maximum power transfer to the load? CO1 L3 6M
- b Find Thevenin's equivalent for the following circuit CO1 L3 6M



OR

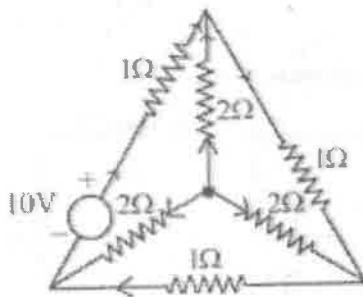- 2 a Define and state the properties of incidence matrix. CO1 L2 6M
- b For the network shown below draw the graph and find incidence and tie set matrices. CO1 L3 6M



UNIT-II

- 3 a Explain the phasor relation for R,L,C elements. CO1 L3 6M
- b A resistor of 50Ω, inductance of 100mH and a capacitance of 100μF are connected in series across 200V, 50Hz supply. Determine the following (i) Impedance (ii) current flowing through the circuit (iii) power factor (iv) voltage across R,L &C (v) power in watts CO1 L3 6M

OR

- 4 a Explain the phasor relation for parallel RLC circuit. CO1 L2 6M
- b A parallel RLC circuit is supplied with a voltage source of 230 V, 50Hz. Determine circuit current and power factor if R=40Ω, L=0.2H and C=50μF. CO1 L3 6M

UNIT-III


- 5 Obtain the expression for resonant frequency, bandwidth and Q-factor for Series R-L-C circuit. CO2 L3 12M

OR

- 6 a In a parallel resonance circuit (Tank circuit) $R=2\Omega$, $L=1\text{mH}$ and $C=10\mu\text{F}$, Find the Resonant frequency, Dynamic impedance and Bandwidth. CO2 L3 6M
- b Obtain the expression for resonant frequency for parallel RL-RC circuit. CO2 L3 6M

UNIT-IV

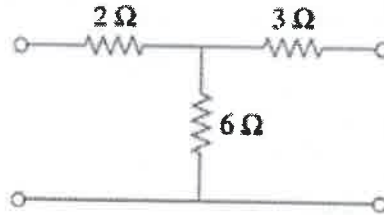- 7 a Find the Y- parameters for the following circuit. CO2 L3 6M



- b Express h parameters in terms of ABCD parameters. L3 6M
- OR**
- 8 a What are the advantages of state variable analysis. CO2 L3 6M
- b The transfer function of a system is $G(s)=2/(s+1)(s+2)$. Obtain a state variable representation for the system. CO2 L3 6M

UNIT-V

- 9 a What is a filter? Explain about various types of filters. CO3 L2 6M
- b Explain the classification of pass band and stop band in detail. CO3 L2 6M
- OR**
- 10 What is high pass filter. Explain the general configuration and parameters of a constant-K high pass filter. CO3 L2 12M

*** END ***