

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR** ✓  
(AUTONOMOUS)

**B.Tech II Year II Semester Supplementary Examinations May/June-2024**

**ANALOG CIRCUITS**

**(Electronics and Communication Engineering)**

**Time: 3 Hours**

**Max. Marks: 60**

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- |   |   |  |     |    |    |
|---|---|--|-----|----|----|
| 1 | a | What is cutoff frequency, $f_{\beta}$ and write down its expression.                           | CO1 | L2 | 2M |
|   | b | Compare the performance of various feedback amplifiers.  | CO2 | L2 | 2M |
|   | c | What are the differences between Push Pull and Complementary symmetry class B power amplifier? | CO3 | L1 | 2M |
|   | d | List the characteristics of an ideal opamp.  | CO4 | L1 | 2M |
|   | e | Mention the types of DACs.   | CO5 | L1 | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |   |  |  |     |    |     |
|---|--|--|-----|----|-----|
| 2 |  | With the help of necessary circuit diagrams and approximations obtain the expression for CE short circuit current gain and derive the relation between $f_{\beta}$ and $f_T$ . | CO1 | L2 | 10M |
|---|--|--|-----|----|-----|

**OR**

- |   |   |   |     |    |    |
|---|---|---|-----|----|----|
| 3 | a | Explain the effect of cascading on bandwidth of multistage amplifier.   | CO1 | L2 | 6M |
|   | b | If the overall lower and higher cutoff frequencies of a two identical amplifier cascade are 600 Hz and 18 kHz respectively, compute the values of individual cutoff frequencies of both the amplifier stages. | CO1 | L3 | 4M |

**UNIT-II**

- |   |  |   |     |    |     |
|---|--|---|-----|----|-----|
| 4 |  | Describe the working principle of Wein bridge oscillator and derive the expression for frequency of oscillations. | CO2 | L2 | 10M |
|---|--|---|-----|----|-----|


**OR**

- |   |   |  |     |    |    |
|---|---|--|-----|----|----|
| 5 | a | Describe the working principle of Colpitts oscillator and derive the expression for frequency of oscillations.   | CO2 | L2 | 8M |
|   | b | In the Colpitts oscillator, $C_1 = 0.2\mu\text{F}$ and $C_2 = 0.02\mu\text{F}$ . If the frequency of oscillation is 10kHz, find the value of inductor. | CO2 | L3 | 2M |

**UNIT-III**

- |   |   |   |     |    |    |
|---|---|---|-----|----|----|
| 6 | a | With neat diagram explain Series fed, Directly coupled Class A Power Amplifier and derive its maximum efficiency. | CO3 | L2 | 5M |
|---|---|---|-----|----|----|

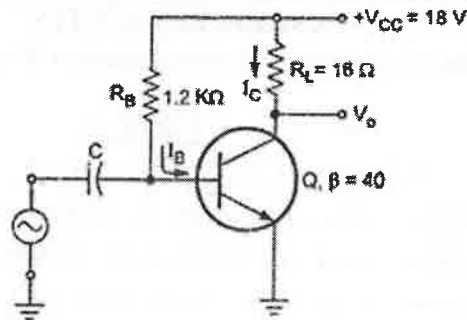- b A series fed Class A amplifier shown in the Fig, operates from dc source  $+V_{CC} = 18V$  and applied sinusoidal input signal generates peak base current  $9mA$ . Calculate : (i) Quiescent current  $I_{CQ}$ , (ii) Quiescent voltage  $V_{CEQ}$ , (iii) DC



input power  $P_{DC}$ , (iv) AC output power  $P_{AC}$  and (v) Efficiency.

OR

- 7 a Discuss with diagram, Transformer coupled Class A Power Amplifier and derive its Maximum efficiency. CO3 L1 5M  
 b A Class B push pull amplifier drives a load of  $16\Omega$ , connected to the secondary of ideal transformer. The  $V_{CC}$  is  $25V$ . If number of turns on primary is 200 and secondary is 50. Calculate maximum power output, DC power input and efficiency. CO3 L3 5M

#### UNIT-IV

- 8 a Draw a non inverting amplifier using an opamp and derive the expression for its closed loop voltage gain. CO4 L2 5M  
 b Draw the circuit diagram of a Differential Amplifier and derive the expression for its output voltage. Write about difference and common mode gains. CO4 L2 5M

OR

- 9 Explain the Schmitt Trigger with neat circuit diagram, input and output waveforms. CO4 L2 10M

#### UNIT-V

- 10 a Draw a First order low pass active filter and derive the transfer function its frequency response. CO5 L2 5M  
 b Design a second order Butterworth low pass filter having upper cutoff frequency of  $1KHz$ . CO5 L3 5M

OR

- 11 Draw the circuit diagram of inverted R-2R ladder DAC network. Explain its working. List out the advantages over R-2R ladder network. CO5 L2 10M

\*\*\* END \*\*\*