

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B Tech II Year II Semeste Supplementary Examinations May/June-2024**  
**BASIC ELECTRICAL & ELECTRONICS ENGINEERING**

(Mechanical Engineering)

**Time: 3 Hours**

**Max. Marks: 60**

(Answer all Six Units 6 X 10 = 60 Marks)


**PART-A**

**UNIT-I**

- 1 Three resistances of values 20, 30 and 50 are connected in series across 20 V DC supply. Calculate, CO1 L3 10M  
 i) Equivalent resistance of the circuit.  
 ii) Total current from the supply.  
 iii) Voltage drop across each resistor.  
 iv) Power dissipated in each resistor

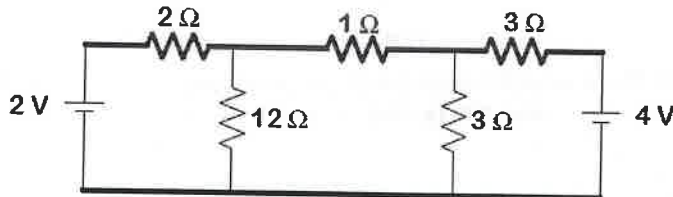
**OR**

- 2 Find the current through 12Ω resistor for the given circuit using Kirchoff's laws. CO1 L3 10M



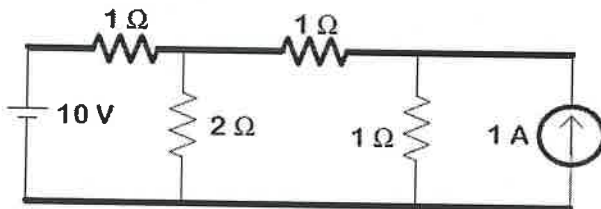
**UNIT-II**

- 3 Calculate the current in 20Ω resistor in the given circuit using super position theorem. CO2 L3 10M



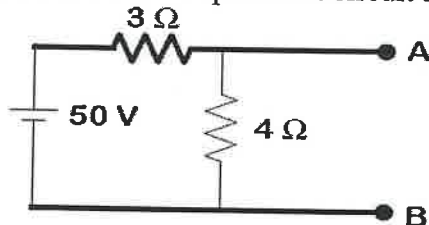**OR**

- 4 Find Norton's equivalent circuit across AB for the circuit shown. CO2 L3 10M



**UNIT-III**

- 5 Discuss about the principle of operation and constructional Details of DC motor. CO3 L2 10M

**OR**

- 6 a Derive EMF equation of a transformer CO3 L3 5M  
 b A 100 kVA, 11000/400 V, 50 Hz transformer has 40 secondary turns. Calculate the number of primary turns and primary and secondary currents. CO3 L3 5M

**PART-B**

**UNIT-IV**

7 Discuss the conduction properties of semiconductors and explain the process of electron hole Pair generation and recombination. **CO4 L3 10M**

**OR**

8 Explain the working of a PN junction diode when it is connected in forward bias and reverse bias. Draw VI Characteristics of PN Junction Diode. **CO4 L2 10M**

**UNIT-V**

9 Draw the circuit diagram for a common base circuit arrangement and plot its input and Output characteristics. Show the different regions of the output characteristics and explain their occurrence. **CO5 L3 10M**

**OR**

10 With neat circuit diagram and equations, explain Fixed Bias circuit of BJT. **CO5 L2 10M**

**UNIT-VI**

11 a Explain the construction and principle of operation of N-channel JFET. **CO6 L2 5M**  
b Define the JFET Volt-Ampere Characteristics and determine FET parameters. **CO6 L2 5M**

**OR**

12 Explain the CS configuration With construction and its operation. **CO6 L2 10M**

**\*\*\* END \*\*\***