

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year II Semester Regular & Supplementary Examinations June-2024**

**ELECTRONIC CIRCUIT ANALYSIS**  
(Electronics & Communications Engineering)

**Time: 3 Hours**

**Max. Marks: 60**

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- |   |   |     |    |    |
|---|---|-----|----|----|
| 1 | a Draw the Hybrid- $\pi$ model and explain the significance of each and every component in it.                | CO1 | L3 | 4M |
|   | b Deduce the expressions for the hybrid $\pi$ parameters $g_m$ , $g_b'e$ , $g_b'c$ , $r_{bb}'$ and $g_{ce}$ . | CO4 | L4 | 8M |

OR

- |   |   |     |    |     |
|---|---|-----|----|-----|
| 2 | Define Coupling and explain various types of coupling mechanisms used in multistage amplifiers. | CO2 | L2 | 12M |
|---|---|-----|----|-----|

**UNIT-II**

- |   |   |     |    |    |
|---|---|-----|----|----|
| 3 | a Explain in detail about the basic Amplifiers used in Feedback amplifiers. | CO3 | L2 | 6M |
|   | b Explain Feedback amplifier topologies with necessary diagrams.            | CO3 | L2 | 6M |

OR

- |   |  |     |    |    |
|---|--|-----|----|----|
| 4 | a Show that negative feedback reduces gain of an Amplifier.  | CO4 | L2 | 4M |
|   | b Analyze the effect of negative feedback on Output resistance for Voltage series and Current series feedback amplifier. | CO5 | L4 | 8M |

**UNIT-III**

- |   |   |     |    |    |
|---|---|-----|----|----|
| 5 | a Construct RC phase shift oscillator using BJT and deduce its expression for frequency of oscillations.  | CO4 | L4 | 6M |
|   | b Determine the frequency of oscillations when a RC phase shift oscillator has $R=10k\Omega$ , $C=0.01\mu F$ and $RC = 2.2 K\Omega$ . Also find the minimum current gain needed for this purpose. | CO5 | L3 | 6M |

OR

- |   |  |     |    |    |
|---|--|-----|----|----|
| 6 | a Explain the working of a Crystal oscillator and sketch its characteristics.  | CO4 | L3 | 8M |
|   | b In a transistorized Hartley oscillator, the two inductances are 2 mH and 20 $\mu H$ while the frequency is to be changed from 950 KHz to 2050 KHz. Calculate the range over which the capacitor is to be varied. | CO6 | L3 | 4M |

**UNIT-IV**

- |   |  |     |    |    |
|---|--|-----|----|----|
| 7 | a Classify the Large Signal Power Amplifier based on biasing condition.  | CO2 | L4 | 6M |
|   | b Discuss about Transformer coupled Class A Power Amplifier with diagram and determine its Maximum efficiency. | CO2 | L3 | 6M |

OR

- |   |   |     |    |     |
|---|---|-----|----|-----|
| 8 | Compare different types of tuned amplifiers with suitable circuit diagrams. | CO1 | L2 | 12M |
|---|---|-----|----|-----|

**UNIT-V**

- |   |  |     |    |    |
|---|--|-----|----|----|
| 9 | a Define multivibrator? List out the types of multivibrators.  | CO1 | L1 | 4M |
|   | b With a neat circuit diagram explain the working of a collector coupled Astable multivibrator and draw the necessary waveforms. | CO3 | L2 | 8M |

OR

- |    |  |     |    |    |
|----|--|-----|----|----|
| 10 | a Explain the operation of the Emitter Coupled Monostable multivibrator. | CO3 | L2 | 8M |
|    | b List the applications of Monostable multivibrator.                     | CO1 | L1 | 4M |

\*\*\* END \*\*\*

