

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Regular & Supplementary Examinations June-2024
LINEAR & DIGITAL IC APPLICATIONS
(Electronics & Communications Engineering)

Time: 3 Hours**Max. Marks: 60**

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Determine the output voltage of a differential Amplifier for the input voltages of $300\mu\text{V}$ & $240\mu\text{V}$. The Differential gain of the amplifier is 5000. the value of the CMRR is 100. CO1 L3 6M
- b Draw the block diagram of Op-Amp and explain each block. CO2 L1 6M

OR

- 2 a Draw the circuit and explain the working of Current to voltage converter. CO4 L1 6M
- b Explain about the operation of sample and hold circuit with relevant waveforms and neat sketch. CO4 L2 6M

UNIT-II

- 3 a List the types of Filters. CO1 L1 2M
- b Derive the gain of a 1st order high pass Butterworth filter CO4 L3 10M

OR

- 4 a Draw the free running oscillator using 555 timer and also derive the expression for frequency of oscillation. CO2 L3 8M
- b List out any four application of multivibrator. CO1 L1 4M

UNIT-III

- 5 a Draw and Explain the block diagram of Monolithic IC 565. CO2 L2 6M
- b Explain the basic structure of DAC. CO2 L2 6M

OR

- 6 a Discuss about low voltage CMOS and Interfacing. CO5 L2 6M
- b Explain in detail about basic ECL logic circuit. CO5 L2 6M

UNIT-IV

- 7 a Explain the various data types supported by VHDL. Give the necessary examples. CO5 L2 6M
- b Discuss about constants and arrays with an example. CO6 L2 6M

OR

- 8 Design the logic circuit and write VHDL program for the following function. $F(Y) = \Pi A, B, C, D (1, 4, 5, 7, 9, 11, 12, 13, 15)$. CO6 L4 12M

UNIT-V

- 9 a Design a 4 to 16 decoder with 74×138 IC's. CO6 L3 6M
- b Design a 16-bit comparator using 74×85 ICs. CO5 L3 6M

OR

- 10 a Distinguish between the synchronous and asynchronous counters. CO6 L4 6M
- b Design an 8-bit serial in and parallel out shift register. CO6 L3 6M

*** END ***

July

1918

1918

1918

1918

1918

1918

1918